


**AI CONTENT FOR**

**DIPLOMA IN ELECTRICAL ENGINEERING**

**AC Fundamental**

**Subject Code: DI02000171**

**Semester: 2**

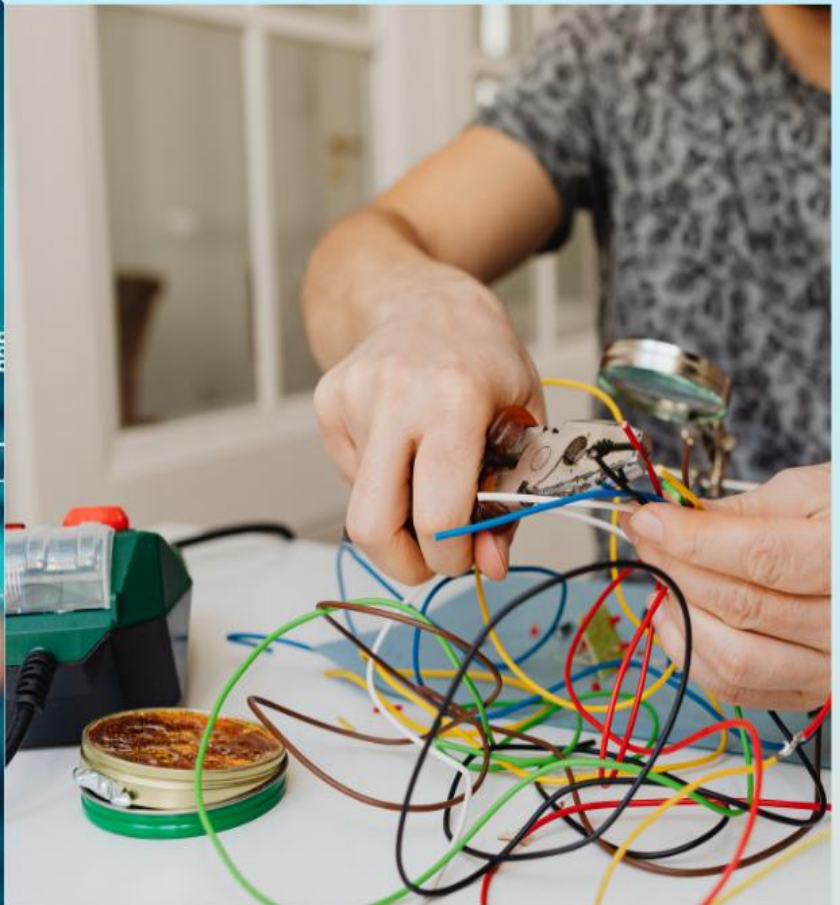

**Directorate of Technical Education**

**Gujarat**

# DISCLAIMER FOR AI-ASSISTED ACADEMIC CONTENT

## Disclaimer for AI-Assisted Content and Copyright Compliance

This academic content, including but not limited to **study plans, lecture notes, descriptive content, student toolkits, question banks, model question papers, digital resources, and supplementary materials**, has been developed with the assistance of **Artificial Intelligence (AI) tools**, under the guidance and supervision of subject experts.

While due care has been taken to ensure quality, relevance, and academic usefulness, users are requested to note the following:

### 1. Accuracy and Academic Responsibility

AI-assisted systems may occasionally generate information that is **incomplete, simplified, or unintentionally inaccurate**. Faculty members and students are strongly advised to:

- Cross-verify critical information with **standard textbooks, official syllabi, and faculty guidance**
- Use this material as a **supporting academic resource**, not as the sole source of learning

### 2. Nature of Use

This content is intended **strictly for educational and non-commercial purposes**, including:

- Classroom teaching
- Student self-learning
- Institutional academic use within the state

It is **not intended for commercial publication, resale, or profit-oriented distribution**.

### 3. Role of Human Oversight

AI-generated content may not always capture **discipline-specific nuances, contextual depth, or recent advancements**. Therefore:

- Faculty review, contextualization, and explanation remain essential
- Practical learning, laboratory work, and instructor-led teaching are indispensable

### 4. Copyright and Image Usage Compliance

Special care has been taken regarding the use of **images, diagrams, figures, and visual elements** included or referenced in this material.

All visuals used in this content fall under **one or more** of the following categories:

- **Original diagrams** created or redrawn by faculty/authors
- AI-generated images or diagrams
- AI generated content for Computer Networking – Hitesh Panchal 2
- Content sourced from **public domain or Creative Commons–licensed resources**, with attribution where applicable

Images have **not** been intentionally copied from copyrighted textbooks, paid publications, or restricted online sources.

Any references to images, videos, animations, or visual resources are provided **purely for academic illustration** and with the understanding that:

- Their use complies with applicable **copyright laws**
- Institutions and users will adhere to **license terms and attribution requirements**, wherever applicable

#### **5. Disclaimer on Inadvertent Inclusion**

If any copyrighted material has been **unintentionally included**, such inclusion is **purely incidental and unintentional**. The concerned material will be **removed or replaced promptly** upon notification by the rightful copyright holder.

#### **6. Distribution and Sharing**

This content may be:

- Shared among **students and faculty within the state**
- Uploaded to **institutional LMS, academic portals, or official repositories**

However, **unauthorized modification, commercial redistribution, or external publication** without institutional approval is discouraged.

#### **7. Acceptance of Terms**

By accessing or using this material, users acknowledge that:

- They understand the **AI-assisted nature** of the content
- They accept responsibility for **academic verification and ethical use**
- They agree to abide by **copyright, academic integrity, and institutional guidelines**

**We encourage learners and educators to actively engage with the material, question concepts, apply critical thinking, and complement this content with authoritative academic resources and expert instruction.**

## Table of Contents

Sr. No.	Topic / Chapter	Subtopic / Section	Page No.
<b>1</b>	<b>Unit 1: Fundamentals of Alternating Voltage &amp; Current</b>	<b>Study Plan &amp; Strategic Breakdown</b>	<b>1</b>
1.1		Lecture 1: Comparison between AC and DC Systems	2–3
1.2		Lecture 2: Generation of Alternating Voltage (Faraday’s Law)	4–5
1.3		Lecture 3: Sinusoidal Function Terminology	6–7
1.4		Lecture 4: Values of AC Quantities (RMS, Avg, Peak)	8–9
1.5		Lecture 5: Phase Difference (Lagging & Leading)	10–11
1.6		Lecture 6: Vector Representation of Alternating Quantity	12–13
1.7		Lecture 7: Addition of Alternating Quantities (Vector Methods)	14–15
1.8		Lecture 8: Vector Transformations (Rectangular & Polar)	16–17
1.9		Lecture 9: Mathematical Operations of Vectors	18–19
1.10		Lecture 10: Numerical Mastery & Problem Solving	20–21
1.11	<b>Unit 1 Resources &amp; Assessment</b>	AI Tools & Digital Learning Repository	22
		Beyond the Syllabus: Emerging Technologies	23

Sr. No.	Topic / Chapter	Subtopic / Section	Page No.
		Predicted Question Bank (Unit 1)	24–25
<b>2</b>	<b>Unit 2: Single Phase AC Series Circuits</b>	<b>Study Plan &amp; Weightage</b>	<b>26</b>
2.1		Lecture 1: AC through Pure R, L, and C Circuits	27–28
2.2		Lecture 2: Behavior of RL, RC, and RLC Series Circuits	29–30
2.3		Lecture 3: Power Factor (Lagging, Leading, Unity)	31–32
2.4		Lecture 4: The Power Triangle (Active, Reactive, Apparent)	33–34
2.5		Lecture 5: Series Resonance & Resonant Frequency	35–36
2.6		Lecture 6: Numerical Problem Solving (Series Circuits)	37–38
2.7	<b>Unit 2 Resources &amp; Assessment</b>	Mastery Check: Key Definitions & Glossary	39
		AI Tools, Digital Labs & Video Repository	40
		Predicted Question Bank (Unit 2)	41–42
<b>3</b>	<b>Unit 3: Single Phase AC Parallel Circuits</b>	<b>Study Plan &amp; Topic Sequence</b>	<b>43</b>
3.1		Topic 1: Phasor Method for Parallel Circuits	44–45
3.2		Topic 2: Admittance, Conductance & Susceptance	46–47
3.3		Topic 3: The Admittance Method (Solving Parallel Circuits)	48–49

Sr. No.	Topic / Chapter	Subtopic / Section	Page No.
3.4		Topic 4: Complex Algebra Method	50–51
3.5		Topic 5: Parallel Resonance Condition	52–53
3.6		Topic 6: Comparison: Series vs. Parallel Resonance	54–55
3.7		Topic 7: Numerical Problem Solving (Parallel Circuits)	56–57
3.8	<b>Unit 3 Resources &amp; Assessment</b>	Mastery Check: Glossary & FAQs	58
		Digital Resource Library & External Exposure	59
		Predicted Question Bank (Unit 3)	60–61
<b>4</b>	<b>Unit 4: Three Phase System and Circuits</b>	<b>Strategic Study Plan</b>	<b>62</b>
4.1		Topic 1: Comparison of Single Phase vs. Three Phase Systems	63–64
4.2		Topic 2: Generation of Three Phase Alternating Voltage	65–66
4.3		Topic 3: Three Phase Terminology (Phase Sequence, Balanced Load)	67–68
4.4		Topic 4: Line vs. Phase Values (Voltage & Current)	69–70
4.5		Topic 5: Three Phase Star Connection (Y)	71–72
4.6		Topic 6: Three Phase Delta Connection ( $\Delta$ )	73–74
4.7		Topic 7: Numerical Problem Solving (Star & Delta)	75–76

Sr. No.	Topic / Chapter	Subtopic / Section	Page No.
4.8	<b>Unit 4 Resources &amp; Assessment</b>	Student AI Toolkit & Mastery Check	77
		External Exposure Module (Smart Grids, Field Visits)	78
		Predicted Question Bank (Unit 4)	79–80



## Unit 1: Study Plan- Fundamentals of Alternating Voltage and Current

Sr. No	Topic Breakdown	Sequence / Level	Topic Category	Suggested Hours	Exam Importance	Practical Relevance
1.1	<b>Introduction to AC &amp; DC:</b> Differences, advantages, and limitations.	Introductory	Supporting	1 Hr	Moderate	High (System Selection)
1.2	<b>Generation of Alternating Voltage:</b> Faraday's Law application, waveform production.	Introductory	<b>Core</b>	2 Hrs	High	Essential (Power Plants)
1.3	<b>AC Terminology:</b> Cycle, Frequency, Time Period, Amplitude.	Intermediate	Supporting	1 Hr	High	Fundamental (Testing)
1.4	<b>Sinusoidal Waveform Values:</b> Average value, RMS value, Form factor, Peak factor.	Intermediate	<b>Core</b>	3 Hrs	<b>Critical</b>	High (Meter Readings)
1.5	<b>Phasor Representation:</b> Polar and Rectangular forms, phase	Advanced	<b>Core</b>	2 Hrs	High	Essential (Circuit Analysis)

Sr. No	Topic Breakdown	Sequence / Level	Topic Category	Suggested Hours	Exam Importance	Practical Relevance
	difference, lagging/leading.					
1.6	<b>AC through Pure R, L, and C:</b> Voltage-current relationship, power in pure circuits.	Advanced	Application	3 Hrs	<b>Critical</b>	Industrial (Load Study)

### Strategic Breakdown for Success

- **Core Topics:** These are the "must-know" concepts. You cannot master electrical engineering without a deep understanding of **RMS values** and **Phasor Algebra**.
- **Logical Flow:** We start with the "Why" (DC vs. AC), move to the "How" (Generation), define the "What" (Terminology), and conclude with the "Application" (R-L-C circuits).
- **Diploma-Level Depth:** Our focus is on conceptual clarity and practical calculation rather than abstract mathematical proofs, ensuring you are "industry-ready".

### Outcome-Based Education (OBE) Objectives

By the end of this unit, you will be able to:

1. Differentiate between AC and DC systems effectively.
2. Calculate various parameters of a sinusoidal wave for equipment rating.
3. Analyse the behaviour of basic components under AC supply

### Lecture 1: Comparison between AC and DC Systems

**Branch:** Electrical Engineering / Renewable Energy

**Unit 1:** Fundamentals of Alternating Voltage and Current **Time:** 60 Minutes

#### 1. Hook / Introduction (≈ 5 minutes)

Think about the smartphone in your pocket and the ceiling fan spinning above you. Did you know they "speak" two different electrical languages? Your phone battery runs on **Direct Current (DC)**, but the wall socket powering your charger provides **Alternating Current (AC)**. Why do we use both?

In the late 1880s, two great inventors, Thomas Edison and Nikola Tesla, fought the "War of Currents" over this very question. Today, we learn why Tesla's AC eventually won the battle for our power grids, while Edison's DC still rules our electronic gadgets. Understanding this choice is the first step to becoming a master "Electrical Technocrat."

---

## 2. Core Concepts (≈ 40 minutes)

### What is Direct Current (DC)?

DC is like a steady stream of water flowing in one direction through a pipe. The electrons move from the negative terminal to the positive terminal at a constant magnitude over time.


- **Source:** Batteries, Solar Cells, DC Generators.
- **Visual:** Imagine a straight horizontal line on a graph where the Y-axis is Voltage and the X-axis is Time.

### What is Alternating Current (AC)?

AC is like the tides of the ocean, moving back and forth. The magnitude and direction of the current change periodically. It reaches a maximum value, returns to zero, and then repeats in the opposite direction.

- **Source:** AC Generators (Alternators) found in power plants.
- **Visual:** Draw a "Sinusoidal Waveform"—a smooth, repeating S-curve that goes above and below the zero-line.

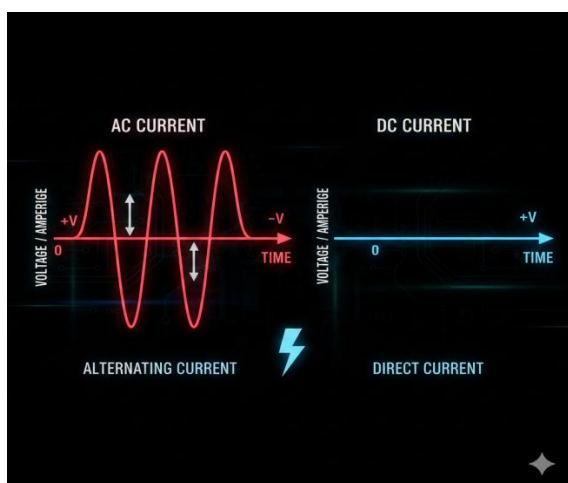**Why AC is King for the Grid:** The biggest advantage of AC is the ability to use **Transformers**. We can "step up" the voltage to very high levels (like 400,000V) to reduce energy loss during travel and then "step it down" safely for your home.



### 3. Real-World / Industry Applications (≈ 10 minutes)

In industry, the choice between AC and DC is tactical:

- **AC Power:** Used for the national grid, heavy industrial motors (Induction Motors), and household appliances like ACs and refrigerators.
  - **DC Power:** Crucial for Electronic circuits (your laptop), Electric Vehicle (EV) batteries, and specialized industrial processes like **Electroplating** or Aluminium smelting where a constant direction of current is required.
  - **Fun Fact:** Even though the grid is AC, high-tech "HVDC" (High Voltage Direct Current) lines are now used to connect different regional grids because they are more stable for extremely long distances.
- 

### 4. Summary & Q&A (≈ 5 minutes)

- **Key Takeaway:** DC is constant and storable; AC is periodic and easy to transform.
- **Quick Revision:** Which current has a frequency of 50Hz? (Answer: AC). Which current is used in a TV remote battery? (Answer: DC).
- **Student Doubt:** "If AC changes direction, why don't my lights flicker?"

**Answer:** It happens 50 times every second (50Hz)! Your eyes are not fast enough to see it, so the light appears constant.

---

### Mentorship Note

Mastering the differences between AC and DC is the "Universal Key" for your career. Whether you are designing a solar power plant (DC to AC conversion) or troubleshooting an industrial motor drive, this fundamental concept will be your most used tool. Stay curious—the future of "Green Energy" relies entirely on how well we manage these two currents!

### Lecture 2: Principle of Generation of Alternating Voltage

**Branch:** Electrical Engineering / Renewable Energy **Unit 1:** Fundamentals of Alternating Voltage and Current **Time:** 60 Minutes

---

#### 1.

Hook / Introduction (≈ 5 minutes)

Have you ever wondered how a massive, silent hydroelectric dam or a roaring thermal power plant actually "creates" electricity out of thin air? It isn't magic; it's a beautiful dance between magnetism and motion.

In 1831, Michael Faraday discovered that if you move a magnet near a wire, the wire "wakes up" with electrical energy. This simple observation is the reason we can light up entire cities today. Today, we will go behind the scenes of the power plant to understand the fundamental mechanics of how alternating voltage is born.


## 2.

Core Concepts ( $\approx$  40 minutes)
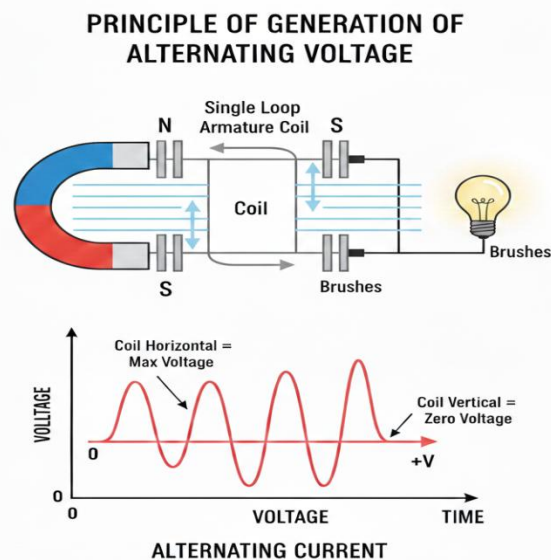
### The Foundation: Faraday's Law of Electromagnetic Induction

The heart of AC generation is Faraday's First Law: *"Whenever a conductor cuts magnetic flux, an electromotive force (EMF) is induced in it."*

- **The ingredients:** You need three things to generate voltage: a **Magnetic Field** (from magnets), a **Conductor** (copper wire), and **Relative Motion** between them.
- **The Analogy:** Imagine a sharp knife (the conductor) slicing through a loaf of bread (the magnetic flux lines). If the knife doesn't move, it doesn't slice. The faster and more effectively you "slice," the more "voltage" you produce.



### The Mechanism: A Simple Loop Generator

- Imagine a single rectangular loop of wire rotating in a uniform magnetic field between a North and South pole.
- **Position  $0^\circ$ :** The loop moves parallel to the magnetic lines. It "cuts" nothing.  
Induced EMF = **Zero**.
- **Position  $90^\circ$ :** The loop moves perpendicular to the lines, cutting them at a maximum rate.  
Induced EMF = **Maximum Positive**.
- **Position  $180^\circ$ :** Again, it moves parallel. Induced EMF = **Zero**.

- **Position 270°:** The loop cuts the lines again, but in the opposite direction.

Induced EMF = **Maximum Negative**.

- **Position 360°:** Back to the start.

Induced EMF = **Zero**.

### Why is it "Alternating"?

Because the loop is rotating, the direction in which it cuts the magnetic field reverses every half-cycle. This produces a **Sinusoidal Waveform**—a voltage that smoothly rises, falls, and changes polarity.

---

### 3.

Real-World / Industry Applications (≈ 10 minutes)

This isn't just theory; it is the backbone of the global power industry:

- **Power Plants:** Whether it's a nuclear, coal, or hydro plant, they all use this principle. They use steam or water to spin a massive **Alternator** (AC Generator) to produce the electricity you use right now.
  - **Renewable Energy:** Wind turbines use the wind to turn blades connected to a generator, applying this exact principle to create green energy.
  - **Automobiles:** Your car has a small alternator that generates AC (which is then converted to DC) to charge your battery while you drive.
- 

### 4.

Summary & Q&A (≈ 5 minutes)

- **Key Takeaways:** AC voltage is generated by the relative motion between a conductor and a magnetic field (Faraday's Law). The rotating motion naturally produces a sine wave.
- **Typical Student Doubt:** *"Does the magnet have to move, or the wire?"*

**Answer:** It doesn't matter! In small generators, the wire moves. In massive power plant alternators, we actually spin the magnets (the rotor) inside stationary coils (the stator) because it's more efficient for high voltages.

---

### Mentorship Note

Understanding the principle of generation is your first step into "Power Systems". If you master how EMF is induced, you will find it much easier to understand Transformers, Motors, and Generators in your upcoming semesters. This concept is a favourite in **Placement Interviews** for power companies—know your "slicing" and you'll shine.

### Lecture 3: Sinusoidal Function Terminology

Branch: Electrical Engineering / Renewable Energy

Unit 1: Fundamentals of Alternating Voltage and Current

Time: 60 Minutes

---

### 1. Hook / Introduction (≈ 5 minutes)


Ever noticed how music is visualized on a screen as a dancing line, or how a heart monitor in a hospital blip in a repeating pattern?<sup>3</sup>. In the world of Electrical Engineering, AC power has its own "heartbeat. We call it a **Sinusoidal Waveform**. Just as a doctor needs to understand heart rate and rhythm to treat a patient, an Electrical Engineer must master the "anatomy" of a sine wave to control power systems. Today, we are going to learn the language of AC—the specific terms that describe its rhythm, speed, and strength<sup>6</sup>.

---

### 2. Core Concepts (≈ 40 minutes)
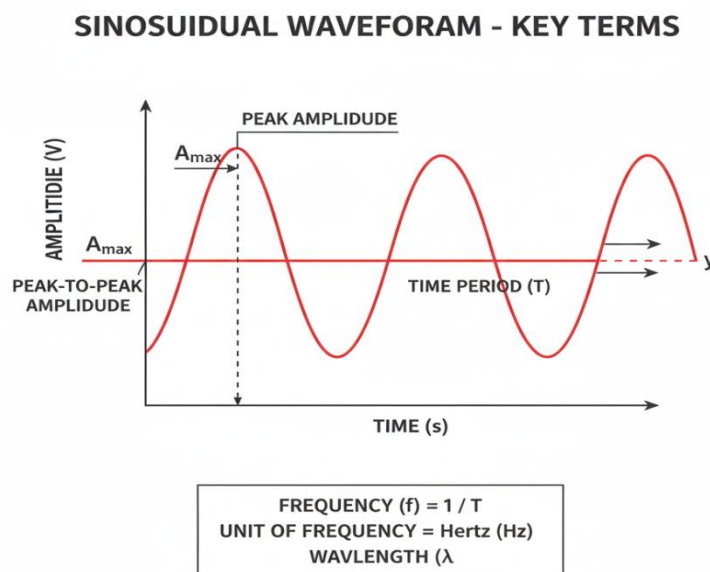
#### A. Defining the Anatomy of a Sine Wave

To talk like an engineer, we must use precise terms to describe what we see on an oscilloscope:



1. **Waveform:** The graph obtained by plotting the instantaneous values of an alternating quantity against time.
2. **Cycle:** One complete set of positive and negative values of an alternating quantity. It represents one full revolution of the generator's loop.
3. **Time Period (T):** The time taken, in seconds, to complete one full cycle.
4. **Frequency (f):** The number of cycles completed per second. In India, our power grid has a frequency of 50 Hz, meaning it completes 50 full cycles every single second!

5. **Amplitude (Peak Value):** The maximum value (either positive or negative) reached by an alternating quantity during one cycle.
6. **Angular Frequency ( $\omega$ ):** The rate of change of the angle in radians per second.

### B. Establishing the Relationships

These terms aren't just independent; they are mathematically linked:

- **Frequency and Time:** They are opposites.  $f = 1/T$ . If the time period is small, the frequency is high.
- **Angular Frequency:** Since one cycle is  $360^\circ$  (or  $2\pi$  radians), the relationship is  $\omega = 2\pi f$ .

### C. Forms of Sinusoidal Quantities

We can express an alternating voltage or current in different mathematical ways depending on what we need to calculate:

- **Standard Equation:**  $v = V_m \sin(\theta)$ .
- 

## 3. Real-World / Industry Applications ( $\approx$ 10 minutes)

In the industry, these terms are your daily tools:

- **Grid Stability:** Power engineers at load centres monitor **Frequency** constantly. If it drops below 48.5 Hz, the entire regional grid could collapse.
  - **Electronics Design:** When you use an oscilloscope (CRO) to troubleshoot a circuit, you are looking for the **Amplitude** to see if a component is getting too much voltage and the **Time Period** to check for timing errors.
  - **Fun Fact:** Your ears can hear frequencies from 20 Hz to 20,000 Hz. The 50 Hz hum you sometimes hear from a large transformer is actually the sound of the AC frequency vibrating the metal core.
- 

## 4. Summary & Q&A ( $\approx$ 5 minutes)

- **Key Takeaways:** A cycle is a full "round trip"; frequency is how many trips occur in a second; and amplitude is the "height" of the wave.
- **Quick Revision:** If a wave has a Time Period of 0.02 seconds, what is its frequency?  
(Answer:  $1/0.02 = 50$  Hz).
- **Typical Student Doubt:** "Why do we use  $2\pi$  in the formulas.

**Answer:** Because generators rotate in a circle, and a full circle is  $2\pi$  radians. We are just converting circular motion into a wave on a graph.

---

### **Mentorship Note:**

Mastering these terminologies is the "foundation stone" of your diploma. When you go for a **Placement Interview**, an examiner won't just ask "What is AC?" they will ask you to calculate the **Angular Frequency** of a system or explain a **Phase Shift**. Treat these terms like the alphabet of your profession; once you know the letters, you can start writing the complex "sentences" of power system analysis.

## **Lecture 4: Various Values of Sinusoidal Alternating Quantities**

**Branch:** Electrical Engineering / Renewable Energy

**Unit 1:** Fundamentals of Alternating Voltage and Current

**Time:** 60 Minutes

---

### **1.**

Hook / Introduction ( $\approx$  5 minutes) <sup>4</sup>

Imagine you are buying a 100-watt light bulb. If you look closely at the packaging, it says "230V AC." But wait—didn't we just learn in our previous lecture that AC is constantly changing? It goes from zero to a positive peak, back to zero, and then to a negative peak. If the voltage is always moving, what does "230V" actually mean? Is it the maximum? The average? Or something else entirely?

Today, we solve this mystery. As engineers, we can't just say the voltage is "changing"; we need specific "ruler measurements" to rate our equipment, bill our customers, and ensure our motors don't burn out. Today, we learn the different "faces" of AC voltage and current.

---

### **2.**

Core Concepts ( $\approx$  40 minutes)

#### **A.**

Defining the Critical Values

To accurately describe an AC wave, we use six primary terms:

1. **Instantaneous Value ( $v$  or  $i$ ):** The value of an alternating quantity at any specific instant of time. It is represented by small letters.
2. **Maximum Value ( $V_m$  or  $I_m$ ):** Also known as the peak value or amplitude, this is the highest value reached by the wave in either half-cycle.
3. **Average Value ( $V_{avg}$  or  $I_{avg}$ ):** The arithmetic mean of all instantaneous values over one half-cycle. For a full sine wave, the average over a full cycle is zero (since positive and negative halves cancel), so we calculate it for a half-cycle.
4. **RMS (Root Mean Square) Value ( $V$  or  $I$ ):** This is the "effective" value. It is the value of AC that produces the same amount of heat in a resistor as a corresponding DC value. It is what your multimeter actually measures  $0.707 \times$  Peak Value.

5. **Form Factor (K):** The ratio of the RMS value to the Average value. For a sine wave, this is always **1.11**.
6. **Peak Factor (K<sub>p</sub>):** The ratio of the Maximum value to the RMS value. For a sine wave, this is **1.414**.

## B.

### State Relations Among These Values

In your exams and practicals, you will often need to convert one value to another. For a purely sinusoidal wave:

1. RMS (Root Mean Square) Value of Voltage  
 $V_{rms} = V_m / \sqrt{2} = 0.707V_m$   
 Where  $V_m$  = Maximum (peak) value of voltage
2. Average Value of Voltage  
 (The average value of AC is taken over one half cycle)  
 $V_{avg} = 2V_m / \pi = 0.637 V_m$
3. Form Factor = RMS value / Average value =  $V_{rms} / V_{avg}$   
 For sinusoidal waveform: Form Factor =  $0.707V_m / 0.637V_m$   
 Form Factor = 1.11
4. Peak Factor (Crest Factor) = Maximum value / RMS value =  $V_m / V_{rms}$   
 For sinusoidal waveform: Peak Factor =  $V_m / 0.707V_m$   
 Peak Factor = 1.414

## 3.

### Real-World / Industry Applications ( $\approx$ 10 minutes)

- **Household Appliances:** When we say the Indian supply is 230V, that is the **RMS value**. The actual peak voltage hitting your appliances is roughly 325V (1.414 times 230). Insulation in wires must be designed to withstand this peak, not just the RMS.
- **Metering:** Standard analog and digital voltmeters in your lab are calibrated to display the **RMS value** because that represents the actual "work" or "heating" capability of the electricity. <sup>24242424</sup>
- **Form Factor Importance:** Transformers and generators are designed based on the **Form Factor**. If the wave shape distorts (becoming non-sinusoidal), the form factor changes, which can lead to overheating in industrial equipment.

## 4.

### Summary & Q&A ( $\approx$ 5 minutes)

- **Key Takeaways:** Peak is the "limit," Average is the "mean," and RMS is the "work-horse" value.
- **Quick Revision:** If a wave's peak is 100V, what is its RMS? (Answer: 70.7V). What is the Form Factor of a sine wave?  
 (Answer: 1.11).

- **Typical Student Doubt:** "Why don't we just use the peak value for everything?"

**Answer:** Because the wave is only at the peak for a tiny fraction of time. Using the peak value to calculate power would give us a false sense of how much work the electricity is doing. The RMS value gives us the "real" equivalent to DC.

---

### **Mentorship Note**

Understanding these values is the difference between a technician and an **Electrical Engineer**. When you go for a **viva-voce** or a **job interview** at a power utility like GETCO or a private firm, they will test your ability to distinguish between these values. <sup>31313131</sup>Mastering these calculations now will make your future work with motors, transformers, and power systems much more intuitive. <sup>32</sup>Keep practicing the numerical—they are the "math of power"!

## **Lecture 5: Phase Difference - Lagging and Leading Quantities**

Branch: Electrical Engineering / Renewable Energy

Unit 1: Fundamentals of Alternating Voltage and Current 2

Time: 60 Minutes

---

### **1. Hook / Introduction (≈ 5 minutes)**

Imagine two world-class sprinters at the starting line of a 100-meter dash. If they both start at the exact same millisecond, they are "in-sync." But what if one athlete starts a fraction of a second later? Even if they run at the same speed, there is a "gap" between them throughout the race.

In Electrical Engineering, AC voltages and currents are like those runners. They are constantly moving waves, and they don't always start or reach their peaks at the same time. This "gap" or time-shift is what we call **Phase Difference**. Understanding this isn't just a math exercise—it's the secret to understanding why some electrical motors run efficiently while others overheat. Today, we learn how to measure the "timing" of electricity.

---

### **2. Core Concepts (≈ 40 minutes)**

#### **What is Phase?**

Phase represents the fraction of a cycle that has elapsed relative to a reference point<sup>3</sup>. When we compare two sinusoidal waves of the same frequency, we look at their relative positions in time.

#### **Phase Difference ( $\phi$ )**

When two alternating quantities of the same frequency do not pass through their zero values at the same instant, they are said to have a phase difference.

- **In-Phase:** Two waves are in-phase if they reach their maximum and zero values at the exact same instant.
- **Out-of-Phase:** If there is a time or angle gap between their peaks, they are out-of-phase.

## Leading vs. Lagging Quantities

This is the most critical concept for an Electrical Technocrat to master:

1. **Leading Quantity:** An alternating quantity that reaches its maximum or zero value *earlier* than another quantity.

$$\text{Equation: } V = V_m \sin(\omega t + \phi)$$

2. **Lagging Quantity:** An alternating quantity that reaches its maximum or zero value *later* than another quantity.

$$\text{Equation: } V = V_m \sin(\omega t - \phi)$$

## The Analogy of the Two Clocks

Think of two clocks. Clock A shows the correct time. Clock B is 10 minutes slow. Clock B is "lagging" behind Clock A. In electrical circuits, purely inductive loads (like motor coils) cause the current to "lag" behind the voltage, while capacitive loads (like capacitors) cause the current to "lead" the voltage.

---

## 3. Real-World / Industry Applications (≈ 10 minutes)

Why does this matter in a factory or a power plant?

- **Power Factor:** Phase difference is the root of "Power Factor." If the phase difference between voltage and current is too large (high lag), the system becomes inefficient. Industries pay heavy penalties to electricity boards if their current lags too much!
- **Motor Operation:** Induction motors, the workhorses of the industry, naturally cause current to lag. Engineers use "Capacitor Banks" to create a "leading" effect to cancel out the lag and keep the system balanced.
- **Synchronization:** Before connecting a massive generator to the national grid, engineers must ensure its phase matches the grid exactly. If the phases are off, it can cause an explosion or massive equipment failure!

---

## 4. Summary & Q&A (≈ 5 minutes)

- Key Takeaways: Phase difference is the angular "gap" between two waves. "Leading" means ahead (+), and "Lagging" means behind (-). Quick Revision: If Current  $I = I_m \sin(\omega t - 30^\circ)$ , is it leading or lagging the voltage
- $V = V_m \sin(\omega t)$ ? (Answer: Lagging by  $30^\circ$ ).
- Typical Student Doubt: "Can frequency be different when measuring phase difference?"

**Answer:** No! We only compare phase difference between waves of the *same* frequency. If the frequencies are different, the "gap" between them would change constantly, making the comparison meaningless.

## Mentorship Note

In your career as an Electrical Engineer, you will spend a lot of time fighting "Lagging Current." Mastering this topic now is your first step toward becoming a **Power Quality Expert**. When you look at an industrial electricity bill, you won't just see numbers; you'll see the "Phase" relationship of an entire factory. Learn to visualize these waves in your head, and you'll find that complex AC circuit analysis becomes as simple as telling time!

## Lecture 6: Vector representation of alternating quantity

### 1. Most Repeated / High-Probability Questions

*These questions form the foundation of the theory exam and carry significant weightage (typically 4–8 marks each).*

#### A. Core Definitions & Concepts

Define the following terms related to A.C. Series circuits:

Inductive Reactance ( $X_L$ ) and Capacitive Reactance ( $X_C$ ).

Impedance ( $Z$ ) and Admittance ( $Y$ ).

Power Factor ( $\cos\phi$ ) and its significance.

1. Explain the concept of "Phasor" and why it is used to represent A.C. quantities instead of simple scalar addition.

#### B. Derivations and Circuit Analysis

3. Purely Resistive, Inductive, and Capacitive Circuits:

Derive the expression for current and power in a purely inductive circuit. Show that current lags the voltage by  $90^\circ$ .

Draw the voltage and current waveforms for a purely capacitive circuit.

4. Series R-L and R-C Circuits:

Derive the expression for total Impedance ( $Z$ ) for an R-L series circuit.

Draw the Impedance Triangle and Voltage Triangle for an R-C series circuit.

5. Series R-L-C Circuit:

Explain the behaviour of an R-L-C series circuit when:

1.  $X_L > X_C$  (Inductive nature)
2.  $X_C > X_L$  (Capacitive nature)
3.  $X_L = X_C$  (Resonance)

#### C. Resonance and Power

6. Series Resonance:


Define Resonance in a series R-L-C circuit.

Derive the formula for Resonant Frequency ( $f_r$ ).

List the characteristics of a series resonant circuit (Impedance, Current, Power Factor).
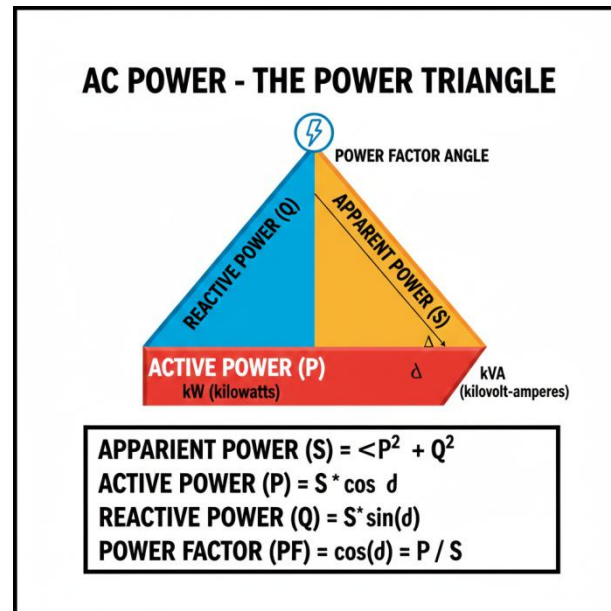
### 7. The Power Triangle:

Explain Active Power (P), Reactive Power (Q), and Apparent Power (S).



## 2. Application & Logical Thinking Questions

*These questions test your ability to apply theory to real-world scenarios. Mastering these will help you move from a "Pass" to an "A+" grade.*

### Q1. The Choke Coil Mystery:

A choke coil (R-L circuit) is connected across a D.C. supply and then across an A.C. supply of the same voltage. In which case will the current be higher? Justify your answer using the concept of Reactance.

### Q2. Power Factor Correction Logic:

Most industrial loads are inductive (motors). Why do engineers connect a capacitor in series/parallel to improve the power factor? What happens to the total current drawn from the source when the power factor is improved?

### Q3. The Resonance Safety Concern:

In a series R-L-C circuit at resonance, the voltage across the inductor (L) or capacitor (C) can be much higher than the supply voltage. Explain this "Voltage Magnification" and why it can be dangerous for insulation in electrical equipment.

### Q4. Component Identification:

You are given a "Black Box" with two terminals. When connected to an A.C. source, the current is found to lead the voltage by  $45^\circ$ . What are the likely components inside the box? Draw the phasor diagram to support your conclusion.

#### Q5. Tuning Circuit Application:

How is the principle of Series Resonance used in a traditional Radio Receiver to select a particular station frequency? Explain the role of the variable capacitor.

---

#### Quick Revision Checklist

Can I draw the phasor diagram for R-L, R-C, and R-L-C circuits?

Do I know the difference between kVA, kW, and kVAR?

Can I calculate  $Z = \sqrt{R^2 + (X_L - X_C)^2}$  accurately?

Do I understand why  $\cos \phi = R / Z$ ?

### Lecture 7: Addition of Alternating Quantities – Graphical and Analytical Methods

Branch: Electrical Engineering / Renewable Energy

Unit 1: Fundamentals of Alternating Voltage and Current

Time: 60 Minutes

---

#### 1. Hook / Introduction ( $\approx$ 5 minutes)

Imagine you are part of a rescue team pulling a stuck vehicle out of the mud. If two people pull in the exact same direction, their forces add up perfectly. But what if they pull at different angles? The total force isn't just a simple sum anymore; it depends on the direction.

In AC circuits, we deal with multiple voltages and currents simultaneously. However, because they have different "phases" (they reach their peaks at different times), we cannot simply add them like  $2 + 2 = 4$ . If you have two 10V sources that are out of phase, the result might be 15V, 5V, or even zero! Today, we will master the techniques to combine these "electrical forces" accurately using Vectors.

---

#### 2. Core Concepts ( $\approx$ 40 minutes)

##### The Challenge: Why can't we use Simple Arithmetic?

In DC,  $10A + 5A$  is always  $15A$ . In AC, alternating quantities are "Vector" quantities. They have both **Magnitude** (RMS value) and **Direction** (Phase angle). To find their sum (the Resultant), we use two primary methods.

##### Method A: Graphical Method (Parallelogram Law)

This is the visual way to "see" how waves combine.

1. **Represent:** Draw two vectors,  $V_1$  and  $V_2$ , from a common origin. The length represents the magnitude, and the angle from the horizontal represents the phase.

2. **Construct:** Draw lines parallel to each vector to form a parallelogram.
3. **Resultant:** The diagonal of this parallelogram starting from the origin represents the Resultant Vector (VR).
4. **Measurement:** Measure the length of the diagonal and the angle it makes with the reference axis to get the total voltage and the new phase.

### Method B: Analytical Method (Trigonometry)

This is the precise "Engineer's Way" using the **Cosine Rule**. If we have two quantities E1 and E2 with a phase difference  $\phi$  between them:

#### Resultant Magnitude (ER):

$$ER = \sqrt{E1^2 + E2^2 + 2E1E2 \cos \phi}$$

#### Resultant Phase( $\alpha$ ):

$$\tan \alpha = (E2 \sin \phi) / (E1 + E2 \cos \phi)$$

**The Component Method:** Another highly effective analytical approach is breaking each vector into Horizontal component:  $X = E \cos \theta$  components and Vertical component:  $Y = E \sin \theta$

You sum all X-components and all Y-components, then find the final resultant using Pythagoras' theorem: Resultant Magnitude:  $ER = \sqrt{(\Sigma X)^2 + (\Sigma Y)^2}$

---

### 3. Real-World / Industry Applications ( $\approx$ 10 minutes)

- **Three-Phase Systems:** This is how we calculate the "Neutral" current. In a balanced 3-phase system, adding the three current vectors results in zero—this is why a balanced neutral carries no current!
  - **Substation Load Management:** When two different feeders (power lines) are connected to the same busbar, engineers must use vector addition to ensure the total load doesn't exceed the transformer's capacity.
  - **Fun Fact:** If you accidentally connect two AC generators that are 180° out of phase, the "addition" results in a massive short circuit because the voltages oppose each other completely. This is why "Synchronization" is the most stressful part of a power plant operator's job!
- 

### 4. Summary & Q&A ( $\approx$ 5 minutes)

- **Key Takeaways:** AC quantities are added as vectors. The Graphical method is good for visualization; the Analytical method is required for precision.
- **Quick Revision:** If two 10 V waves are in phase ( $0^\circ$ ),

what is the sum?

Answer: 20 V

If they are 180° out of phase,

what is the sum?

Answer: 0 V

- **Typical Student Doubt:** "Do I use Peak or RMS values for vector addition?"

**Answer:** Always use **RMS values** for vector addition in power circuits, as meters and equipment ratings are based on RMS.

---

### Mentorship Note

Mastering vector addition is the "Divide and Conquer" strategy of Electrical Engineering. This isn't just a Unit 1 topic—it is the tool you will use in **AC Machines, Power Systems, and Protection Engineering**. If you can resolve vectors into components today, you will be the student who solves complex 3-phase problems in 5 minutes while others are still scratching their heads. Practice the "Component Method"—it is the industry favourite for its accuracy and speed!

## Lecture 8: Vector Transformations – Rectangular to Polar and Vice-Versa

Branch: Electrical Engineering / Renewable Energy

Unit 1: Fundamentals of Alternating Voltage and Current

Time: 60 Minutes

---

### 1. Hook / Introduction (≈ 5 minutes)

Have you ever tried to describe a location to a friend? You could say, "Go 3 blocks East and 4 blocks North" (that's a grid system), or you could say, "Walk 5 blocks at an angle of 53 degrees" (that's a direct line). Both get you to the exact same spot, but one might be easier to follow depending on whether you are walking through buildings or flying a drone.

In Electrical Engineering, AC quantities are like that location. Sometimes it is easier to look at them as "Horizontal and Vertical parts" (**Rectangular form**), and sometimes it is easier to see them as "Strength and Direction" (**Polar form**). Today, we learn how to switch between these two "languages" fluently. This is the "Secret Translator" skill that separates a great engineer from a struggling student!

---

### 2. Core Concepts (≈ 40 minutes)

#### A. The Two Languages of Vectors

Every AC quantity (Voltage or Current) can be represented on a complex plane (X-axis for real/horizontal, Y-axis for imaginary/vertical).

1. **Rectangular Form ( $A = a + jb$ ):** Here, 'a' is the horizontal component (Real) and 'b' is the vertical component (Imaginary, indicated by 'j').

*Analogy:* The "GPS coordinates" of a point.

2. **Polar Form ( $A = Z \angle \theta$ ):** Here, 'Z' is the magnitude (length of the vector) and 'θ' is the phase angle.

*Analogy:* The "Speed and Heading" of a ship.

#### B. Transferring from Rectangular to Polar ( $a + jb \rightarrow Z \angle \theta$ )

When we want to know the total magnitude and the phase angle:

Step 1: Find Magnitude (Z)

Use Pythagoras' theorem:

$$Z = \sqrt{a^2 + b^2}$$

Step 2: Find Angle (θ)

Use trigonometry:  $\theta = \tan^{-1}(b/a)$

Example:  $3 + j4$

$$\text{Magnitude: } Z = \sqrt{3^2 + 4^2} = 5$$

$$\text{Angle: } \theta = \tan^{-1}(4/3) = 53.13^\circ$$

Therefore,  $3 + j4 = 5 \angle 53.13^\circ$

#### C. Transferring from Polar to Rectangular ( $Z \angle \theta \rightarrow a + jb$ )

When we need to add or subtract vectors (which is easier in rectangular form):

Step 1: Find Real part

$$(a) a = Z \cos \theta$$

Step 2: Find Imaginary part

(b)

$$b = Z \sin \theta$$

Example:

$$10 \angle 30^\circ$$

$$\text{Real part: } 10 \cos 30^\circ = 8.66$$

$$\text{Imaginary part: } 10 \sin 30^\circ = 5$$

Therefore,

$$10 \angle 30^\circ = 8.66 + j5$$

---

### 3. Real-World / Industry Applications (≈ 10 minutes)

- **Calculator Skills:** In the industry, you won't always do this by hand. Modern scientific calculators have "Pol" and "Rec" buttons. Mastery of this transformation allows you to calculate the **Impedance** of a motor in seconds.
- **Power System Analysis:** When calculating voltage drops in long transmission lines, engineers use rectangular form to handle the resistance and reactance separately, then switch to Polar form to report the final voltage and phase angle to the control center.
- **Fun Fact:** The letter 'j' is used by electrical engineers instead of 'i' (used in pure math) because 'I' is already reserved for "Current".

---

### 4. Summary & Q&A (≈ 5 minutes)

- **Key Takeaways:** Use **Rectangular** for addition/subtraction.

Use **Polar** for multiplication/division and for final answers.

- **Quick Revision:**

If a vector is  $5 + j0$ , what is its angle?

Answer:  $0^\circ$

If a vector is  $10 \angle 90^\circ$ , what is its real part?

Answer: 0

**Typical Student Doubt:** "Why do we use the 'j' operator?"

**Answer:** It tells us the value is 90 degrees out of phase. It helps us keep the horizontal "Resistance" and vertical "Reactance" separate in our math so they don't get mixed up!

---

### **Mentorship Note**

Here is a career secret: The students who master **Scientific Calculator** shortcuts for Rectangular-to-Polar conversions are the ones who finish their exams 30 minutes early. But more importantly, in a professional setting, being able to mentally estimate these conversions helps you "feel" the circuit. If you see a large '\$j\$' component, you immediately know you are dealing with a highly inductive or capacitive system. Practice this until it becomes second nature—it is the most used mathematical tool in an electrical engineer's belt!

## **Lecture 9: Mathematical Operations of Vectors**

Branch: Electrical Engineering / Renewable Energy

Unit 1: Fundamentals of Alternating Voltage and Current

Time: 60 Minutes

---

### **1. Hook / Introduction (≈ 5 minutes)**

Imagine you are a Chef preparing a complex dish. Some ingredients need to be chopped and mixed (Addition), while others need to be blended to change their texture entirely (Multiplication). If you try to blend a whole carrot without chopping it, or try to chop a liquid, you'll end up with a mess!

In our previous lecture, we learned that AC quantities have two "forms": **Rectangular** and **Polar**. Today's secret to becoming an expert Electrical Technocrat is knowing which "kitchen tool" to use for which mathematical operation. Why struggle with complex trigonometry for addition when a simple rectangular sum will do? Today, we master the "Shortcuts of the Pros" to perform vector math with speed and precision.

---

### **2. Core Concepts (≈ 40 minutes)**

#### **The Golden Rule of Vector Math**

Before we pick up our pens, memorize this rule:

- **Addition and Subtraction** are easiest in **Rectangular Form ( $a + jb$ )**.
- **Multiplication and Division** are easiest in **Polar Form  $Z \angle \theta$**

### A. Addition and Subtraction (Rectangular Style)

When we add two voltages or currents, we simply combine the "Real" parts and the "Imaginary" parts separately.

- **Addition:**  $(A + jB) + (C + jD) = (A+C) + j(B+D)$
- **Subtraction:**  $(A + jB) - (C + jD) = (A-C) + j(B-D)$
- *Analogy:* It's like sorting coins. You put all the 5-rupee coins in one pile and all the 10-rupee coins in another. You don't mix them until the very end.

### B. Multiplication (Polar Style)

Multiplying in rectangular form involves a lot of messy FOIL math and  $j^2 = -1$  complications. In Polar, it's a breeze:

1. Multiply the Magnitudes.
2. Add the Angles.

Formula:

$$(Z_1 \angle \theta_1) \times (Z_2 \angle \theta_2) = (Z_1 \times Z_2) \angle (\theta_1 + \theta_2)$$

---

### Division (Polar Style)

1. Divide the Magnitudes.
2. Subtract the Angles (Numerator angle minus Denominator angle).

Formula:

$$(Z_1 \angle \theta_1) \div (Z_2 \angle \theta_2) = (Z_1 / Z_2) \angle (\theta_1 - \theta_2)$$

---

### D. The Conjugate Concept

Sometimes we need to find the "Mirror Image" of a vector, especially when calculating complex power. To find the conjugate of  $(a + jb)$ , we just flip the sign of the  $j$  part:  $(a - jb)$ . In polar,  $(Z \angle \theta)$  becomes  $(Z \angle -\theta)$

---

### 3. Real-World / Industry Applications ( $\approx$ 10 minutes)

- Ohm's Law in AC:  $V = I \times Z$ . In a factory, the Current ( $I$ ) and Impedance ( $Z$ ) are always vectors. We use the Multiplication Rule (Polar) to quickly find the required Voltage.
  - Power Calculations: To find Complex Power ( $S = V \times I$ ), we use the conjugate of the current. This calculation tells an engineer how much "Useful Power" (Watts) vs "Wasted Power" (VARs) a motor is drawing.
  - Fun Fact: Computers in modern "Smart Grids" perform millions of these polar-to-rectangular conversions every second to balance the electricity supply across the city!
- 

### 4. Summary & Q&A ( $\approx$ 5 minutes)

- Key Takeaways: Rectangular for  $+/-$ , Polar for  $\times / \div$ .
- Quick Revision: If I multiply  $10 \angle 30^\circ$  by  $2 \angle 20^\circ$ , what is the result?

Answer:  $20 \angle 50^\circ$

- Typical Student Doubt: "What if my problem gives me addition in Polar form?"  
Answer: You must convert it to Rectangular first! There is no direct way to add polar angles accurately without conversion.

---

### Mentorship Note

In your future semesters—especially in **Circuit Theory** and **AC Machines**—you will face "Giant" equations. Students who try to do everything in one form get lost in the math. The "Smart Engineer" is a hybrid: they switch forms constantly to keep the math simple. Mastering this skill now will reduce your exam stress by 50% and make you look like a wizard during lab calculations. Practice these operations on your calculator until your fingers move automatically!

## Lecture 10: Numerical Mastery – Fundamentals of Alternating Quantities

**Branch:** Electrical Engineering / Renewable Energy

**Unit 1:** Fundamentals of Alternating Voltage and Current

**Time:** 60 Minutes

---

### 1. Hook / Introduction (≈ 5 minutes)

Imagine you are a structural engineer. You've studied the properties of steel and concrete, but now you're asked: "Will this bridge hold 50 tons?" To answer, you need more than definitions; you need **math**.

In Electrical Engineering, knowing the definition of RMS or Frequency is the "theory," but solving a numerical is the "engineering." Today, we bridge the gap between "knowing" and "doing." We are going to transform from students into calculators. By the end of this hour, when you see a complex AC equation, you won't see a jumble of letters—you'll see the exact behaviour of a power system.

---

### 2. Core Concepts (≈ 40 minutes)

The Engineering Toolkit: Key Formulas

Before we solve, let's keep our "tools" ready:

1. The Standard Equation:  $v = V_m \sin(\omega t \pm \phi)$
  2. Frequency / Time:  $f = 1 / T$  and  $\omega = 2\pi f$
  3. Values:  $V_{RMS} = 0.707 V_m$  and  $V_{avg} = 0.637 V_m$
- 

Problem Type 1: Waveform Analysis

Problem: An alternating current is given by  $i = 141.4 \sin(314t)$ . Find the (i) Maximum Value, (ii) Frequency, and (iii) RMS Value.

Step 1: Compare the given equation with  $i = I_m \sin(\omega t)$ .

Step 2 (Max Value):  $I_m = 141.4 \text{ A}$

Step 3 (Frequency):  $\omega = 314$

Since  $\omega = 2\pi f$ , then  $f = 314 / (2 \times 3.14) = 50$  Hz  
Step 4 (RMS Value):  $I_{RMS} = 141.4 \times 0.707 = 100$  A

---

Problem Type 2: Phase Difference

Problem: Two voltages are  $v_1 = 100 \sin(\omega t)$  and  $v_2 = 100 \sin(\omega t - 45^\circ)$ . What is the phase relationship?

Solution:  $v_2$  has a  $-45^\circ$  shift. This means  $v_2$  lags  $v_1$  by  $45^\circ$ .

In a vector diagram,  $v_1$  would be on the X-axis, and  $v_2$  would be  $45^\circ$  below it.

---

Problem Type 3: Vector Math

Problem: Add  $V_1 = 10 + j10$  and  $V_2 = 10 \angle 30^\circ$ .

Step 1: Convert  $V_2$  to Rectangular form:

$$V_2 = 10 \cos 30^\circ + j 10 \sin 30^\circ = 8.66 + j 5$$

Step 2: Add Real and Imaginary parts:

$$V_{total} = (10 + 8.66) + j (10 + 5) = 18.66 + j 15$$

Step 3: Convert back to Polar for the final answer:

$$V_{total} = \sqrt{(18.66^2 + 15^2)} \angle \tan^{-1}(15 / 18.66) \approx 23.94 \angle 38.8^\circ \text{ V}$$

---

### 3. Real-World / Industry Applications ( $\approx 10$ minutes)

- **Nameplate Reading:** Every motor has a nameplate. If it says "415V," you now know that is the **RMS** value. If you are designing the insulation, you must calculate the **Peak** ( $415 \times 1.414 \approx 587 \text{ V}$ ) to prevent a flashover.
  - **UPS and Inverters:** Home inverters convert DC to AC. To ensure your ceiling fan runs at the right speed, the inverter's internal program must solve these frequency and voltage equations  $v = V_m \sin(\omega t)$  thousands of times per second.
  - **Fun Fact:** In early telegraph systems, they didn't have calculators. Engineers used large physical "Vector Addition Boards" with strings and weights to solve these problems!
- 

### 4. Summary & Q&A ( $\approx 5$ minutes)

- **Key Takeaways:** Always identify  $V_m$  and  $\omega$  first. Use Rectangular for addition and Polar for final representation.
- **Quick Revision:** If  $\omega = 628$ , what is  $f$ ?  
Answer: 100 Hz
- If  $V_{RMS} = 100$ , what is  $V_m$ ?  
Answer: 141.4 V
- **Typical Student Doubt:** "Why did my calculator give me the wrong angle?"

**Answer:** Check your calculator mode! It must be in **DEGREES (D)** for phase angles, not **RADIANS (R)**, unless the problem specifically asks for it.

---

### **Mentorship Note**

Here is a secret from the industry: **Calculators don't make mistakes; engineers do.** Mastery of numerical isn't just about getting the right answer; it's about developing "numerical intuition." When you look at an answer, ask yourself: "Does this make sense?" If you find an RMS value higher than the Maximum value, you know something is wrong. Developing this "internal alarm" will make you a highly reliable engineer in the field, where a small calculation error can lead to a big equipment failure. Keep practicing—math is the only language electricity truly understands!

### **A. Low-Level Prompts (10 Prompts – Remember & Understand)**

*Focus: Definitions, basic terminology, and simple concepts.*

1. "Explain the basic concept of [Topic Name] in simple terms as if you are teaching a first-year Diploma student."
  2. "Define the term [Term Name, e.g., RMS Value] and provide its standard mathematical formula and unit of measurement."
  3. "Give me a list of the 5 most important definitions from [Topic Name] that are frequently asked in Diploma exams."
  4. "Create a 5-point summary of the main characteristics of [Topic Name] for quick revision."
  5. "Explain the difference between [Term A] and [Term B] using a simple daily-life analogy."
  6. "Provide a clear, step-by-step description of how [Process/Principle Name] works."
  7. "List the key formulas required to solve numerical problems in [Topic Name] and explain what each symbol represents."
  8. "I am confused about [Concept Name]. Can you explain it again using a different perspective or a simpler example?"
  9. "Create a set of 5 multiple-choice questions (MCQs) with answers to test my basic understanding of [Topic Name]."
  10. "What are the standard symbols and notations used in [Topic Name] that I should use in my exam papers?"
- 

### **B. Moderate-Level Prompts (10 Prompts – Apply & Analyse)**

*Focus: Application, comparisons, and problem-solving logic.*

11. "Compare [System A] and [System B] in a tabular format based on efficiency, cost, and practical applications."
12. "Give me 3 real-world industrial examples where [Concept Name] is used and explain why it is important there."

13. "Provide a step-by-step solved numerical problem for [Problem Type, e.g., Vector Addition] showing every mathematical transition clearly."
  14. "If I increase the [Parameter Name, e.g., Frequency], how will it affect the [Resultant Parameter, e.g., Time Period]? Explain the logic."
  15. "Create a checklist of common mistakes students make when solving problems related to [Topic Name] and how to avoid them."
  16. "Explain the significance of [Factor Name, e.g., Peak Factor] in determining the safety or rating of engineering equipment."
  17. "Analyse why [Concept/Method] is preferred over [Alternative Method] in modern engineering practices."
  18. "Generate 3 mid-level practice problems on [Topic Name] and provide the final answers so I can check my work."
  19. "Describe a laboratory experiment that demonstrates [Principle Name] and explain what the expected observations should be."
  20. "How does [Concept Name] relate to the previous unit on [Previous Unit Name]? Help me connect these two ideas."
- 

### **C. High-Level Prompts (5 Prompts – Design & Create)**

*Focus: Logical reasoning, system-level thinking, and exam distinction.*

21. "Act as an examiner. Give me a challenging 'out-of-the-box' problem that combines [Topic A] and [Topic B], then explain the logic to solve it."
  22. "Create a logical flowchart or mental map that connects all the sub-topics within [Unit Title] to show how they depend on each other."
  23. "I have to design a small system that uses [Concept Name]. What are the key technical constraints and safety factors I must consider?"
  24. "Explain the long-term career importance of mastering [Unit Title]. Which specific engineering roles or industries require deep expertise in this?"
  25. "Critique the following statement: '[Incorrect or Partial Engineering Statement]'. Explain why it is technically incomplete and provide the correct professional version."
- 

#### **How to use this Toolkit:**

- **Step 1:** Choose a prompt based on your current level of understanding.
- **Step 2:** Replace the bracketed text [ ] with specific terms from your Unit 1 syllabus (e.g., replace [Topic Name] with Sinusoidal Waveform).
- **Step 3:** Review the AI's response and ask follow-up questions if you need more clarity.

**Mentorship Tip:** Don't just ask the AI for answers; ask it to *explain the steps*. In the engineering industry, your value is not in knowing the "result," but in understanding the "process" that led to it!

### Part 1: Key Definitions / Glossary (Top 15 Terms)

1. **Alternating Quantity:** A quantity whose magnitude changes continuously and direction reverses periodically with time.
2. **Waveform:** The shape of the curve obtained by plotting the instantaneous values of an alternating quantity against time.
3. **Cycle:** One complete set of positive and negative values of an alternating quantity.
4. **Time Period (T):** The time taken in seconds by an alternating quantity to complete one full cycle.
5. **Frequency (f):** The number of cycles completed per second by an alternating quantity (Measured in Hertz).
6. **Amplitude:** The maximum or peak value attained by an alternating quantity during one cycle.
7. **Instantaneous Value:** The value of an alternating quantity at any specific instant of time.
8. **RMS (Root Mean Square) Value:** The "effective" value of AC that produces the same heating effect as a corresponding DC value.
9. **Average Value:** The arithmetic mean of all instantaneous values taken over one half-cycle.
10. **Form Factor:** The ratio of the RMS value to the average value (1.11 for a sine wave).
11. **Peak Factor:** The ratio of the maximum value to the RMS value (1.414 for a sine wave).
12. **Phasor:** A rotating vector used to represent a sinusoidally varying alternating quantity.
13. **Phase Difference:** The angular displacement between two alternating quantities having the same frequency.
14. **Lagging Quantity:** An AC quantity that reaches its maximum or zero value later than the reference quantity.
15. **Leading Quantity:** An AC quantity that reaches its maximum or zero value earlier than the reference quantity.

---

### Part 2: FAQ & Assessment Section

#### A. Multiple Choice Questions (MCQs)

[1] What is the frequency of DC supply?

(a) 50 Hz (b) 60 Hz (c) 0 Hz (d) 100 Hz

[2] For a sine wave with peak voltage  $V_m$ , the RMS value is:

(a)  $0.637 V_m$

(b)  $0.707 V_m$

- (c)  $1.414 V_m$
- (d)  $V_m / \pi$

[3] In India, the standard domestic AC frequency is:

- (a) 60 Hz (b) 50 Hz (c) 230 Hz (d) 110 Hz

[4] A cycle consists of:

- (a) One positive half-cycle
- (b) One negative half-cycle
- (c) Two positive half-cycles
- (d) One positive and one negative half-cycle

[5] The relation between  $\omega$  (angular frequency) and  $f$  (frequency) is:

- (a)  $\omega = 2\pi f$
- (b)  $\omega = \pi f$
- (c)  $f = 2\pi \omega$
- (d)  $\omega = f / 2\pi$

[6] Which value of AC is measured by a standard Multimeter?

- (a) Peak value (b) Average value (c) RMS value (d) Instantaneous value

[7] The form factor for a purely sinusoidal wave is:

- (a) 1.414 (b) 0.707 (c) 1.11 (d) 0.637

[8] If the time period of a wave is 0.02 seconds, the frequency is:

- (a) 25 Hz (b) 50 Hz (c) 100 Hz (d) 20 Hz

[9] Two waves are "in-phase" if their phase difference is:

- (a)  $90^\circ$  (b)  $180^\circ$  (c)  $0^\circ$  (d)  $270^\circ$

[10] The peak factor of a sine wave is:

- (a) 1.11 (b) 1.414 (c) 1.21 (d) 0.707

[11] An alternating quantity is represented as  $v = 200 \sin(314t)$ . The peak voltage is:

- (a) 100V (b) 200V (c) 314V (d) 141.4V

[12] Addition of two AC voltages is done using:

- (a) Arithmetic sum (b) Algebraic sum (c) Vector sum (d) Geometric mean

[13] To multiply two vectors, which form is most convenient?

- (a) Rectangular (b) Polar (c) Triangular (d) Linear

[14] The average value of a full sine wave over one complete cycle is:

- (a)  $0.637 V_m$  (b)  $V_m$  (c) Zero (d)  $2 V_m$

[15] Which current is easier to step up or step down using a transformer?

(a) DC (b) Pulsating DC (c) AC (d) Pure DC

[16] The RMS value of AC is also known as:

(a) Maximum value (b) Effective value (c) Average value (d) Mean value

---

### B. Short Answer / Viva Questions

1. Why is AC preferred over DC for long-distance transmission?
  2. Define "RMS value" and explain its physical significance in terms of heating.
  3. Why is the average value of a sine wave calculated over a half-cycle instead of a full cycle?
  4. What is the significance of "Form Factor" in electrical machine design?
  5. Explain the difference between a "Leading" and a "Lagging" alternating quantity.
  6. Draw the phasor representation of two voltages where  $V_2$  lags  $V_1$  by  $90^\circ$
  7. State the mathematical relationship between Peak Value and RMS Value for a sine wave.
  8. Why do we use the  $j$ -operator in AC circuit analysis?
  9. Convert the vector  $3 + j4$  into Polar form.
  10. What happens to the time period of an AC signal if the frequency is doubled?
- 

### Answer Key for MCQs

1(c), 2(b), 3(b), 4(d), 5(a), 6(c), 7(c), 8(b), 9(c), 10(b), 11(b), 12(c), 13(c), 14(b), 15(b), 16(c), 17(c), 18(c), 19(c), 20(b).

---

### Mentorship Note

When preparing for exams, remember that **Unit 1** carries nearly **30% weightage**. Focus heavily on the definitions and the conversion between Polar and Rectangular forms. In your practical Vivas, examiners love to ask about the **heating effect of RMS values**—master that concept, and you will stand out as a top-tier student. Good luck with your revision!

### 1. AI Tools & Digital Learning Tools

These tools are selected to help you move from theoretical formulas to practical, visual understanding:

- **Falstad Circuit Simulator (Applet):**

**Purpose:** A powerful, web-based interactive circuit simulator.

**How it helps:** You can visualize AC current flow in real-time. It allows you to see the "movement" of electrons as sine waves and observe how phase differences occur when adding components.

- **Phet Interactive Simulations (University of Colorado):**

**Purpose:** Provides "Generator" and "Faraday's Law" simulations.

**How it helps:** Perfect for **Topic 1.2**. You can manually spin a magnet and watch the AC voltage waveform be generated in real-time, helping you understand the relationship between rotation and frequency.

- **GeoGebra (Graphing Calculator):**

**Purpose:** A mathematical tool for 2D/3D graphing and geometry.

**How it helps:** Excellent for **Topic 1.7 & 1.8**. You can plot vectors, perform vector additions, and visualize how the resultant vector changes as you change the phase angle ( $\phi$ ).

**VLab (Virtual Labs by Ministry of Education, India):**

**Purpose:** Online access to labs for various engineering disciplines.

**How it helps:** Use the "Basic Electrical Engineering Lab" to perform virtual experiments on AC waveforms. It is great for practicing how to use a Virtual Oscilloscope to measure Peak and RMS values.

## 2. Video Learning Repository

Use these specific search keywords on YouTube or NPTEL to find the best lectures for this unit:

Topic Name	Recommended Channel / Course / Lecturer Name	Search Keywords
AC vs DC Comparison	Engineering Mindset	"AC vs DC power explained Engineering Mindset"
Generation of AC Voltage	Lesics (formerly Learn Engineering)	"How an Alternator works Lesics"
AC Terminologies (RMS, Avg, etc.)	NPTEL - Basic Electrical (Prof. Nagendra Krishnapura)	"RMS and Average value of sine wave NPTEL"
Phase & Phase Difference	Khan Academy (Physics/Electrical)	"Phase and phase difference in AC circuits"
Vector/Phasor Representation	The Organic Chemistry Tutor (Engineering Physics)	"Introduction to Phasors and AC circuits"
Rectangular to Polar Conversion	Math and Science (Jason Gibson)	"Convert complex numbers rectangular to polar"

Topic Name	Recommended Channel / Course / Lecturer Name	Search Keywords
<b>Vector Addition (Analytical)</b>	Ikeda	"Addition of alternating quantities using phasor diagram"
<b>Fundamentals of AC (Full Unit)</b>	Learn Engineering / Engineering Funda	"AC Fundamentals Diploma Electrical Engineering"

---

### Mentorship Note

In today's digital age, the most successful engineers are those who use **Virtual Tools** to test their ideas before touching physical wires. Spend at least 30 minutes on the **Falstad Simulator**; seeing the current "slosh" back and forth in an AC circuit will give you an "Aha!" moment that no textbook can provide. When you go for your **Practical Exams**, mention that you've used these simulators to verify your calculations—it shows your examiners that you have the "Digital Fluency" required in the modern industry!

### 1. Beyond the Syllabus – Emerging Technologies

As a Diploma student, you must realize that the AC fundamentals you learn in Unit 1 are the building blocks for technologies that are currently changing the world.

- **Smart Grids and Phasor Measurement Units (PMUs):**

**The Connection:** In class, we study "Phasors" as a way to represent AC. In the modern power industry, a PMU is a device that measures the electrical waves on an electricity grid in real-time using a common time source for synchronization.

**Why it Matters:** Traditional grids were "blind," but Smart Grids use these synchronized phasor measurements to prevent blackouts. If you master vector representation and phase angles now, you can pursue a career in Grid Automation—a field that is currently seeing massive investment globally.

- **Wireless Power Transfer (WPT) for Electric Vehicles:**

**The Connection:** WPT relies on "Resonance" and "Alternating Magnetic Fields"—concepts that begin with Faraday's Law and AC generation.

**Why it Matters:** Imagine charging your EV just by parking it over a pad. This technology uses high-frequency alternating current to create a magnetic field that transfers energy without wires. Understanding frequency and AC waveforms is essential if you want to work in the R&D departments of EV giants like Tesla, Tata Motors, or MG.

---

### 2. MOOC & Online Course Recommendations

To gain a "Distinction" grade and improve your resume, I recommend these specific courses:

- **Course Title:** Basic Electrical Circuits

**Platform:** NPTEL / SWAYAM

**How it Complements:** This course is taught by top IIT professors. It provides advanced mathematical insights into AC waveforms and serves as a perfect bridge between your Diploma studies and a Degree (B.E./B.Tech) in the future.

- **Course Title:** Introduction to Solar Systems and AC Fundamentals

**Platform:** Coursera (Audit Mode)

**How it Complements:** Since your branch is Electrical/Renewable Energy, this course shows you how the DC power generated by solar panels is converted into the AC power we studied in Unit 1 using Inverters.

---

### 3. Industrial Exposure / Field Visit Suggestions

To truly understand AC Fundamentals, you need to see the scale at which it operates. Here are three field visit suggestions:

- **220kV or 400kV Electrical Substation (e.g., GETCO/PGCIL):**

**What to Observe:** Look at the massive transformers and the **Capacitor Banks**.

**The Unit 1 Connection:** You will see the physical equipment used to correct the "Phase Lag" we discussed in Lecture 5. Seeing a capacitor bank as large as a room makes the concept of "Leading Power Factor" unforgettable.

- **A Local Thermal or Hydroelectric Power Plant:**

**What to Observe:** The **Alternator** (AC Generator).

**The Unit 1 Connection:** Observe the RPM (speed) of the turbine and how it is strictly maintained to ensure a constant **Frequency of 50 Hz**. You will see Faraday's Law in action at a massive scale.

- **Industrial Manufacturing Unit (with large Induction Motors):**

**What to Observe:** The Control Panel and the **Power Factor Meter**.

**The Unit 1 Connection:** Watch the meter as heavy motors start. You will see how the phase difference between voltage and current changes with the load, bringing your "Lagging and Leading" theory to life.

---

### 4. AI Avatar Video Script (Unit 1 Overview)

**Duration:** 60 Seconds

**Tone:** Energetic, Professional, and Motivational

**[0:00 - 0:10] WELCOME & HOOK:***(Avatar smiles, standing in a virtual high-tech lab)* "Hello, future Electrical Technocrats! Welcome to the world of AC Fundamentals. Did you know that every light, fan, and motor around you is dancing to the rhythm of a sine wave? Today, we unlock the secrets of that rhythm."

**[0:10 - 0:30] CORE CONTENT (The Sine Wave):***(Graphic appears: A rotating loop generator and a sine wave forming next to it)* "In Unit 1, we don't just see electricity; we measure its pulse. From Faraday's Law to the generation of alternating voltage, we learn why AC is the backbone of our modern world. We'll master the language of Frequency, RMS values, and the power of Phasors."

**[0:30 - 0:50] INDUSTRY RELEVANCE:***(Visual shifts to a Smart City grid and an EV Charging station)* "Why does this matter? Because whether you are managing a national power grid or designing the next generation of Electric Vehicles, your success depends on understanding how AC quantities lead, lag, and combine. This isn't just theory—it's the foundation of your engineering career."

**[0:50 - 1:00] SUMMARY & TRANSITION:** "By the end of this unit, you'll be able to calculate AC values like a pro and visualize vectors with ease. Get ready to power up your knowledge as we dive into Topic 1: The Basics of AC Generation. Let's get started!"

---

### **Mentorship Note**

Mastering AC Fundamentals is like learning the DNA of Electrical Engineering. Don't be intimidated by the math; instead, focus on the **visualization**. Use the simulators, watch the field visit videos, and always ask yourself: "*How would this look on an oscilloscope?*" If you can visualize the wave, you can solve any problem. You've got this!

### **1. Most Repeated / High-Probability Questions**

Based on standard Diploma Board patterns (like GTU, MSBTE, etc.), these questions represent the core requirements of the syllabus<sup>1111</sup>.

#### **A. Core Definitions & Short Answer (2–3 Marks Each)**

1. Define **Cycle**, **Time Period**, and **Frequency**. State the mathematical relationship between them.
2. Define **Instantaneous Value** and **Maximum Value** of an alternating quantity.
3. Explain the terms **RMS Value** and **Average Value**. Why is the RMS value called the "effective value"?
4. Define **Form Factor** and **Peak Factor**. State their values for a purely sinusoidal wave.
5. What is meant by **Phase Difference**? Briefly explain "In-phase" quantities.

#### **B. Explanatory & Diagram-Based Questions (3–4 Marks Each)**

6. Explain the generation of alternating voltage in a single loop generator with a neat sketch and relevant equations.
7. Represent a sinusoidal alternating quantity as a **Phasor (Vector)**. Explain why vectors are used in AC analysis.
8. Differentiate between **Lagging** and **Leading** alternating quantities with the help of waveforms and mathematical equations.
9. Explain the **Graphical Method** for the addition of two alternating quantities using the parallelogram law of vectors.

10. Describe the **Analytical Method** (Component Method) for adding two vectors  $V_1$  and  $V_2$  having a phase difference  $\phi$
- 

## 2. Application & Logical Thinking Questions

*These questions are designed to test your deeper understanding and help you achieve "Distinction" level scores.*

1. **System Rating:** If the peak voltage of a household supply is 325V, why do we refer to it as a "230V supply"? Justify your answer using the concept of RMS value.
  2. **Frequency Change:** A motor is designed to work at 50 Hz. If the frequency of the supply increases to 60 Hz, what will happen to the Time Period ( $T$ ) and the Angular Frequency ( $\omega$ )? Calculate the percentage change.
  3. **Vector Transformation:** You are given an impedance in rectangular form as  $Z = 3 + j4$ . Why is it necessary to convert this into Polar form ( $Z \angle \theta$ ) before performing multiplication or division in an AC circuit?
  4. **Phase Justification:** In a particular circuit, the current reaches its maximum value 30 degrees after the voltage. (a) Is the current leading or lagging? (b) Write the standard sinusoidal equations for both if  $V_m = 100V$  and  $I_m = 10A$ .
  5. **Waveform Analysis:** Why is the "Average Value" of a complete sinusoidal cycle zero? Explain how engineers overcome this problem to find a meaningful average for power calculations.
- 

### Mentorship Note

In Diploma exams, **Unit 1** is the foundation for the entire AC circuit syllabus. Examiners often prioritize **Vector Math** (Rectangular to Polar) and **RMS/Average definitions**. If you can master the derivation of  $V_{RMS} = 0.707 V_m$ , you have already secured a significant portion of your marks. Don't just memorize the definitions—draw the waveforms! A well-labelled diagram can often earn you full marks even if your explanation is brief.

## Unit 2 Study Plan: Single Phase AC Series Circuits

Total Weightage: 29% | Suggested Time: 12 Lecture Hours

Sequence	Topic Breakdown	Category	Time (Hrs)	Exam Importance	Practical Relevance
1	<b>Pure Resistive (R) Circuits:</b> Equations for $V_R$ , $I_R$ , $P_R$ , and power factor; waveforms and vector diagrams <sup>555</sup> .	Core	1.5	Moderate	High (Heating loads)
2	<b>Pure Inductive (L) Circuits:</b> Inductive reactance ( $X_L$ ), phase lag, and power equations <sup>666</sup> .	Core	1.5	High	High (Motors/Chokes)
3	<b>Pure Capacitive (C) Circuits:</b> Capacitive reactance ( $X_C$ ), phase lead, and power equations <sup>777</sup> .	Core	1.5	High	High (Capacitor banks)
4	<b>RL and RC Series Circuits:</b>	Supporting	2.5	Very High	Critical (Real-

Sequence	Topic Breakdown	Category	Time (Hrs)	Exam Importance	Practical Relevance
	Impedance ( $Z$ ) derivation, impedance triangle, and phasor diagrams <sup>8</sup> .				world loads)
5	<b>RLC Series Circuits:</b> Resultant impedance, voltage triangles, and phase angle calculations <sup>9</sup> .	Core	2.0	Very High	Fundamental for systems
6	<b>Power Concepts:</b> Active ( $P$ ), Reactive ( $Q$ ), and Apparent ( $S$ ) power; The Power Triangle.	Application	1.0	Critical	Billing & Efficiency
7	<b>Series Resonance:</b> Resonance frequency ( $f_r$ ) condition, derivation, and effects on circuit impedance.	Advanced	1.0	Very High	Tuning & Protection
8	<b>Numerical Problem Solving:</b> Comprehensive practice covering all series configurations.	Application	1.0	Critical	Essential for ESE

#### Strategic Insights for Success

- **The "Core" Focus:** You must develop mastery over the **Impedance Triangle** and **Power Triangle**. These are the visual maps that make complex AC math simple.

- **Outcome-Based Goal:** By the end of this unit, you should be able to apply these principles to solve and troubleshoot industrial electrical circuits.
- **Practical Synergy:** While studying this theory, focus on your laboratory experiments (Practicals 3 through 8), as they directly verify the voltage, current, and resonance concepts we discuss here.

### Suggested Learning Resources


- **Primary Text:** *A Text Book of Electrical Technology (Vol-1)* by B.L. Theraja.
- **Digital Supplement:** Electronics-Tutorials: AC Circuits

As an expert lecturer in Electrical Engineering, I am delighted to break down the core behaviors of Alternating Current (AC) through these three fundamental components. Understanding these is like learning the "ABC" of AC circuits; it's the foundation for everything else you will learn.

## Lecture 1: Behavior of AC through pure resistive, inductive and capacitive circuit
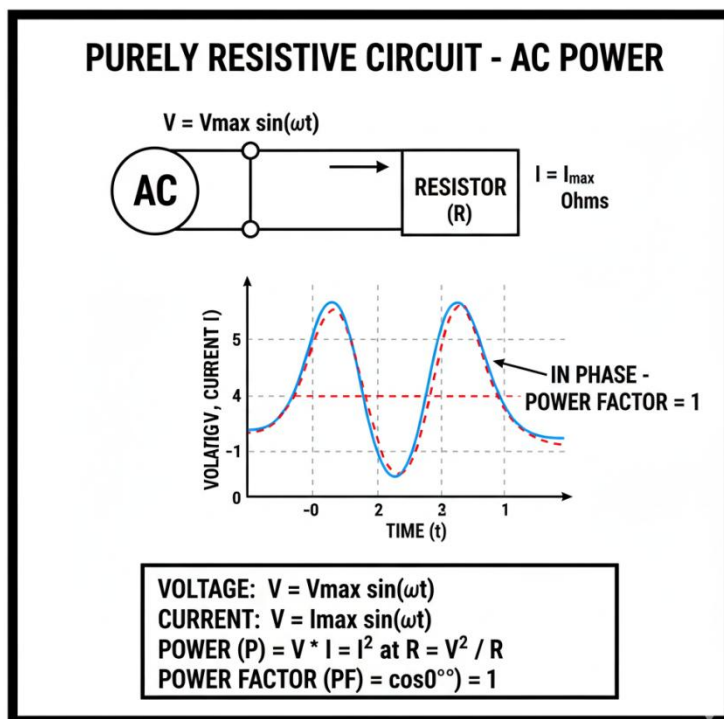
### 1. Purely Resistive Circuit

In a purely resistive circuit, the component offers simple resistance ( $R$ ) to the flow of current, and all electrical energy is converted into heat.



[a] Equations:

**Voltage:**  $v = V_m \times \sin(\omega t)$

**Current:**  $i = I_m \times \sin(\omega t)$ , where  $I_m = V_m / R$

**Instantaneous Power:**  $p = v \times i = V_m \times I_m \times \sin^2(\omega t)$

**Average Power:**  $P = V_{rms} \times I_{rms}$  (measured in Watts)

**Power Factor:**  $\cos(\phi) = 1$  (Unity)


[b] Diagrams:

**Waveform:** Voltage and current waveforms reach their peaks and zeros at the same time.

**Vector (Phasor) Diagram:** The voltage and current vectors are aligned (in phase).
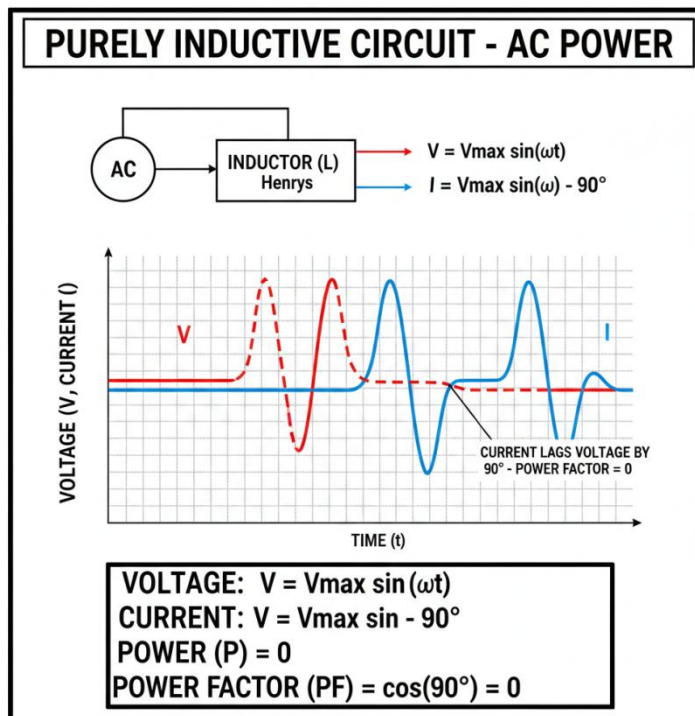
## 2. Purely Inductive Circuit

A pure inductor opposes changes in current by inducing a "back EMF," causing the current to lag behind the voltage.



(a) Equations:

Voltage:  $v = V_m \times \sin(\omega t)$

Current:  $i = I_m \times \sin(\omega t - 90^\circ)$ ,  
where  $I_m = V_m / X_L$

Average Power:  $P_{avg} = 0$

(Energy alternates between the source and the inductor's magnetic field)

Power Factor:  $\cos(90^\circ) = 0$  (Lagging)

(b) Inductive Reactance ( $X_L$ ):

This is the opposition offered by an inductor to AC.


It is defined as:  $X_L = 2 \times \pi \times f \times L = \omega \times L$ , measured in Ohms ( $\Omega$ )

(c) Diagrams:

- **Waveform:** The current wave starts 90° (a quarter-cycle) after the voltage wave.

- **Vector Diagram:** The current vector ( $I$ ) is drawn  $90^\circ$  clockwise (lagging) relative to the voltage vector ( $V$ ).

#### 4. Purely Capacitive Circuit

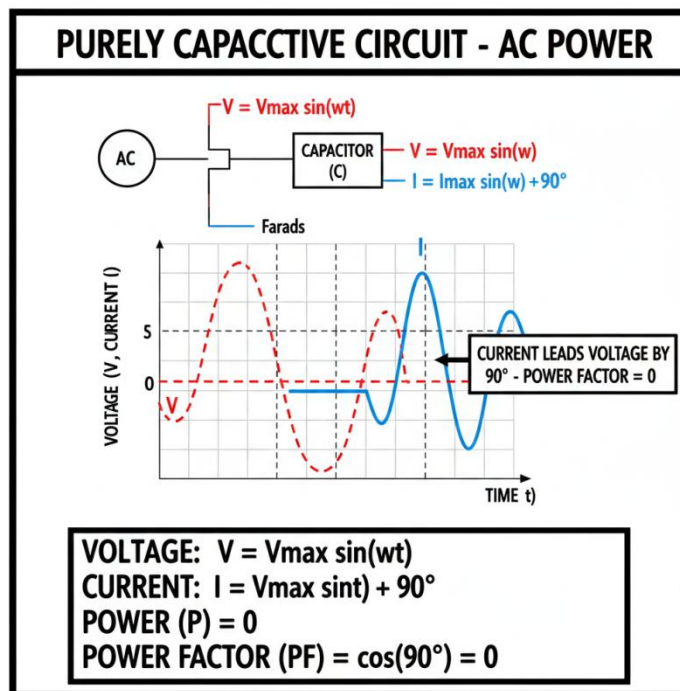

A capacitor opposes changes in voltage. As the voltage increases, the capacitor charges, causing current to lead the voltage.

##### (a) Equations:

**Voltage:**  $v = V_m \times \sin(\omega t)$

**Current:**  $i = I_m \times \sin(\omega t + 90^\circ)$ ,

where  $I_m = V_m / X_c$

**Average Power:**  $P_{avg} = 0$

(Energy alternates between the source and the capacitor's electric field)

**Power Factor:**  $\cos(90^\circ) = 0$  (Leading)

##### (b) Capacitive Reactance ( $X_c$ ):

This is the opposition offered by a capacitor to AC.

It is defined as:  $X_c = 1 / (2 \times \pi \times f \times C) = 1 / (\omega \times C)$ , measured in Ohms ( $\Omega$ )

##### (c) Diagrams:

- **Waveform:** The current wave starts  $90^\circ$  before the voltage wave.

- **Vector Diagram: The current vector (I) is drawn 90° counter-clockwise (leading) relative to the voltage vector (V).**

Circuit Element	Opposition	Current Phase	Power Factor	Average Power
<b>Resistor (R)</b>	R	In Phase (0°)	1 (Unity)	$V \times I$
<b>Inductor (L)</b>	$X_L = \omega \times L$	Lags by 90°	0 (Lagging)	0
<b>Capacitor (C)</b>	$X_C = 1 / (\omega \times C)$	Leads by 90°	0 (Leading)	0

#### Behavior of a Pure Capacitor in an AC Circuit

This video provides a visual and mathematical walkthrough of how a pure capacitor interacts with AC, reinforcing the lead/lag concepts we just discussed.

<https://youtu.be/ef1dVXXwF90>

## **Lecture 2: Behaviour of AC through RL, RC, and RLC series circuit:**


### **1. The Hook: Why does your fan motor get hot? (5 Minutes)**

Think about the ceiling fan in your room. It has a copper coil (an inductor). If it were a *pure* inductor, it wouldn't consume any real power—it would just "borrow" energy and give it back. But after running for an hour, the motor feels hot. Why? Because the wire has internal **Resistance (R)**. You are actually looking at an **RL Series Circuit**. Understanding these combinations is the secret to knowing why your electricity bill is what it is!

---

### **2. Core Concepts: The Power of Three (40 Minutes)**
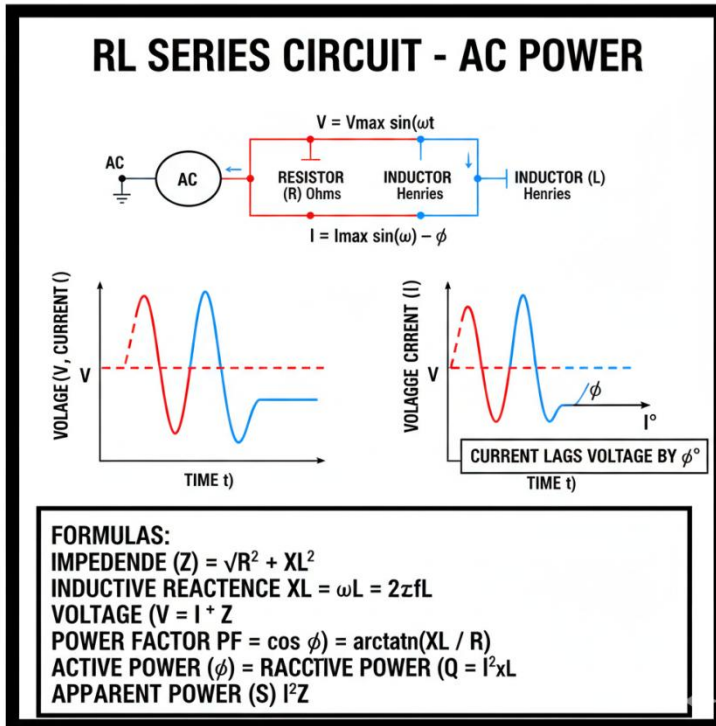
#### **A. The RL Series Circuit (Resistance + Inductance)**



When we connect R and L in series, the same current (I) flows through both.


Voltage Equations: The total voltage V is the vector sum of VR (voltage across resistor) and VL (voltage across inductor).

$$V = \sqrt{V_R^2 + V_L^2} = I \times \sqrt{R^2 + X_L^2}$$

- Impedance (Z): The total opposition is  $Z = \sqrt{R^2 + X_L^2}$
- 
- Current (I):  $I = V / Z$ . In an RL circuit, the current lags the voltage by an angle  $\phi$ .
- 
- Power Factor:  $\cos(\phi) = R / Z$
- 

#### B. The RC Series Circuit (Resistance + Capacitance)

## RC SERIES CIRCUIT - AC POWER

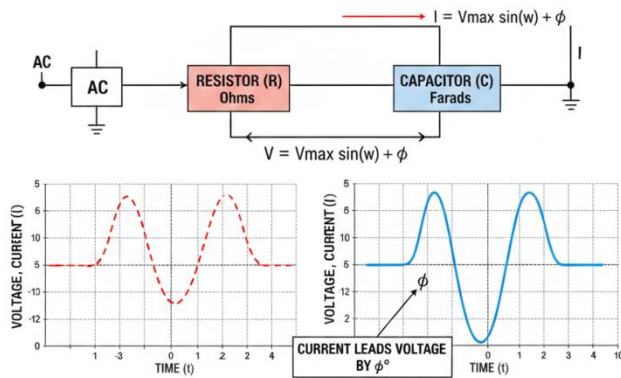


### FORMULAS:

IMPEDENCE (Z) =  $\sqrt{R^2 + X_C^2}$   
 CAPACITIVE REACTANCE  $X_C = 1/2\pi fC$   
 POWER FACTOR PF =  $\cos \phi = \arctan(X_C / R)$   
 ACTIVE POWER (P) = REACTIVE POWER (Q) =  $I^2 X_C$   
 APPARENT POWER (S) =  $I^2 Z$

Here, the capacitor introduces a "leading" effect.

- Voltage:  $V = \sqrt{V_R^2 + V_C^2} = I \times \sqrt{R^2 + X_C^2}$
- 
- Impedance:  $Z = \sqrt{R^2 + X_C^2}$
- 
- Current: I leads the voltage by angle  $\phi$

C. The RLC Series Circuit:

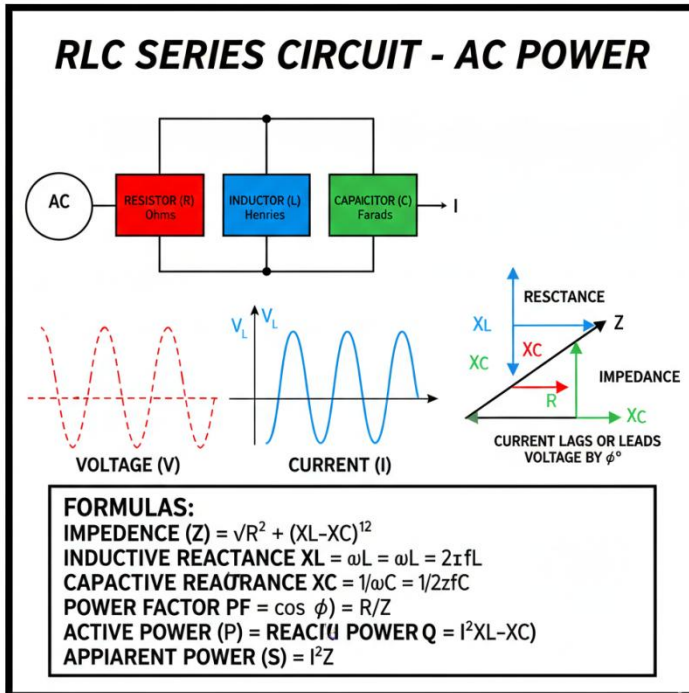

The Ultimate Battle In an RLC circuit, L tries to make current lag, while C tries to make it lead.

- Net Reactance (X):  $X = X_L - X_C$
- Total Impedance:  $Z = \sqrt{R^2 + (X_L - X_C)^2}$
- Phase Angle: If  $X_L > X_C$ , the circuit is inductive (lagging). If  $X_C > X_L$ , it is capacitive (leading)

#### The Impedance Triangle (Visual Tool)

Imagine a right-angled triangle. The base is Resistance (R), the height is Net Reactance ( $X_L - X_C$ ), and the hypotenuse is the total Impedance (Z). This triangle is your best friend for solving numerical problems!

### 3. Real-World / Industry Applications (10 Minutes)

In industry, almost all AC motors are **RL loads**. Because they are inductive, they have a "poor" lagging power factor. Factories use **Capacitor Banks (C)** in series or parallel to create an **RLC environment** that "corrects" the power factor back toward unity<sup>888</sup>. This reduces the current drawn from the grid, saving thousands of dollars in electricity penalties.

### 4. Summary & Q&A (5 Minutes)

**Key Takeaway:** Impedance (Z) is the combined opposition of resistance and reactance.

**Quick Formula Check:**  $V = I \times Z$  ; **Power (P)** =  $V \times I \times \cos(\phi)$

**Common Doubt:** "Sir, can we just add VR and VL like  $2 + 2 = 4$ ?"

**Answer:** No! Because they are out of phase, we must use Vector Addition (Pythagoras theorem).

### Mentorship Note: The "System" Perspective

Mastering RL and RLC circuits is the first step toward becoming a **Power Systems Engineer**. Whether you are designing a simple home inverter or managing a massive substation, these equations stay the same. If you can visualize the **Impedance Triangle** in your head, you will be able to troubleshoot complex industrial faults that others might miss. Keep practicing the numerical—your calculator is your most powerful tool this semester!

Hello students! Welcome to today's session on what I like to call the "efficiency metric" of the electrical world. If you've ever wondered why some electrical systems are considered "healthy" while others are "wasteful," today you will find the answer. We are diving into the **Concepts of Power Factor: Lagging, Leading, and Unity**.

---

## Lecture 3: Concepts of power factor: lagging, leading and unity power factor

### 1. Hook / Introduction: The "Frothy Coffee" Analogy (≈ 5 minutes)

Imagine you walk into a café and order a large mug of cappuccino. When the waiter brings it, the mug is full to the brim. However, as you look closer, you see that 80% of the mug is liquid coffee, but the top 20% is just foam.

In electrical engineering, that **liquid coffee** is the "Active Power" (the stuff that actually does the work, like turning a motor). The **foam** is "Reactive Power" (necessary to create magnetic fields but doesn't do "work"). The **entire mug**—coffee plus foam—is "Apparent Power."

**The Question:** If you are paying for the whole mug, wouldn't you want as much coffee and as little foam as possible? That ratio of coffee to the whole mug is exactly what **Power Factor** is! <sup>1</sup>

---

### 2. Core Concepts: The Three Faces of Power Factor (≈ 40 minutes)

- Technically, the Power Factor (PF) is defined as the cosine of the phase angle ( $\phi$ ) between the voltage (V) and the current (I).
- $PF = \cos(\phi) = \text{Active Power (W)} / \text{Apparent Power (VA)} = R / Z$
- A. Unity Power Factor ( $\cos \phi = 1$ )
- **The Scenario:** Voltage and current are perfectly in step—they reach their peaks and zeros at the exact same time<sup>3</sup>.
- **The Cause:** This happens in purely resistive circuits, such as an electric heater or an old-fashioned incandescent bulb<sup>444</sup>.
- **The Result:** There is zero "foam" (reactive power). Every bit of energy sent from the source is converted into useful work or heat.

#### B. Lagging Power Factor


- **The Scenario:** The current "lags" behind the voltage. Imagine the voltage starting to run and the current trailing behind by an angle  $\phi$ <sup>5</sup>.
- **The Cause:** This is caused by **Inductive loads** like motors, transformers, and fan coils<sup>666</sup>. These devices use energy to build magnetic fields, which "delays" the current.

+1

- **The Impact:** Most industrial equipment is inductive, meaning the majority of the world operates at a lagging PF.
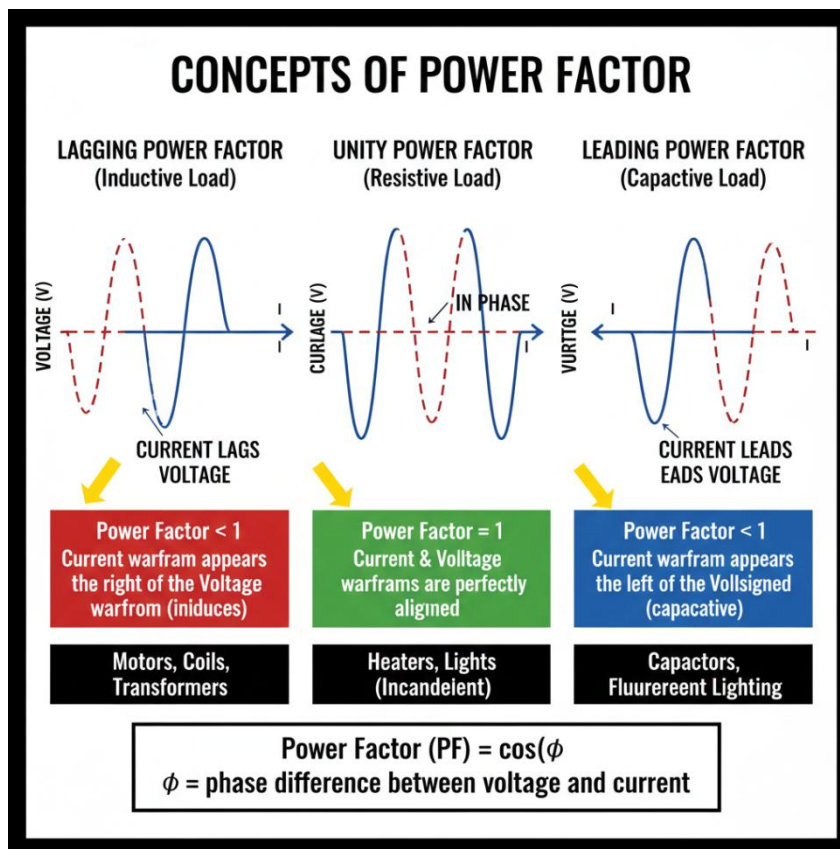
### C. Leading Power Factor

- **The Scenario:** The current gets a "head start" and leads the voltage<sup>7</sup>.
- **The Cause:** This is caused by **Capacitive loads**<sup>88</sup>. Capacitors store energy in electric fields and "push" the current ahead.
- **The Strategy:** In engineering, we don't usually have "purely" capacitive machines. Instead, we use capacitors as "medicine" to fix the lagging problems caused by motors.



### 3. Real-World / Industry Applications (≈ 10 minutes)

In a factory filled with heavy motors (lagging loads), the Power Factor can drop to 0.7 or lower. This is bad news for two reasons:

1. **I<sup>2</sup>R Losses:** To provide the same amount of work, a low PF circuit must draw much more current, which heats up the wires and wastes energy.
2. **Penalties:** Electricity distribution companies like GETCO or PGVCL monitor your PF. If it drops below a certain limit (usually 0.9 or 0.95), they charge a massive **Power Factor Penalty** on your bill<sup>9</sup>.

**The Solution:** Engineers install **Capacitor Banks**<sup>10101010</sup>. The leading PF of the capacitors "cancels out" the lagging PF of the motors, bringing the system back toward **Unity**.

+1

---

#### 4. Summary & Q&A (≈ 5 minutes)

- **Key Takeaway:** Power Factor tells us how efficiently we are using electricity.
  - **Quick Revision:** Inductors = Lagging; Capacitors = Leading; Resistors = Unity<sup>11</sup>.
  - **Common Doubt:** "Sir, is a Leading PF 'better' than a Lagging one?"
    - **Answer:** Not necessarily. Any deviation from 1.0 (Unity) means you are carrying "foam" in your mug. However, we love Leading PF because it is the tool we use to neutralize Lagging PF.
- 

#### Mentorship Note: Your Career as a Power Quality Expert

Mastering the Power Factor is your first step toward becoming a **Power Quality Consultant** or a **Utility Engineer**. Large industries pay top dollar to electrical technocrats who can analyze their circuits and suggest the right capacitor banks to eliminate electricity bill penalties<sup>12</sup>. As you move into your lab sessions to measure PF in RL and RLC circuits, remember: that phase shift you see on the CRO is where millions of rupees are saved or lost in the industry<sup>13</sup>!

Hello students! Welcome to our session on the "Three Dimensions of Power." If you've ever looked at an industrial electricity bill, you might have noticed it's much more complex than the one you get at home. Today, we are going to understand the mathematical and physical reality behind those numbers: **Active, Reactive, and Apparent Power**.

---

### Lecture 4: Active power, reactive power, apparent power and power triangle

#### 1. Hook / Introduction: The "Glass of Juice" Analogy (≈ 5 minutes)

Imagine you are very thirsty and order a glass of fresh orange juice. The waiter brings a tall glass. At the bottom, you have the delicious **liquid juice**, but at the top, there is a thick layer of **foam**.

- The **liquid juice** is what actually quenches your thirst.
- The **foam** is there, taking up space in the glass, but it doesn't quench your thirst.
- The **total glass** (juice + foam) is what you have to hold and what the waiter had to carry from the kitchen.

In our electrical system, the liquid is **Active Power**, the foam is **Reactive Power**, and the whole glass is **Apparent Power**. Let's see why we need to understand all three to be successful electrical engineers!

---

## 2. Core Concepts: The Power Triangle ( $\approx$ 40 minutes)

In AC circuits, because of the phase difference between voltage and current, we deal with three types of power<sup>1111</sup>.

### A. Active Power (P)

- **Definition:** This is the "Real" or "True" power that actually performs work, such as rotating a motor shaft or heating an element<sup>2222</sup>.
- **Formula:**  $P = V I \cos(\phi)$
- **Unit:** Watts (W) or Kilowatts (kW).

### B. Reactive Power (Q)

- **Definition:** This power oscillates between the source and the load. It is used to create the magnetic fields in inductors or electric fields in capacitors<sup>3333</sup>. It does no "useful" work but is necessary for the equipment to function.
- **Formula:**  $Q = V I \sin(\phi)$
- **Unit:** Volt-Ampere Reactive (VAR) or kVAR.

### C. Apparent Power (S)

- **Definition:** This is the total power that the electricity provider must supply to the circuit. It is the vector sum of active and reactive power<sup>4444</sup>.
- **Formula:**  $S = V I$  or  $S = \sqrt{P^2 + Q^2}$
- **Unit:** Volt-Ampere (VA) or kVA.

### The Power Triangle

Visualizing these is easy with a right-angled triangle:

1. **Base:** Active Power (P)
2. **Perpendicular:** Reactive Power (Q)
3. Hypotenuse: Apparent Power (S)

The angle between  $P$  and  $S$  is our old friend, the phase angle ( $\phi$ ). Therefore,  $\cos(\phi) = P / S$  which is the Power Factor!

---

## 3. Real-World / Industry Applications ( $\approx$ 10 minutes)

Why does this matter to a Diploma Engineer?

- **Equipment Rating:** Transformers and Alternators are always rated in **kVA (Apparent Power)**, not kW<sup>5</sup>. Why? Because the manufacturer doesn't know if you will connect a heater (Active load) or a motor (Reactive load). They must build the machine to handle the total current (Apparent Power).

- **Billing:** Large industries are billed based on their **kVA** demand. If they have too much "foam" (Reactive Power), their kVA goes up, and their bill skyrockets. This is why we use capacitor banks to reduce Q and bring S closer to P.
- 

#### 4. Summary & Q&A (≈ 5 minutes)

- **Key Takeaway:** P is for work, Q is for fields, and S is the total supply.
  - **Quick Check:** If  $\phi = 0$  (Unity PF), then  $Q = 0$  and  $S = P$
  - **Common Doubt:** "Sir, if Reactive Power doesn't do work, why can't we just eliminate it?"  
**Answer:** We can't! You cannot run an induction motor without a magnetic field, and you cannot have a magnetic field without Reactive Power. We just try to supply it locally (using capacitors) rather than drawing it from the grid.
- 

#### Mentorship Note: The "Big Picture" Engineer

Mastering the **Power Triangle** is what differentiates a technician from an Engineer. When you go for an interview at a power plant or a manufacturing unit, they will likely ask you why transformers are rated in kVA. Your ability to explain the relationship between these three powers shows that you understand the economic and technical efficiency of a power system. Keep this triangle in your heart—it is the foundation of power system analysis!

### Lecture 5: Resonant condition and resonance frequency in RLC series circuit

#### 1. Hook / Introduction: The Playground Swing (≈ 5 minutes)

Have you ever noticed that when you push someone on a swing, there is a specific "rhythm" or timing you need to follow? If you push too fast or too slow, the swing doesn't go very high. But if you push at just the right moment, the swing reaches its maximum height with very little effort.

In Electrical Engineering, every RLC circuit has its own "natural rhythm." When we provide AC power at exactly that frequency, the circuit "resonates." The result? The opposition to current drops to its absolute minimum, and the current reaches its maximum peak. Today, we will learn how to find that "sweet spot" known as the **Resonance Frequency**<sup>1</sup>.

---

#### 2. Core Concepts: The State of Perfect Balance (≈ 40 minutes)

##### A. The Condition for Resonance


In an RLC series circuit, total Impedance (Z) is given by:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance occurs when the "rivalry" between the Inductive Reactance ( $X_L$ ) and Capacitive Reactance ( $X_C$ ) ends in a tie.

- **Condition:**  $X_L = X_C$

## SERIES AC RESONANCE CONDITION

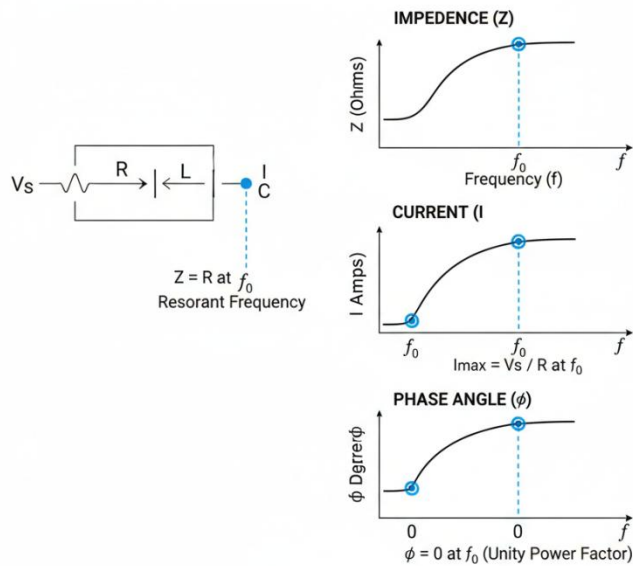

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- When this happens, the term  $(X_L - X_C)$  becomes zero.
- The Impedance becomes **Minimum** and purely resistive:  $Z = R$ .

### B. Deriving Resonance Frequency ( $f_r$ )

To find the exact frequency where this happens, we set the reactance equal:

$2\pi f_r L = 1 / (2\pi f_r C)$  Solving for  $f_r$ , we get the Golden Formula:

$f_r = 1 / (2\pi \sqrt{LC})$

### C. Characteristics of Series Resonance

1. **Impedance is Minimum:**  $Z = R$ .
2. **Current is Maximum:**  $I = V / R$ .
3. **Power Factor is Unity:**  $\cos(\phi) = 1$  The circuit behaves like a pure resistor.
4. **Voltage Magnification:** Paradoxically, the voltage across L or C can be much higher than the supply voltage!

### 3. Real-World / Industry Applications ( $\approx 10$ minutes)

Why do we care about resonance?

- **Radio and TV Tuning:** When you turn the dial on an old radio to "tune in" to a station, you are actually changing a variable capacitor inside. You are adjusting the circuit's  $f_r$  to match the station's frequency. When they match, resonance occurs, the current peaks, and you hear the music!

- **Communication Filters:** Resonance allows us to "accept" one specific frequency while "rejecting" all others.
- **Hazardous Resonance:** In power systems, accidental resonance can cause massive voltage spikes that can blow up transformers. Engineers must design systems to *avoid* resonance in power lines.

#### 4. Summary & Q&A (≈ 5 minutes)

- **Key Takeaway:** Resonance happens when  $X_L = X_C$ .
- **The Formula:**  $f_r = 1 / (2\pi \sqrt{L C})$ .
- **Typical Student Doubt:** "Sir, if  $X_L$  and  $X_C$  cancel out, does that mean there is no voltage across them?"

**Answer:** No! There is actually a *lot* of voltage across them, but they are 180° out of phase, so they cancel each other out from the perspective of the power source.

#### Mentorship Note: The "Frequency" of Your Career

Mastering resonance is the key to entering the high-tech world of **Telecommunications and Signal Processing**. While Unit 2 focuses on power, these same principles allow your smartphone to pick up a 5G signal out of the air. As you perform **Practical No. 8** in the lab<sup>6</sup>, pay close attention to how the ammeter suddenly jumps to a peak value—that is the moment you've hit resonance. Understanding this "tuning" will make you an invaluable asset in both power industries and electronic design firms!

### Lecture 6: Resonant condition and resonance frequency in RLC series circuit

#### 1. Hook / Introduction: The "Electrical Doctor" (≈ 5 minutes)

Imagine you are a doctor, and a patient (a factory) comes to you because their electricity bill is too high. You can't just say, "You have an inductor problem." You need to calculate *exactly* how much capacitance to add to fix it. Today, you learn to write that "prescription." We are going to solve real-world scenarios where we find the "missing links" in a circuit—be it current, power, or that perfect resonance frequency<sup>22</sup>.

#### 2. Core Concepts: The Problem-Solving Roadmap (≈ 40 minutes)

To solve any AC series numerical, we follow a logical 4-step workflow. Let's walk through it using a classic RLC series example.

##### Step 1: Reactance and Impedance (Z)

First, identify your opponents. If you are given Inductance ( $\$L\$$ ) and Capacitance ( $\$C\$$ ), convert them to Ohms ( $X_L$  and  $X_C$ ) using the frequency ( $f$ ):

$$X_L = 2\pi f L$$

- $X_C = 1 / (2\pi f C)$

- Total Impedance:  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

### Step 2: Current and Voltage Drops

Once you have the total opposition ( $Z$ ), find the total current:  $I = V / Z$ .

- Pro Tip: In a series circuit, current ( $I$ ) is the same everywhere! Use it to find voltage across any component:  $V_R = I \cdot R$ ,  $V_L = I \cdot X_L$ ,  $V_C = I \cdot X_C$

- **Step 3: Power and Power Factor**

Calculate the "useful" work and the "efficiency":

Power Factor:  $\cos(\phi) = R / Z$

Active Power:  $P = V \cdot I \cdot \cos(\phi)$

### Step 4: The Resonance Special Case

If the problem asks for the "Resonance Frequency" ( $f_r$ ), it means  $X_L = X_C$ . You don't even need  $V$  to find this; you just need  $L$  and  $C$ :

$$f_r = 1 / (2\pi \sqrt{LC})$$


---

### 3. Real-World / Industry Applications ( $\approx$ 10 minutes)

In industry, these calculations are used for **Load Balancing**. For example, if a workshop adds a new 5HP induction motor, a diploma engineer calculates the new total  $Z$  and the resulting drop in power factor<sup>11111111</sup>. If the power factor drops below 0.9, you use your numerical skills to calculate the exact kVAR of capacitors needed to avoid heavy penalties from the electricity board<sup>1212</sup>. These aren't just "exam problems"—they are "money-saving" calculations!

---

### 4. Summary & Q&A ( $\approx$ 5 minutes)

- **Key Takeaway:** Always find  $X_L$  and  $X_C$  first.
  - **Revision Point:** If  $X_L > X_C$ , the circuit is inductive (lagging). If  $X_C > X_L$ , it's capacitive (leading).
  - **Typical Student Doubt:** "Sir, why does  $V_L + V_R$  sometimes add up to more than the supply voltage  $V$ ?"
    - **Answer:** Because they are vectors! You must add them using the Pythagoras theorem  $V = \sqrt{V_R^2 + V_L^2}$ , not simple addition.
- 

### Mentorship Note: The Competitive Edge

Mastering these numerical is your "secret weapon" for competitive exams and job interviews. Whether it's the GETCO junior engineer exam or a private technical interview, they will test your ability to solve RLC circuits quickly<sup>15</sup>. Practice these until the **Power Triangle** becomes second nature to you. An engineer who can calculate accurately is an engineer who can be trusted with a multi-million rupee power system! Keep your calculators ready—see you in the tutorial session<sup>16</sup>!

### A. Low-Level Prompts (Remember & Understand)

Focus: Mastering the basics and clear definitions.

1. "Explain the basic concept of [Single Phase AC Series Circuits] in very simple terms, as if you are teaching a beginner."
2. "Give me a list of the top 10 most important terms and definitions I need to know for [Unit 2: Single Phase AC Series Circuits]."
3. "Summarize the behaviour of a [Purely Inductive Circuit] into five clear bullet points for quick revision."
4. "Create a 'Cheat Sheet' of all the fundamental formulas used in [AC Series Circuits], including units for each variable."
5. "What is the difference between [Inductive Reactance] and [Capacitive Reactance]? Explain with a simple analogy."
6. "Explain why [Power Factor] is important in AC circuits using a non-engineering example."
7. "Provide a step-by-step definition for [Active, Reactive, and Apparent Power] and how they relate to each other."
8. "List the three main conditions that must be met for [Series Resonance] to occur."
9. "Create a 5-question multiple-choice quiz on the basics of [Series RLC Circuits] and provide the answers with explanations."
10. "Act as a tutor and explain the significance of the [Impedance Triangle] in solving circuit problems."

---

## **B. Moderate-Level Prompts (Apply & Analyze)**

Focus: Applying your knowledge to solve problems and compare concepts.

11. "I have a circuit with [Resistance, Inductance, and Capacitance] in series. Walk me through the logical steps to find the total Impedance."
12. "Compare a [Purely Resistive Circuit] and a [Purely Capacitive Circuit] in terms of their power consumption and phase angle."
13. "Explain the real-world consequences of having a [Low Lagging Power Factor] in an industrial setting."
14. "Show me how the [Power Triangle] changes when we add a capacitor to a circuit that was previously purely inductive."
15. "Create a practice numerical problem for an [RLC Series Circuit] and show me the step-by-step solution using the vector method."
16. "Analyze why the current is at its maximum value during [Series Resonance]. What happens to the impedance at this point?"
17. "Provide three examples of how [AC Series Circuits] are used in everyday household appliances."

18. "Explain how to draw a [Phasor Diagram] for an RL circuit. Which quantity should I draw on the reference axis and why?"
19. "What are the practical advantages and disadvantages of [Series Resonance] in communication systems?"
20. "If I increase the frequency in an [RLC Series Circuit], how does it affect the Inductive Reactance and the Capacitive Reactance differently?"

### C. High-Level Prompts (Design & Create)

Focus: Solving complex problems and system-level thinking.

21. "Design a step-by-step workflow or 'Algorithm' that I can follow to solve any complex [Single Phase AC Series Circuit] numerical."
22. "Create a troubleshooting guide for an electrical system experiencing [High Reactive Power]. What steps should an engineer take to fix it?"
23. "Develop a logical argument for why a factory should invest in [Power Factor Correction]. Include the technical and economic benefits."
24. "Act as a lead engineer and explain how the concept of [Resonance] is used to design a radio tuning circuit."
25. "Synthesize everything we've learned about [Unit 2] and create a 'Master Concept Map' that connects Reactance, Impedance, Power Factor, and Resonance."

---

### Mentorship Note: AI is Your Assistant, Not Your Replacement

Mastering these prompts will make your self-study sessions 10x more productive. However, the real "engineering magic" happens when you can do these calculations on paper during an exam or troubleshoot a live panel in the lab.

### Part 1: Key Definitions / Glossary

*Essential vocabulary for every Electrical Engineer.*

1. **Inductive Reactance (XL):** The opposition offered by an inductor to the flow of alternating current, measured in Ohms<sup>2</sup>.
2. **Capacitive Reactance (XC):** The opposition offered by a capacitor to the flow of alternating current, measured in Ohms<sup>3</sup>.
3. **Impedance (Z):** The total effective opposition of a circuit to alternating current, combining resistance and reactance<sup>4</sup>.
4. **Phase Angle  $\phi$ :** The angular displacement between the voltage and current vectors in an AC circuit<sup>5</sup>.
5. **Power Factor:** The cosine of the phase angle between voltage and current, indicating circuit efficiency<sup>6</sup>.
6. **Active Power (P):** The actual power consumed by the resistive part of a circuit to perform useful work, measured in Watts<sup>7</sup>.

7. **Reactive Power (Q):** The power that oscillates between source and load to maintain magnetic or electric fields, measured in VAR<sup>8</sup>.
  8. **Apparent Power (S):** The product of RMS voltage and RMS current, representing the total power supplied, measured in VA<sup>9</sup>.
  9. **Admittance (Y):** The reciprocal of impedance, representing the ease with which current flows<sup>10</sup>.
  10. **Series Resonance:** A condition where  $X_L = X_C$ , resulting in minimum impedance and maximum current<sup>11</sup>.
  11. **Resonant Frequency (fr):** The specific frequency at which a series RLC circuit enters a state of resonance<sup>12</sup>.
  12. **Lagging Power Factor:** A condition where current peaks after the voltage, typical in inductive loads<sup>13</sup>.
  13. **Leading Power Factor:** A condition where current peaks before the voltage, typical in capacitive loads.
  14. **Unity Power Factor:** A condition where voltage and current are in phase, resulting in a power factor of 1.0.
  15. **Choke Coil:** An inductor used to limit AC current with minimum power loss.
- 

## Part 2: FAQ & Assessment Section

### A. Multiple Choice Questions (MCQs)

1. In a purely inductive circuit, current \_\_\_\_ the voltage by 90°.
2. The unit of Apparent Power is \_\_\_\_.
3. At series resonance, the impedance of the circuit is \_\_\_\_.
4. A pure capacitor consumes \_\_\_\_ average power.
5. If  $X_L > X_C$ , the circuit power factor is \_\_\_\_.
6. The formula for Inductive Reactance is \_\_\_\_.
7. The power factor of a purely resistive circuit is \_\_\_\_.
8. In an RLC series circuit, the vector sum of  $V_R$ ,  $V_L$ , and  $V_C$  equals \_\_\_\_.
9. As frequency increases, Capacitive Reactance ( $X_C$ ) \_\_\_\_.
10. The ratio of  $R/Z$  represents the \_\_\_\_.
11. Reactive power is measured in \_\_\_\_.
12. At resonance, the phase angle  $\phi$  is \_\_\_\_.
13. The "foam" in the coffee analogy represents \_\_\_\_ power.
14. Transformers are usually rated in \_\_\_\_.

15. A circuit with a power factor of 0.8 lagging is likely \_\_\_\_.
16. The hypotenuse of the Impedance Triangle represents \_\_\_\_.
17.  $f_r = 1 / (2\pi \sqrt{LC})$  is the formula for \_\_\_\_.
18. In an RC series circuit, the current \_\_\_\_ the voltage.
19. To improve a lagging power factor, we connect a \_\_\_\_.
20. The real work-doing component of power is \_\_\_\_.

### B. Short Answer / Viva Questions

1. Why is the power factor of a pure inductor zero?
2. What is the physical significance of the "Power Triangle"?
3. Why do we use the term "Impedance" instead of just "Resistance" in AC?
4. What happens to the current in a series RLC circuit if the frequency is changed from  $f_r$  to a higher frequency?
5. Why are capacitors used in industries with many motors?
6. Explain the condition  $X_L = X_C$  in terms of energy exchange.
7. How does a choke coil differ from a pure resistor in terms of power loss?
8. Can the voltage across a capacitor in a series RLC circuit be higher than the source voltage? Why?
9. Define "Unity Power Factor" and its importance for electricity billing.
10. What is the relationship between the Impedance Triangle and the Power Triangle?

---

### Answer Key for MCQs

1. Lags | 2. VA | 3. Minimum (equal to R) | 4. Zero | 5. Lagging | 6.  $2\pi f L$  | 7. Unity (1.0) | 8. Supply Voltage (V) | 9. Decreases | 10. Power Factor | 11. VAR | 12. Zero degrees | 13. Reactive | 14. kVA | 15. Inductive | 16. Impedance ( $Z$ ) | 17. Resonant Frequency | 18. Leads | 19. Capacitor | 20. Active Power
- 

### Mentorship Note: The Examiner's Mindset

When you sit for your viva or theory exam, remember that examiners look for **conceptual links**. Don't just memorize the resonance formula; understand that it represents a "balance of forces." When you solve numericals, always draw the **Impedance Triangle** first<sup>17</sup>. It prevents calculation errors and shows the examiner you have a "visual" grasp of the physics. Mastery of this unit is your passport to understanding advanced power systems—keep practicing, and stay curious!

### 1. AI Tools & Digital Learning Tools

These tools will help you simulate circuits, visualize phasors, and simplify the heavy mathematical calculations required for this unit.

- **Phet Interactive Simulations (University of Colorado Boulder)**

**Purpose / Use-case:** Virtual circuit construction and visualization.

**How it helps:** Use the "Circuit Construction Kit: AC" to build RL, RC, and RLC series circuits. It allows you to visualize current flow and voltage drops in real-time using virtual oscilloscopes, which is perfect for understanding phase differences.

- **WolframAlpha (Computational Intelligence)**

**Purpose / Use-case:** Advanced mathematical solving and step-by-step calculus.

**How it helps:** It is an incredible calculator for complex number operations (rectangular to polar conversions) and solving resonance frequency equations. You can input "RLC circuit resonance" to see generated impedance plots and transfer functions.

- **EveryCircuit (Mobile/Web Simulator)**

**Purpose / Use-case:** Real-time animated circuit simulation.

**How it helps:** This tool provides a highly visual way to see how changing frequency affects the "glow" of a bulb in a series circuit. It is excellent for practicing problem-solving logic before heading into the physical laboratory.

+4

- **Virtual Labs (vlab.co.in - MoE, Government of India)**

**Purpose / Use-case:** Remote access to physical lab experiments.

**How it helps:** Specifically designed for Diploma and Degree students, the "Basic Electrical Engineering Lab" allows you to virtually perform experiments like measuring the power factor of an RL series circuit or finding the resonant frequency of an RLC circuit

Topic Name	Recommended Channel / Course / Lecturer Name	Search Keywords
Purely Resistive, Inductive, and Capacitive Circuits	NPTEL-NOC IITM / Prof. Satyabrata Jit	AC through pure R L C circuits NPTEL
RL, RC, and RLC Series Circuits (Phasor Diagrams)	Learn Engineering (now Lesics)	RLC series circuit phasor diagram visualization
Power Factor (Lagging, Leading, and Unity)	Electrical4U / Engineering Mindset	Power factor explained lagging leading unity

Topic Name	Recommended Channel / Course / Lecturer Name	Search Keywords
Active, Reactive, and Apparent Power	The Engineering Mindset	Active Reactive Apparent Power Triangle explained
Series Resonance and Resonant Frequency	Swayam Prabha / CEC-UGC	Series resonance in RLC circuit lecture
Numerical Solving: AC Series Circuits	Gate Academy / Electrical Engineering Concepts	Solved problems AC series circuits RLC

### Mentorship Note: Building Your Digital Portfolio

Mastering these digital tools does more than just help you pass Unit 2—it prepares you for the modern industry. Many placement interviews now value students who can demonstrate their understanding using simulation software or reports generated from digital experiments. I encourage you to use these simulators to take screenshots of your results and add them to your course portfolio

### 1. Beyond the Syllabus – Emerging Technologies

#### A. Smart Grids and Advanced Metering Infrastructure (AMI)

In your classroom, you learn about steady-state A.C. circuits. In the real world, the **Smart Grid** is the evolution of this. It uses digital communication to manage A.C. distribution.

- **Application:** Smart grids use real-time data to balance supply and demand. The fundamentals of **Phase angle and Frequency monitoring** are critical here to ensure grid stability when integrating renewable energy like solar and wind.
- **Career Impact:** As a Diploma engineer, understanding how digital controllers interact with A.C. cycles will make you essential for modern utility companies.

#### B. Wireless Power Transfer (WPT) for Electric Vehicles

This technology uses the principle of **Resonance**—the same concept you study in RLC series/parallel circuits.

- **Application:** By matching the resonant frequency of a primary coil (in the ground) and a secondary coil (in the car), power is transferred through magnetic fields without wires.
- **Career Impact:** The EV revolution is just beginning. Knowing how to tune A.C. circuits for maximum power transfer is a high-demand skill in the automotive electronics sector.

Course Title / Theme	Platform	How it Complements the Subject

Course Title / Theme	Platform	How it Complements the Subject
Basic Electrical Circuits	NPTEL / SWAYAM	Provides a rigorous look at KVL/KCL in A.C. circuits and helps master complex number calculations.
Electric Power Systems	Coursera (Audit Mode)	Shows how A.C. fundamentals apply to large-scale power generation and transmission systems.
Introduction to Smart Grid	NPTEL	Connects your knowledge of A.C. waveforms to the future of automated energy management.

### 3. Industrial Exposure / Field Visit Suggestions

Seeing A.C. fundamentals in action at a massive scale is the best way to learn. Here are three regional suggestions:

#### 1. Electrical Substations (220kV/132kV/66kV)

- **What to Observe:** Large capacitor banks used for **Power Factor Correction**, huge transformers, and bus-bar arrangements.
- **Learning Goal:** Understand why maintaining a high power factor is critical for industrial efficiency and how "Reactive Power" is managed in real-time.

#### 2. Solar Power Plants / Solar Parks

- **What to Observe:** The role of **Inverters**. Solar panels produce D.C., but the grid requires A.C.
- **Learning Goal:** Observe the synchronization process where D.C. is converted to a pure 50Hz A.C. sine wave to match the grid.

#### 3. Regional Load Despatch Centres (RLDC)

- **What to Observe:** Real-time monitoring of **System Frequency**.
- **Learning Goal:** See how even a tiny deviation from 50Hz impacts the entire power network, emphasizing the importance of A.C. frequency stability.

---

### 4. Conferences, Seminars & Technical Events

Staying updated with professional bodies is a hallmark of a lifelong learner.

- **IEEE Power & Energy Society (PES) Conferences:** These events focus on the "Powering a Sustainable Future" theme.
  - *Why Attend:* You will see student paper competitions and posters that show how A.C. fundamentals are used to solve global energy crises.

- **National Systems Conference (NSC):** A reputed Indian forum for system-level engineering.
  - *Why Attend:* It exposes you to "System Thinking," helping you move from solving a single circuit on paper to understanding how millions of circuits interact across the country.

## 1. Beyond the Syllabus – Emerging Technologies

### A. Smart Grids and Advanced Metering Infrastructure (AMI)

In your classroom, you learn about steady-state A.C. circuits. In the real world, the **Smart Grid** is the evolution of this. It uses digital communication to manage A.C. distribution.

- **Application:** Smart grids use real-time data to balance supply and demand. The fundamentals of **Phase angle and Frequency monitoring** are critical here to ensure grid stability when integrating renewable energy like solar and wind.
- **Career Impact:** As a Diploma engineer, understanding how digital controllers interact with A.C. cycles will make you essential for modern utility companies.

### B. Wireless Power Transfer (WPT) for Electric Vehicles

This technology uses the principle of **Resonance**—the same concept you study in RLC series/parallel circuits.

- **Application:** By matching the resonant frequency of a primary coil (in the ground) and a secondary coil (in the car), power is transferred through magnetic fields without wires.
- **Career Impact:** The EV revolution is just beginning. Knowing how to tune A.C. circuits for maximum power transfer is a high-demand skill in the automotive electronics sector.

## 2. MOOC & Online Course Recommendations

To strengthen your CV and gain a deeper perspective, I recommend exploring these courses:

Course Title / Theme	Platform	How it Complements the Subject
Basic Electrical Circuits	NPTEL / SWAYAM	Provides a rigorous look at KVL/KCL in A.C. circuits and helps master complex number calculations.
Electric Power Systems	Coursera (Audit Mode)	Shows how A.C. fundamentals apply to large-scale power generation and transmission systems.
Introduction to Smart Grid	NPTEL	Connects your knowledge of A.C. waveforms to the future of automated energy management.

## 3. Industrial Exposure / Field Visit Suggestions

Seeing A.C. fundamentals in action at a massive scale is the best way to learn. Here are three regional suggestions:

### 1. Electrical Substations (220kV/132kV/66kV)

- **What to Observe:** Large capacitor banks used for **Power Factor Correction**, huge transformers, and bus-bar arrangements.
- **Learning Goal:** Understand why maintaining a high power factor is critical for industrial efficiency and how "Reactive Power" is managed in real-time.

### 2. Solar Power Plants / Solar Parks

- **What to Observe:** The role of **Inverters**. Solar panels produce D.C., but the grid requires A.C.
- **Learning Goal:** Observe the synchronization process where D.C. is converted to a pure 50Hz A.C. sine wave to match the grid.

### 3. Regional Load Despatch Centres (RLDC)

- **What to Observe:** Real-time monitoring of **System Frequency**.
- **Learning Goal:** See how even a tiny deviation from 50Hz impacts the entire power network, emphasizing the importance of A.C. frequency stability.

---

### 4. Conferences, Seminars & Technical Events

Staying updated with professional bodies is a hallmark of a lifelong learner.

- **IEEE Power & Energy Society (PES) Conferences:** These events focus on the "Powering a Sustainable Future" theme.

*Why Attend:* You will see student paper competitions and posters that show how A.C. fundamentals are used to solve global energy crises.

- **National Systems Conference (NSC):** A reputed Indian forum for system-level engineering.

*Why Attend:* It exposes you to "System Thinking," helping you move from solving a single circuit on paper to understanding how millions of circuits interact across the country.

### Unit 3: Single Phase AC Parallel Circuits — Study Plan

- **Total Weightage:** 19% (approx. 14 marks in ESE)
- **Allocated Time:** 9 Hours
- **RBT Level:** Application (A)
- **Prerequisite:** Mastery of Vector/Phasor representation and Series AC Circuits (Unit 2).

#### 1. Topic-Wise Breakdown & Sequence

The syllabus content is broken down here into a logical teaching sequence, moving from visualization (Phasors) to calculation (Algebra) and finally to behavior (Resonance).

Sequence	Topic Name	Detailed Content (As per Syllabus)	Hours	Category
3.1	<b>Introduction &amp; Phasor Method</b>	• Concept of parallel circuits (Voltage is constant). • Phasor (Vector) method for solving AC parallel circuits.	1 Hr	Core
3.2	<b>Admittance Terminology</b>	• Define terms: Admittance (Y), Conductance (G), and Susceptance (B). • Relationship between Z & Y, R & G, X & B.	1 Hr	Supporting
3.3	<b>The Admittance Triangle</b>	• Draw Admittance Triangle. • Admittance method for solving AC parallel circuits.	1 Hr	Core
3.4	<b>Complex Algebra Method</b>	• Complex algebra method for solving AC parallel circuits (j operator). • Rectangular vs. Polar form in parallel.	2 Hrs	Core
3.5	<b>Numerical Problem Solving</b>	• Numerical based on AC parallel circuits (RL, RC, RLC parallel branches). •	2 Hrs	Application

Sequence	Topic Name	Detailed Content (As per Syllabus)	Hours	Category
		Calculation of branch currents and total current.		
3.6	Parallel Resonance	• Resonance condition and resonant frequency in parallel AC circuits. • Dynamic Impedance.	1 Hr	Advanced
3.7	Series vs. Parallel Comparison	• Comparison between series and parallel resonance. • Numerical based on parallel resonance.	1 Hr	Supporting

## 2. Strategic Categorization of Topics

To teach effectively, we classify topics by their function in the curriculum.

### Core Topics (The “Must-Knows”)

- **Phasor & Complex Algebra Methods:** Students must realize they cannot simply add branch currents like DC ( $I_T \neq I_1 + I_2$ ). They must use vector addition or complex numbers.
- **Admittance ( $Y = G - jB$ ):** Crucial for simplifying parallel calculations where adding admittances is easier than dealing with reciprocal impedances.

### Supporting Topics (Conceptual Bridges)

- **Admittance Triangle:** A visual tool to help students understand why Conductance ( $G$ ) is the real part and Susceptance ( $B$ ) is the imaginary part of admittance.
- **Comparison of Resonances:** Helps distinguish between “Voltage Magnification” (Series) and “Current Magnification” (Parallel).

### Application-Oriented Topics (Real World)

- **Numericals:** This is an “Application” level unit. Students are expected to calculate total current and power factor for loads connected in parallel (e.g., a fan and a bulb connected to the same supply).
- **Resonance:** Fundamental for understanding radio tuning and filter circuits.

### 3. Exam Importance & Practical Relevance

Topic	Exam Weight	Practical Relevance
Solving Parallel Circuits (Complex/Admittance)	High	Essential. All domestic and industrial loads (lights, motors) are connected in parallel.
Definitions (Admittance, Conductance, Susceptance)	Medium	Important for viva/oral exams and understanding component specs.
Parallel Resonance	High	Critical for communication engineering and power factor correction.
Derivation of Resonant Frequency	Medium	Often asked as a theory question.

### 4. Suggested Activities & Resources

To align with NEP-2020 and the syllabus “Suggested Activities”:

1. **Lab Integration:**

- Perform experiments 9, 10, & 11: Measure voltage, current, and power factor in RL, RC, and RLC parallel circuits.
- Tip: Show students that the source current is less than the arithmetic sum of branch currents.

2. **Chart Making:**

- Activity 10: “Prepare chart of graphical representation of series and parallel resonance”.

3. **Digital Learning:**

- Use CircuitGlobe or Khan Academy (referenced in syllabus [cite: 82, 89]) to visualize how current splits in parallel branches.

Course: Diploma in Electrical Engineering

Subject: AC Fundamental (Code: DI02000171)

Unit 3: Single Phase AC Parallel Circuits

Topic 1: Phasor (Vector) method for solving AC parallel circuits

Duration: 60 Minutes

## Lecture Transcript

### 1. The Hook: Why “Parallel” Matters (5 Minutes)

“Good morning, future engineers! Welcome back. In Unit 2, we conquered Series AC circuits. Remember the old style of decorative lights? If one bulb fused, the whole string went dark because the current had nowhere else to go. That’s a series circuit.

Now, look around this classroom. We have lights, fans, and maybe a projector plugged in. If I switch off the fan, do the lights go out? Of course not. They operate independently. This is because they are connected in **parallel**.

Almost every practical electrical system in the real world—from the wiring in your home to the machines on a factory floor—is connected in parallel. Today, we are going to learn the fundamental method to analyze these circuits: The Phasor (or Vector) Method.


### 2. Core Concepts: The Rule of Voltage and Vector Currents (40 Minutes)

**The Golden Rule of Parallel Circuits** In a series circuit, current was common. In a parallel circuit, the rules flip. The most important concept you must remember today is this:

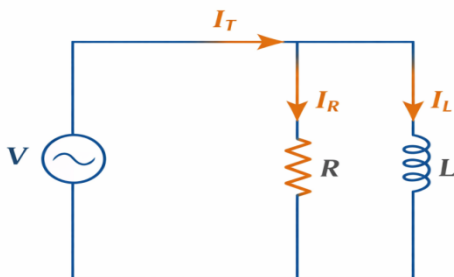**In a Parallel Circuit, the Voltage across all branches is the SAME.**

Whether you have a resistive branch, an inductive branch, or a capacitive branch connected in parallel, they all experience the exact same source voltage ( $V$ ) at the same instant.

**[VISUAL DESCRIPTION 1: Circuit Diagram]** (Imagine a circuit diagram with an AC Voltage Source ‘ $V$ ’ on the left. Two vertical branches are connected across it. Branch 1 contains a Resistor  $R$ . Branch 2 contains an Inductor  $L$ . Show the total current  $I_T$  leaving the source, splitting into  $I_R$  going down the first branch, and  $I_L$  going down the second branch.)



**The Challenge: Adding AC Currents** According to Kirchhoff's Current Law (KCL), the total current ( $I_T$ ) entering a junction must equal the sum of currents leaving it. So,  $I_T = I_R + I_L + \dots$

But here is the catch for Diploma students: **This is NOT simple arithmetic addition.**


If  $I_R$  is 4 Amps and  $I_L$  is 3 Amps, the total current is NOT 7 Amps. Why? Because in AC, these currents happen at different times—they have a phase difference.

**The Solution: The Phasor Diagram** To add currents that are out of phase, we must use phasors (vectors). We need a reference point to start our drawing.

Since voltage ( $V$ ) is common to all branches, we always take Voltage as our reference vector.

Let's draw the phasor diagram for a parallel R-L circuit:

**[VISUAL DESCRIPTION 2: Phasor Diagram Construction]** (Step 1: Draw a horizontal arrow pointing to the right. Label this vector 'V'. This is our reference at  $0^\circ$ .) (Step 2: We know current in a resistor is in phase with voltage. Draw another arrow representing  $I_R$  right on top of the 'V' arrow, pointing right.) (Step 3: We know current in a pure inductor LAGS voltage by  $90^\circ$ . Draw an arrow representing  $I_L$  starting from the origin and pointing straight DOWNWARDS.)

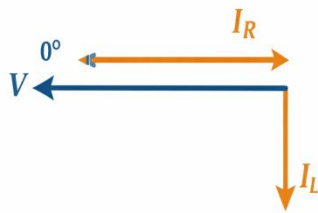

**Finding the Total Current** Now look at your diagram. You have  $I_R$  going right (horizontal component) and  $I_L$  going down (vertical component). The total current  $I_T$  is the resultant vector—the hypotenuse connecting them.

Using Pythagoras theorem on this vector triangle: Total Current,  $I_T = \sqrt{I_R^2 + I_L^2}$

This is why 4A (Resistive) + 3A (Inductive) equals 5A Total, not 7A. We must add them vectorially.

---

**⚡ Electrical Fun Fact:**

Why did AC win over DC for power distribution?

A major reason was the “War of Currents” between Thomas Edison (DC) and Nikola Tesla/George Westinghouse (AC) in the late 1800s. AC won largely because transformers made it easy to step up voltages for efficient long-distance transmission, something very difficult to do with DC at the time.

### 3. Real-World Applications (10 Minutes)

(Connecting theory to practice)

Why are we stressing over parallel circuits? Because as an electrical engineer, you will rarely deal with pure series loads.

1. **Domestic Wiring:** Your house is a giant parallel circuit. Every plug point provides 230V. When you plug in a fridge (RL load) and a heater (R load), you are adding parallel branches. The utility company needs to know the vector sum of these currents to size the transformer outside your house.
2. **Industrial Loads:** A factory might have 50 induction motors running in parallel. These are inductive loads that draw lagging current. The total current drawn from the grid is calculated exactly using the phasor method we just discussed.

### 4. Summary & Q&A (5 Minutes)

Let's recap the key takeaways for Unit 3, Topic 1:

- In parallel circuits, **Voltage is the Reference** vector because it is common to all branches.
- You cannot arithmetically add branch currents ( $I_T \neq I_1 + I_2$ ).
- You must use **Phasor Addition** to find the total current, accounting for the phase angles of different branches (Resistive current is horizontal, Inductive is downwards, Capacitive is upwards).

Common Student Doubt: "Sir, in series circuits, current was the reference. Why did it change?"

Answer: Because the reference is always whatever quantity is common throughout the circuit. In series, current is common. In parallel, voltage is common.

---

**Mentorship Note for Future Engineers:** Don't just memorize the phasor diagram for the exam. Master the concept of vector addition. Whether you become a power system engineer calculating load flows on a transmission network or a design engineer selecting circuit breakers for a building, you are essentially managing the vector sum of thousands of parallel currents. Understanding this foundation makes you a competent and safe engineer.

## Unit 3: Single Phase AC Parallel Circuits

### Topic 2: Terms related to AC parallel circuits:(a) Define term- admittance, conductance and susceptance (b) Draw admittance triangle

Duration: 60 Minutes

Hello everyone. Welcome back to AC Fundamentals.

#### 1. The Hook (5 Minutes)

Remember in the last lecture we realized that in parallel circuits, voltage is common, but currents split? We learned that to find the total impedance ( $Z_T$ ) of parallel branches, we have to use messy reciprocal formulas, like  $\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$

When dealing with complex numbers ( $R \pm jX$ ), doing this algebra is painful and prone to errors.

Engineers are practical people. If a mathematical method is too hard, we invent a new one. We asked ourselves: "Instead of measuring how much a circuit **opposes** current (Impedance), why don't we measure how easily a circuit **allows** current?"

Today, we are going to learn the "language of parallel circuits": Admittance.

#### 3. Core Concepts (40 Minutes)

##### The "Mirror World" of Impedance

If Impedance ( $Z$ ) is obstruction, its exact opposite is **Admittance**, denoted by the symbol  $Y$ .

**Definition:** Admittance ( $Y$ ) is the reciprocal of Impedance ( $Z$ ). It defines how easily a circuit admits the flow of current when voltage is applied.

**Formula:**  $Y = \frac{1}{Z} = \frac{1}{V}$

**Unit:** The unit is **Siemens (S)**. (Fun Fact: Historically, since it's the reverse of Ohm, the unit was spelled backward as "Mho"  $\Omega^{-1}$  with an upside-down omega symbol! You might still see this on old machine nameplates.)

Just as Impedance ( $Z$ ) has two parts (Resistance  $R$  and Reactance  $X$ ), Admittance ( $Y$ ) also has two components.

##### 1. Conductance ( $G$ ) – The Real Part

Conductance is the reciprocal of Resistance in a purely resistive circuit. It represents the ease with which the resistive part of the circuit allows current to pass.

- Symbol:  $G$
- Unit: Siemens (S)
- For a pure resistor:  $G = \frac{1}{R}$

##### 2. Susceptance ( $B$ ) – The Imaginary Part

Susceptance is the reciprocal of Reactance in a purely reactive circuit. It represents how easily the inductor or capacitor allows current to pass.

- Symbol: B
- Unit: Siemens (S)

**The Vital Twist (Pay Attention!):** Because reactance involves the j operator ( $Z_L = jX_L$  and  $Z_C = -jX_C$ ), taking the reciprocal flips the sign, because  $\frac{1}{j} = -j$ .

Therefore:

- **Inductive Susceptance ( $B_L$ ) is NEGATIVE:**  $B_L = -\frac{1}{X_L}$
- **Capacitive Susceptance ( $B_C$ ) is POSITIVE:**  $B_C = +\frac{1}{X_C}$

Make a note of this. This is the biggest mistake students make in exams. In Impedance, Inductive is positive (+j). In Admittance, Inductive is negative (-j).

### The Total Admittance Equation


Putting it together in complex form:  $Y = G \pm jB$  (Use +jB for capacitive circuits, -jB for inductive circuits).

### The Admittance Triangle

Just like the Impedance triangle, we can visualize these three quantities using a right-angled triangle. This is required by your syllabus.

**[VISUAL DESCRIPTION: The Admittance Triangle]** \*(Imagine a standard right-angled triangle.

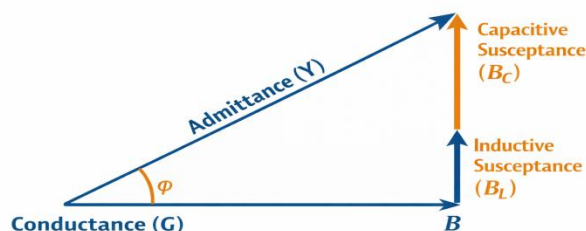1. The horizontal base represents **Conductance (G)**.
2. The vertical side represents **Susceptance (B)**. If it is inductive susceptance ( $B_L$ ), draw it pointing **downwards** from the right end of G. If it is capacitive susceptance ( $B_C$ ), draw it pointing **upwards**.
3. The hypotenuse connecting the origin to the tip of the vertical line represents the total **Admittance (Y)**.
4. The angle between G and Y is the power factor angle  $\phi$ .\*



From this triangle, we get the magnitude relationship using Pythagoras:  $Y = \sqrt{G^2 + B^2}$

### 3. Real-World Applications (10 Minutes)

Why do we force you to learn these new terms?

In the real world, electrical loads are connected in parallel. Imagine a factory with 50 different machines connected to the main supply busbar. If you want to calculate the total load on the supply, adding 50 complex impedances using the reciprocal formula  $\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} \dots$  is nearly impossible by hand.

However, if you convert each machine's impedance into admittance ( $Y_1, Y_2, \dots Y_{50}$ ), you can simply add them up:  $Y_{\text{Total}} = Y_1 + Y_2 + Y_3 + \dots + Y_{50}$

Power system engineers use admittance matrices constantly to model huge electrical grids because it turns complex division into simple addition.


#### 4. Summary & Q&A (5 Minutes)

##### Quick Recap:

1. **Admittance (Y):** The inverse of Impedance ( $1/Z$ ). Unit is Siemens (S).
2. **Conductance (G):** The inverse of Resistance (Real part).
3. **Susceptance (B):** The inverse of Reactance (Imaginary part).
4. **The Golden Rule:** Inductive Susceptance is negative ( $-jB_L$ ); Capacitive Susceptance is positive ( $+jB_C$ ).

**Typical Student Doubt:** Student: "Sir, why is G only  $1/R$  for a pure resistor? What if it's an R-L series branch?" Mentor: Excellent question. If you have an R-L series branch,  $Z = R + jX_L$ . The admittance is  $Y = \frac{1}{R + jX_L}$ . To find G and B, you must rationalize this by multiplying the top and bottom by the conjugate ( $R - jX_L$ ). In that case, G is NOT just  $1/R$ . We will solve a numerical on this in the next class.

---

 **Mentorship Note:** Mastering Admittance isn't just about passing Unit 3. It's about learning to look at a problem from a different perspective to make it easier. This is a core engineering skill. Furthermore, if you plan to study higher-level subjects like Power System Analysis or perform load-flow studies in the industry, the concept of Admittance is fundamental. You will use it for the rest of your career.

### Topic 3: Admittance method for solving AC parallel circuits

Duration: 60 Minutes

Reference: Unit 3, Topic 3

Hello everyone. Welcome back to AC Fundamentals. Today, we are going to unlock the true power of the concepts we learned in the last class.

#### 1. The Hook (5 Minutes)

Let's start with a question. Imagine you are a chef trying to fill a large pot with water. You have three different taps. Tap A has a wide opening and lets water flow easily. Tap B is thin and restricts flow. Tap C is somewhere in between.

If you open all three taps at once, how do you calculate the total rate at which the pot fills up? Do you add up how much each tap restricts the flow? No, that would be complicated. You simply add up how much each tap allows the water to flow.

In electrical circuits, "restriction" is **Impedance (Z)**. "Allowance" is **Admittance (Y)**.

When branches are connected in parallel, they are like those three taps opening into the same main pipe. Trying to find the total effect by adding impedances is like trying to calculate water flow by adding pipe restrictions—it's messy and hard.

Today, we will learn the **Admittance Method**, which is the "chef's secret" for solving parallel circuits easily by just adding up the "allowances."

#### 2. Core Concepts (40 Minutes)

##### The Golden Rule of Parallel Admittance

The beauty of the Admittance method lies in one simple rule. For any number of parallel branches, the total admittance ( $Y_T$ ) is the simple vector sum of the individual branch admittances.

$$Y_T = Y_1 + Y_2 + Y_3 + \dots$$

This is much simpler than the impedance formula:  $\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$

##### Step-by-Step Procedure to Solve a Problem

Let's take a practical example. Suppose we have a circuit with two branches in parallel across a voltage source  $V$ .

- **Branch 1:** A pure resistor ( $R$ ).
- **Branch 2:** A pure inductor with inductive reactance ( $X_L$ ).

Here is the standard procedure you should follow to solve this using the Admittance method.

##### Step 1: Find the Admittance of Each Branch in Rectangular Form ( $G \pm jB$ )

- **For Branch 1 (Resistor  $R$ ):**

The impedance is  $Z_1 = R$ . The admittance is  $Y_1 = \frac{1}{Z_1} = \frac{1}{R}$ . Since there is no reactive part,  $Y_1 = G_1 + j0$ , where  $G_1 = \frac{1}{R}$  Siemens.

- **For Branch 2 (Inductor  $X_L$ ):**

The impedance is  $Z_2 = jX_L$ . The admittance is  $Y_2 = \frac{1}{Z_2} = \frac{1}{jX_L}$ . Crucial Step: Remember that  $\frac{1}{j} = -j$ . So,  $Y_2 = -j\left(\frac{1}{X_L}\right)$ . This is in the form  $0 - jB_L$ , where  $B_L = \frac{1}{X_L}$  Siemens.

### Step 2: Add the Admittances Together

Now, we just add the real parts and the imaginary parts separately.  $Y_T = Y_1 + Y_2$   
 $Y_T = (G_1 + j0) + (0 - jB_L)$   
 $Y_T = G_1 - jB_L$

This gives you the total conductance and total susceptance of the entire circuit.

### Step 3: Convert Total Admittance to Polar Form

To find total current, we need the magnitude and angle of  $Y_T$ .

- Magnitude:  $|Y_T| = \sqrt{G_T^2 + B_T^2}$
- Angle:  $\theta_Y = \tan^{-1}\left(\frac{B_T}{G_T}\right)$

So,  $Y_T = |Y_T| \angle \theta_Y$ .

### Step 4: Calculate Total Current

From Ohm's law for AC,  $I = V/Z$ . Since  $Y = 1/Z$ , this becomes:  $I_{Total} = V \times Y_T$

Using polar form makes multiplication easy:  $I_{Total} = (V \angle 0^\circ) \times (|Y_T| \angle \theta_Y)$   
 $I_{Total} = (V \cdot |Y_T|) \angle (0^\circ + \theta_Y)$

Note: The angle of the current  $\theta_Y$  is also the negative of the power factor angle. If  $\theta_Y$  is negative (inductive circuit), current lags voltage.

**[VISUAL DESCRIPTION: Block Diagram of Procedure]** (Draw a flowchart with four boxes in a sequence. Box 1: "Calculate  $Y = G \pm jB$  for each branch." -> Box 2: "Add all  $Y$ 's:  $Y_T = \Sigma G \pm j\Sigma B$ ." -> Box 3: "Convert  $Y_T$  to Polar Form:  $|Y_T| \angle \theta$ ." -> Box 4: "Calculate Current:  $I_T = V \times Y_T$ ." This visualizes the entire process at a glance.)

## 3. Real-World Applications (10 Minutes)

Where is this used? Everywhere in power distribution.

Consider a substation that supplies power to a residential colony. Every house is a parallel branch. House 1 might have a high resistive load (heaters, geysers), so it has a high conductance ( $G$ ). House 2 might have many air conditioners (inductive motors), so it has a high inductive susceptance ( $B_L$ ).

The substation engineer doesn't calculate the impedance of every house. They model the entire colony as a total admittance  $Y_{Colony} = \Sigma G_{Houses} - j\Sigma B_{Houses}$ . This single complex number tells them exactly how much total current the colony will draw from the grid and what the overall power factor will be. This is essential for sizing transformers and cables.

## 4. Summary & Q&A (5 Minutes)


### Quick Recap:

1. The Admittance Method is the easiest way to solve parallel circuits.
2. The rule is simple: **Total Admittance = Sum of Individual Admittances** ( $Y_T = Y_1 + Y_2 + \dots$ ).
3. Always convert each branch's impedance to admittance form ( $G \pm jB$ ) first.

4. Remember the sign flip: Inductive  $Z$  is  $+j$ , but Inductive  $Y$  is  $-j$ .
5. Total Current is  $I_T = V \times Y_T$ .

**Typical Student Doubt:** Student: "Sir, can we use this method if one branch has a resistor and inductor in series, and that is in parallel with a capacitor?" Mentor: Absolutely! That's the power of this method. First, find the impedance of the series branch ( $Z_1 = R + jX_L$ ). Then find its admittance ( $Y_1 = 1/Z_1$ ). Then find the admittance of the capacitor branch ( $Y_2 = 1/(-jX_C) = j/X_C$ ). Finally, just add them:  $Y_T = Y_1 + Y_2$ . It works for any combination.

---

 **Mentorship Note:** Don't be intimidated by the math. The Admittance Method is just a structured way of organizing information. Once you get comfortable with converting  $Z$  to  $Y$  (especially handling the  $j$ 's), complex parallel circuit problems that look impossible become a simple game of addition. Practice this conversion, and you will find this unit to be one of the most scoring ones in the exam.

## Topic 4: Complex algebra method for solving AC parallel circuits.

Duration: 60 Minutes

Reference: Unit 3, Topic 4

Hello future engineers! Welcome back to our journey through AC circuits.

### 1. The Hook (5 Minutes)

Remember the Admittance Method we just learned? It was a neat trick, wasn't it? Converting everything to admittance made solving parallel circuits a breeze—just simple addition.

But sometimes, you don't want to convert everything. What if you have a circuit that is a mix of series and parallel parts, and you want a single, powerful tool that can handle everything without changing your perspective?

Imagine you have a universal wrench that fits every single bolt in a machine, no matter the size or shape. That would be incredibly convenient, right?

Today, we're going to master that universal wrench of electrical engineering: The **Complex Algebra Method** using impedances directly. It's the most robust mathematical tool you'll ever learn for AC circuits.

### 2. Core Concepts (40 Minutes)

#### The Power of the 'j' Operator

The core of this method lies in using complex numbers ( $a \pm jb$ ) to represent impedance ( $Z = R \pm jX$ ). This isn't just abstract math; it's a way to encode both the magnitude of opposition and the phase shift it causes into a single number.

- Resistors ( $R$ ) are real numbers.
- Inductors ( $X_L$ ) are positive imaginary numbers ( $+jX_L$ ).
- Capacitors ( $X_C$ ) are negative imaginary numbers ( $-jX_C$ ).
- 

#### The Parallel Impedance Formula

Just like in DC circuits, when two resistors  $R_1$  and  $R_2$  are in parallel, the equivalent resistance is  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$ .

In AC circuits, we use the exact same formula, but with complex impedances:  $Z_{Total} = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$

This looks simple, but it involves multiplying and adding complex numbers.

#### Step-by-Step Procedure

Let's solve the same R || L circuit from the last class, but this time using complex impedance.

- **Branch 1:** Resistor  $R$ . So,  $Z_1 = R + j0$ .
- **Branch 2:** Inductor with reactance  $X_L$ . So,  $Z_2 = 0 + jX_L$ .

**Step 1: Calculate the Numerator (Product  $Z_1 \times Z_2$ )** Numerator =  $(R) \times (jX_L) = j(R \cdot X_L)$ . Tip: Multiplication is often easier in polar form, but for simple cases like this, rectangular is fine.

**Step 2: Calculate the Denominator (Sum  $Z_1 + Z_2$ )** Denominator =  $(R + j0) + (0 + jX_L) = R + jX_L$ .

**Step 3: Perform the Division to find  $Z_{\text{Total}}$**   $Z_{\text{Total}} = \frac{j(R \cdot X_L)}{R + jX_L}$

To divide, we must convert both numerator and denominator to **polar form**.

- Numerator:  $j(R \cdot X_L)$  has a magnitude of  $R \cdot X_L$  at an angle of  $+90^\circ$ . So,  $(R \cdot X_L) \angle 90^\circ$ .
- Denominator:  $R + jX_L$  has a magnitude of  $\sqrt{R^2 + X_L^2}$  at an angle of  $\tan^{-1}(X_L/R)$ . Let's call this  $|Z_{\text{den}}| \angle \theta_{\text{den}}$ .

Now divide magnitudes and subtract angles:  $Z_{\text{Total}} = \frac{R \cdot X_L}{|Z_{\text{den}}|} \angle (90^\circ - \theta_{\text{den}})$

This gives you the total impedance in polar form.

**Step 4: Calculate Total Current** Finally, use Ohm's Law:  $I_{\text{Total}} = \frac{V}{Z_{\text{Total}}}$ . Again, perform this division using polar forms.

**[VISUAL DESCRIPTION: Flowchart of Complex Algebra Method]** (Draw a flowchart: Box 1 "Write Z for each branch in Rectangular Form ( $R \pm jX$ )" -> Box 2 "Calculate Sum ( $Z_1 + Z_2$ ) in Rectangular Form" -> Box 3 "Calculate Product ( $Z_1 \times Z_2$ ). Convert to Polar." -> Box 4 "Convert Sum to Polar Form." -> Box 5 "Divide Product by Sum to find  $Z_{\text{Total}}$  in Polar Form." -> Box 6 "Calculate  $I_T = V/Z_{\text{Total}}$  using Polar Division.")

### 3. Real-World Applications (10 Minutes)

Why learn this harder method when Admittance was easier? Because real-world circuits are rarely simple parallel branches.

Consider an industrial induction motor. Its equivalent circuit is not just a resistor and inductor in parallel. It's a complex combination of series and parallel elements representing the stator winding, rotor winding, and magnetic core. To analyze such a motor, or a long transmission line with capacitive effects, you cannot just add admittances. You need the full power of complex algebra to combine series parts, then parallel parts, step-by-step, until you get one total impedance.

### 4. Summary & Q&A (5 Minutes)

#### Quick Recap:

1. The complex algebra method uses impedances ( $Z = R \pm jX$ ) directly.
2. The formula for two parallel branches is  $Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$ .
3. The Golden Rule for Calculation: **Add/Subtract in Rectangular Form. Multiply/Divide in Polar Form.**

**Typical Student Doubt:** Student: "Sir, my scientific calculator can do complex numbers. Can I just type it all in?" Mentor: Yes, you absolutely should learn to use your calculator's complex mode! It will save you enormous amounts of time in the exam. However, you must understand the process on paper first so you can catch errors if your finger slips on the calculator.

---

**Mentorship Note:** Proficiency in complex algebra is what separates a technician from an engineer. It's the mathematical language of AC power. Don't shy away from it. The more you practice converting between rectangular and polar forms, the more intuitive it becomes. This skill is your passport to advanced subjects like Control Systems, Signal Processing, and Power System Protection. Master it now, and future you will be grateful.

## Topic: Resonance condition and resonant frequency in parallel AC circuits

Duration: 60 Minutes

Reference: Unit 3, Topic 5

Hello future engineers! Welcome back to AC Fundamentals.

### 1. The Hook (5 Minutes)

Think back to Unit 2 when we studied **Series Resonance**. Do you remember the magic that happened there? At a specific frequency, the inductive effect ( $X_L$ ) perfectly canceled the capacitive effect ( $X_C$ ). The result? The total impedance became tiny (just  $R$ ), and the current became huge. It was like opening a floodgate for current at that one specific frequency.

Now, here is the thought-provoking question for today: What if we take that same inductor and capacitor and connect them in **parallel** instead of series?

Does the same thing happen? Does the current maximize? Or does something totally opposite occur? Today, we are going to investigate **Parallel Resonance**, a concept crucial for tuning radios and filtering signals[cite: 161, 183].

### 2. Core Concepts (40 Minutes)

#### The Practical Parallel Circuit

In the real world, inductors always have some internal resistance. So, a practical parallel resonant circuit usually looks like this:

**[VISUAL DESCRIPTION: Circuit Diagram]** (Imagine an AC voltage source  $V$  on the left. Connected in parallel across it are two branches. **Branch 1** contains a Resistor  $R$  and an Inductor  $L$  in series (representing a real coil). **Branch 2** contains only a pure Capacitor  $C$ . The total current  $I$  splits into  $I_{coil}$  going through Branch 1 and  $I_C$  going through Branch 2.)

#### The Resonance Condition

Just like in series circuits, resonance in a parallel circuit occurs when the entire circuit behaves like a pure resistor. This means the total voltage  $V$  and total current  $I$  are exactly **in phase**. The power factor is unity (1).

How does this happen?

- The capacitor draws a leading current ( $I_C$ ).
- The coil draws a lagging current ( $I_{coil}$ ).

For the total current to be in phase with voltage, the “upward” leading effect of the capacitor must exactly cancel the “downward” lagging effect of the coil’s inductance.

**[VISUAL DESCRIPTION: Phasor Diagram at Resonance]** (Draw Voltage  $V$  as the horizontal reference vector at  $0^\circ$ . Draw the capacitor current  $I_C$  pointing straight UP at  $90^\circ$ . Draw the coil current  $I_{coil}$  lagging  $V$  by an angle  $\phi_L$ . Now, resolve  $I_{coil}$  into two parts: a horizontal active component ( $I_{coil}\cos\phi_L$ ) and a vertical reactive component pointing DOWN ( $I_{coil}\sin\phi_L$ .)

**The condition for resonance is that the upward vertical component equals the downward vertical component:**  $I_C = I_{coil}\sin\phi_L$

When this happens, the reactive currents cancel out. The only current left flowing from the source is the horizontal component:  $I_{Total} = I_{coil}\cos\phi_L$ .

## The Resonant Frequency Formula

By substituting the standard formulas for these currents ( $I_C = V/X_C$ ,  $I_{coil} = V/Z_{coil}$ , etc.) into the condition above and doing some algebra, we arrive at the formula for the resonant frequency ( $f_r$ ) for this practical circuit:

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Note: If the coil had no resistance ( $R = 0$ ), this formula simplifies back to the familiar  $\frac{1}{2\pi\sqrt{LC}}$ .

## The Great Reversal: Current at Resonance

Here is the main difference from series resonance: At parallel resonance, because the reactive branch currents cancel each other out internally, the **total current drawn from the source is at its MINIMUM**.

Consequently, the total **Impedance is at its MAXIMUM**. This maximum impedance at resonance is often called **Dynamic Impedance**.

## 3. Real-World Applications (10 Minutes)

Why would we want a circuit that blocks current at a specific frequency?

1. **Rejector Circuits:** Sometimes you have an interfering signal at a specific frequency (like humming noise) that you want to block. A parallel LC circuit tuned to that noise frequency will act like a brick wall, stopping that frequency while letting others pass.
2. **Radio Tuning (Tank Circuits):** In the local oscillator of a radio receiver, a parallel LC circuit (called a tank circuit) is used to generate a precise frequency while drawing very little power from the battery because the total current is minimum.

## 4. Summary & Q&A (5 Minutes)

### Quick Recap:

- Parallel resonance occurs when the leading reactive current component ( $I_C$ ) equals the lagging reactive current component ( $I_{coil}\sin\phi_L$ ).
- At resonance, the power factor is **Unity**.
- At resonance, Total Impedance is **Maximum**, and Total Source Current is **Minimum** (the opposite of series resonance).

**Typical Student Doubt:** Student: "Sir, if the source current is minimum, does that mean the currents inside the L and C branches are also small?" Mentor: Excellent question! No. The currents circulating inside the L and C branches can be huge—much larger than the source current. They are just bouncing back and forth between the inductor and capacitor, canceling each other out from the source's perspective. This is called **current magnification**.

---

**Mentorship Note:** Understanding resonance is your gateway to the field of **Communication Engineering**. Every wireless device, from your mobile phone to Wi-Fi routers, relies entirely on resonant circuits to select the right frequency and reject others. Mastering this concept in Diploma will give you a significant head start if you pursue a degree in Electronics or Telecommunication later.

## Topic: Comparison between series and parallel resonance

Duration: 60 Minutes

Reference: Unit 3, Topic 6;

Hello future engineers! Welcome back to our final session on AC Parallel Circuits.

### 1. The Hook: The Tale of Two Gatekeepers (5 Minutes)

We have spent Unit 2 mastering **Series Resonance** and the last few lectures of Unit 3 understanding **Parallel Resonance**.

Imagine them as two very different gatekeepers at a music concert. The **Series** gatekeeper loves one specific note (frequency). When that note plays, he throws the gates wide open, letting maximum crowd (current) rush in with almost zero resistance. The **Parallel** gatekeeper hates that specific note. When that note plays, he slams the gates shut, blocking the entrance almost completely, offering maximum resistance.

Today, we are going to put these two “twins” side-by-side. They look similar—both use Inductors (L) and Capacitors (C)—but their behavior is almost an exact mirror image. Understanding this contrast is crucial for the upcoming exam and for understanding real-world electronics.

### 2. Core Concepts: The Showdown (40 Minutes)

Let’s compare them step-by-step. I want you to visualize a comparison table in your notebooks.

#### A. The Main Characteristic: Impedance ( $Z$ )

**Series Resonance:** Remember that  $X_L$  cancels out  $X_C$ . All that is left is resistance  $R$ . Since the reactive part is gone, the total opposition is at its lowest point.

- Series = Minimum Impedance ( $Z = R$ )

**Parallel Resonance:** As we saw last class, the branch currents cancel out. The circuit refuses to draw reactive current from the source. The overall circuit acts like a massive obstacle at that frequency.

- Parallel = Maximum Impedance (also called Dynamic Impedance)


#### B. The Resulting Current ( $I$ )

By Ohm’s Law, Current is inversely proportional to Impedance ( $I = V/Z$ ). This leads to the most obvious difference.

**[VISUAL DESCRIPTION: Resonance Curves Graph]** (Imagine two graphs side-by-side with Frequency on the X-axis and Current on the Y-axis. **Graph 1 (Series):** Shows a curve starting low, rising to a tall, sharp mountain peak at the resonant frequency ( $f_r$ ), and dropping again. **Graph 2 (Parallel):** Shows a curve starting high, dipping down into a deep valley at resonant frequency ( $f_r$ ), and rising again.)

- **Series:** Since  $Z$  is minimum, the Source Current is **MAXIMUM**.
- **Parallel:** Since  $Z$  is maximum, the Source Current is **MINIMUM**.

## Resonance Curves

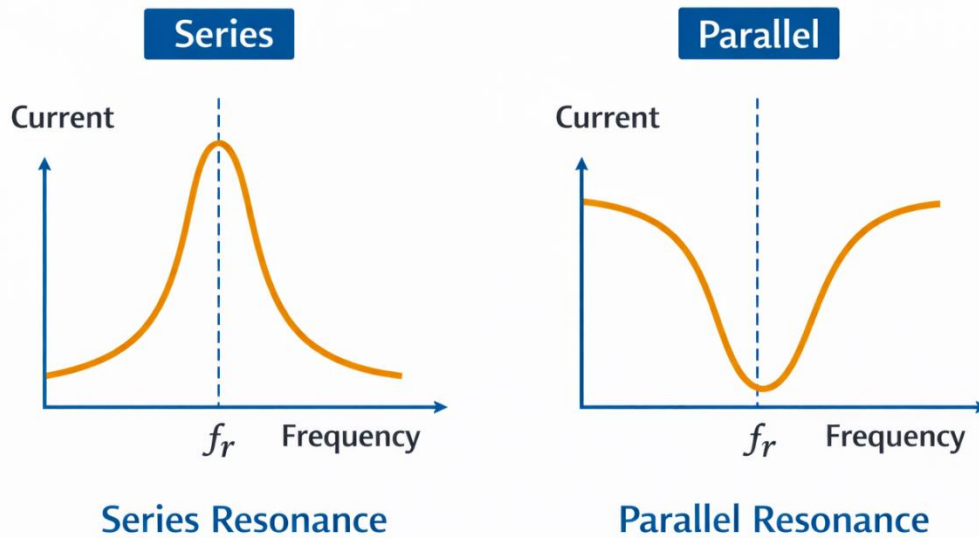

### C. The “Magnification” Phenomenon (Fun Fact!)

This is the coolest difference. Even though they both have unity power factor, they create different types of “electrical stress.”

In a **Series** circuit, because the current is huge, the voltage drop across the inductor ( $V_L = I \times X_L$ ) and capacitor ( $V_C = I \times X_C$ ) can become massive—much larger than the supply voltage!

- Series = Voltage Magnification

In a **Parallel** circuit, the current from the source is tiny. However, the current circulating inside the loop between the capacitor and inductor is huge, bouncing back and forth.

- Parallel = Current Magnification

### 3. Real-World Applications (10 Minutes)

Why do engineers need both types? Because sometimes you want to invite a frequency in, and sometimes you want to kick it out.

1. **The Acceptor Circuit (Series):** Because series resonance allows maximum current at one frequency, it “accepts” that signal. This is used in radio tuning to pick one station out of the air while ignoring others.
2. **The Rejector Circuit (Parallel):** Because parallel resonance blocks current at one frequency, it “rejects” that signal. This is used in “wave traps” in power systems to block unwanted high-frequency communication signals from entering a substation transformer.

#### 4. Summary & Q&A (5 Minutes)

##### Quick Recap Table:

Feature	Series Resonance	Parallel Resonance
Impedance at $f_r$	Minimum ( $R$ )	Maximum
Current at $f_r$	Maximum	Minimum
Magnification	Voltage Magnifier	Current Magnifier
Application Name	Acceptor Circuit	Rejector Circuit

**Typical Student Doubt:** Student: “Sir, is the resonant frequency formula the same for both?”

Mentor: Good catch. For an ideal circuit (no resistance in the coil), yes, both are  $f_r = \frac{1}{2\pi\sqrt{LC}}$ . But in a practical parallel circuit where the coil has resistance, the formula changes slightly, as we derived last lecture.

---

**Mentorship Note:** As an engineer, your value lies not just in knowing how a circuit works, but in knowing which circuit to choose for a specific job. The ability to compare trade-offs—like choosing between an acceptor (series) or a rejector (parallel) filter—is a fundamental design skill. Master this comparison, and you are thinking like a design engineer.

## Topic: Numerical based on AC parallel circuits and parallel resonance

Duration: 60 Minutes

Reference: Unit 3, Topic 7;

Hello future engineers. Welcome to the “dojo.”

### 1. The Hook (5 Minutes)

For the past six lectures, we have been learning the “rules” of parallel AC circuits—phasors, admittance, complex algebra, and resonance. Today, we stop just talking about the rules and start playing the game.

Many students find numericals intimidating. They see  $j$ 's and angles and panic. But I want you to change your perspective. A numerical problem is just a puzzle waiting to be solved. It's the moment where the abstract theory becomes concrete reality. When you calculate a number on your page, and it matches the reality of what a circuit actually does, it's a fantastic feeling of competency.

Today, we are going to take a practical circuit problem and dismantle it, step-by-step, using the tools we've sharpened in this unit. Grab your calculators!

### 2. Core Concepts: The Strategy of Solving (40 Minutes)

We will solve a classic “practical parallel circuit” problem.

**[VISUAL DESCRIPTION: The Problem Circuit]** (Imagine an AC voltage source,  $V = 230\angle 0^\circ$  Volts, 50 Hz. Connected in parallel across it are two branches: **Branch 1 (The Coil)**: A resistor of  $10\Omega$  in series with an inductor of  $0.05H$ . **Branch 2 (The Capacitor)**: A pure capacitor of  $100\mu F$ . Goal: Find Total Current, Overall Power Factor, and draw the phasor diagram.)

#### The “Admittance Attack” Strategy

While you can use complex impedance ( $Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$ ), for parallel circuits, the **Admittance Method** is usually cleaner and less prone to calculator errors.

**Step 1: Prepare the Ingredients (Find  $X_L$  and  $X_C$ )** Before anything else, convert  $L$  and  $C$  into Ohms.

- $X_L = 2\pi fL = 2 \times \pi \times 50 \times 0.05 \approx 15.7\Omega$
- $X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times \pi \times 50 \times 100 \times 10^{-6}} \approx 31.8\Omega$

**Step 2: Define Branch Impedances in Complex Form ( $Z = R \pm jX$ )**

- Branch 1 (Coil):  $Z_1 = 10 + j15.7\Omega$
- Branch 2 (Capacitor):  $Z_2 = 0 - j31.8\Omega$

**Step 3: Convert Impedances to Admittances ( $Y = 1/Z$ )** This is the crucial step. Use your calculator's complex mode.

- $Y_1 = \frac{1}{10 + j15.7} = 0.0288 - j0.0452$  Siemens
- $Y_2 = \frac{1}{-j31.8} = 0 + j0.0314$  Siemens (Remember,  $1/-j = +j$ )

**Step 4: Add Admittances to find Total Admittance ( $Y_T$ )** Now, simply add the real parts and the imaginary parts.

- $Y_T = Y_1 + Y_2$
- $Y_T = (0.0288 + 0) + j(-0.0452 + 0.0314)$
- $Y_T = 0.0288 - j0.0138$  Siemens

**Step 5: Calculate Total Current ( $I_T = V \times Y_T$ )**

- $I_T = (230\angle 0^\circ) \times (0.0288 - j0.0138)$
- $I_T = 6.624 - j3.174$  Amps
- Convert to polar form for the final answer:  $I_T = 7.35\angle -25.6^\circ$  Amps

**Step 6: Find Power Factor** The angle of the total current is  $-25.6^\circ$ . Since it's negative, the current is lagging voltage.

- Power Factor =  $\cos(25.6^\circ) = 0.90$  Lagging.

We have successfully analyzed the entire circuit!

### 3. Real-World Applications (10 Minutes)

Why do you need to be this precise?

Consider an industrial plant. The utility company penalizes them if their power factor is too low (too lagging). The plant engineer must calculate exactly how much capacitance to add in parallel to improve that power factor.

They take the existing plant load (which looks like our Branch 1 coil), determine its lagging var component, and calculate the exact capacitor bank size (Branch 2) needed to supply leading vars to cancel it out, bringing the total current angle closer to zero. This numerical we just did is the basis of **Power Factor Correction**, a massive industry.

### 4. Summary & Q&A (5 Minutes)

**Quick Recap:** The most robust strategy for parallel numericals is:

1. Convert  $L$  and  $C$  to  $X_L$  and  $X_C$ .
2. Write  $Z$  for each branch in rectangular form.
3. Convert every  $Z$  to  $Y$  (Admittance).
4. Add all  $Y$ 's together to get  $Y_{Total}$ .
5. Multiply  $V \times Y_{Total}$  to get Total Current.

**Typical Student Doubt:** Student: "Sir, my calculator gave me a different sign for the imaginary part of  $Y_1$ ." Mentor: Check your input. Remember that  $Y_1 = \frac{1}{R+jX_L}$ . To solve this by hand, you must multiply the numerator and denominator by the conjugate ( $R - jX_L$ ). This results in a positive real part ( $G$ ) and a negative imaginary part ( $B_L$ ). Trust the process; inductive admittance always has a negative  $j$  component.

---

**Mentorship Note:** Mastering these numericals isn't just about getting marks in the final exam. It builds **attention to detail**. In the field, a misplaced decimal point or a wrong sign in a calculation can lead to undersized cables or blown fuses. Treat every calculation step with respect. Disciplined calculation is the mark of a professional engineer.

## Digital Resource Library

### Unit 3: Single Phase AC Parallel Circuits

#### 1. AI Tools & Digital Learning Tools

These tools are selected to help you move beyond static textbook diagrams and perform complex calculations with confidence.

Tool Name & Type	Purpose / Use-case for Unit 3	How it helps in learning AC Parallel Circuits
<b>1. Falstad Circuit Simulator</b> (Web-based Circuit Simulator)	<b>Visualization &amp; Simulation:</b> Ideally suited for visualizing how current splits in parallel branches.	You can build an R-L-C parallel circuit in minutes. It shows animated “current dots” moving faster for higher currents and allows you to see real-time graphs of voltage vs. branch currents, proving that they are out of phase.
<b>2. WolframAlpha</b> (Computational Knowledge Engine / AI Math Tool)	<b>Problem-Solving Aid &amp; Verification:</b> The ultimate tool for handling complex number algebra ( $a + jb$ or $r\angle\theta$ ).	Parallel circuit problems require messy complex division (e.g., calculating total impedance $Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$ ). You can type “ $(10+20i) * (5-10i) / ((10+20i) + (5-10i))$ ” into WolframAlpha to verify your manual calculations step-by-step.
<b>3. Virtual Labs (vlab.co.in)</b> (MHRD Govt. of India Initiative)	<b>Virtual Experimentation:</b> Performing standard electrical lab experiments digitally.	Search for “Electrical Circuit Analysis Lab”. It often contains experiments related to RLC series and parallel resonance, allowing you to take readings and plot resonance curves without being physically in the lab.
<b>4. AI Chat Assistants</b> (e.g., ChatGPT / Claude - Free Versions)	<b>Concept Explanation &amp; Practice Generation:</b> Acting as an on-demand tutor for summarizing concepts or creating new practice problems.	<b>Prompt Idea:</b> “Act as a Diploma Electrical tutor. Explain the difference between Series and Parallel Resonance to a student who is confused. Use a simple analogy.” OR “Generate a practice numerical problem for a parallel RL circuit connected to a 230V source, and provide the step-by-step solution using the admittance method.”

## 2. Video Learning Repository

This repository contains highly recommended video resources tailored for Diploma-level understanding. They are selected for clarity, focus on basics, and exam-oriented problem solving.

**How to use:** Copy the exact Search Keywords into the YouTube search bar to find the recommended video.

Topic Name	Recommended Channel / Lecturer	Search Keywords for YouTube
<b>Introduction to Parallel AC Circuits &amp; Phasors</b>	Neso Academy	Neso Academy Parallel AC Circuits Phasor Diagram
<b>Concept of Admittance, Conductance, Susceptance</b>	Ekeeda (Diploma Section)	Ekeeda admittance conductance susceptance ac circuits
<b>Solving Parallel Circuits (Admittance Method)</b>	Electrical Engineering Videos (Suitable for Diploma)	AC Parallel Circuit using Admittance Method numerical
<b>Solving Parallel Circuits (Complex Algebra Method)</b>	Neso Academy	Neso Academy AC Parallel Circuit Problems Complex Numbers
<b>Parallel Resonance (Concept &amp; Conditions)</b>	CircuitGlobe	CircuitGlobe Parallel Resonance in RLC Circuit Explained
<b>Comparison: Series vs. Parallel Resonance</b>	Last moment tuitions	Difference between Series and Parallel Resonance Last moment tuitions
<b>Complete Unit Revision (Marathon/One-Shot)</b>	Varies based on regional language preference	Suggested search: "AC Parallel Circuits Diploma Engineering one shot"

---

**Curator's Note for Students:** Don't just watch the videos passively. When watching the numerical solution videos (like those from Neso Academy), pause the video before the instructor solves it, try it yourself using your calculator, and then watch the solution to check your steps. Use the Falstad simulator to build the circuit you just solved to see if reality matches your math! Happy learning!

## Mastery Check: Single Phase AC Parallel Circuits

### 1. Key Definitions / Glossary

**Objective:** Master the technical vocabulary required for Unit 3 exams and viva-voce interactions. These terms represent the core content of the syllabus.

1. **Parallel AC Circuit:** A circuit where multiple components (R, L, C) are connected across the same voltage source, resulting in the same voltage across each branch but different currents.
2. **Phasor Sum:** The vector addition of individual branch currents to find the total supply current, as arithmetic addition is not valid in AC circuits.
3. **Admittance ( $Y$ ):** The reciprocal of Impedance ( $Z$ ), representing the ease with which alternating current flows in a circuit. Unit: Siemens ( $S$ ) or Mho ( $\mathcal{U}$ ).
4. **Conductance ( $G$ ):** The real (resistive) part of admittance, representing the ability of the purely resistive element to conduct current. Unit: Siemens ( $S$ ).
5. **Susceptance ( $B$ ):** The imaginary (reactive) part of admittance, representing the ability of the inductive or capacitive element to pass current. Unit: Siemens ( $S$ ).
6. **Admittance Triangle:** A right-angled triangle representing the vector relationship between Conductance ( $G$ ), Susceptance ( $B$ ), and Admittance ( $Y$ ).
7. **Inductive Susceptance ( $B_L$ ):** The reciprocal of inductive reactance, assigned a negative sign in complex algebra math ( $-jB_L$ ).
8. **Capacitive Susceptance ( $B_C$ ):** The reciprocal of capacitive reactance, assigned a positive sign in complex algebra math ( $+jB_C$ ).
9. **Parallel Resonance:** A condition in a parallel R-L-C circuit where the inductive susceptance equals capacitive susceptance, resulting in Unity Power Factor.
10. **Resonant Frequency ( $f_r$ ):** The specific frequency at which the parallel circuit behaves like a pure resistor and the total impedance is maximum.
11. **Dynamic Impedance:** The equivalent resistance of a parallel circuit at resonance; it is the maximum possible impedance the circuit can offer.
12. **Rejector Circuit:** Another name for a parallel resonant circuit, as it offers maximum impedance (rejects current) at the resonant frequency.
13. **Current Magnification:** The phenomenon in parallel resonance where the circulating current within the L-C branches is much larger than the supply current.
14. **Active Component of Current:** The component of the total current that is in phase with the applied voltage (usually  $I\cos\phi$ ).
15. **Reactive Component of Current:** The component of the total current that is  $90^\circ$  out of phase with the applied voltage (usually  $I\sin\phi$ ).

---

### 2. FAQ & Assessment Section

#### A. Multiple Choice Questions (MCQs)

**Context:** These questions test the syllabus topics: Phasor methods, Admittance methods, and Parallel Resonance.

**1. In a parallel AC circuit, which quantity remains the same across all branches?** A) Current B) Voltage C) Power Factor D) Impedance

**2. The unit of Admittance is:** A) Ohm ( $\Omega$ ) B) Henry ( $H$ ) C) Siemens ( $S$ ) D) Farad ( $F$ )

**3. Mathematical relation between Admittance ( $Y$ ) and Impedance ( $Z$ ) is:** A)  $Y = Z$  B)  $Y = Z^2$  C)  $Y = 1/Z$  D)  $Y = 1/Z^2$

**4. Conductance ( $G$ ) in an AC circuit is given by:** A)  $R/Z$  B)  $R/Z^2$  C)  $X/Z$  D)  $Z/R$

**5. In an admittance triangle, the hypotenuse represents:** A) Conductance B) Susceptance C) Admittance D) Reactance

**6. If a parallel circuit has a Resistance ( $R$ ) and Inductance ( $L$ ), the current in the inductor:** A) Lags the voltage by  $90^\circ$  B) Leads the voltage by  $90^\circ$  C) Is in phase with voltage D) Lags the voltage by  $45^\circ$

**7. The total current in a parallel RC circuit is calculated using:** A)  $I = I_R + I_C$  (Arithmetic sum) B)  $I = \sqrt{I_R^2 + I_C^2}$  (Phasor sum) C)  $I = I_R - I_C$  D)  $I = (I_R + I_C)/2$

**8. The reciprocal of Reactance is called:** A) Conductance B) Admittance C) Susceptance D) Impedance

**9. In a parallel R-L-C circuit, if inductive susceptance is greater than capacitive susceptance, the circuit behaves as:** A) Inductive B) Capacitive C) Resistive D) Resonant

**10. At parallel resonance, the power factor of the circuit is:** A) Zero B) 0.5 Lagging C) Unity (1) D) 0.8 Leading

**11. The impedance of a parallel L-C circuit at resonance is:** A) Minimum B) Maximum C) Zero D) Infinite (theoretically)

**12. Parallel resonance is also known as:** A) Voltage resonance B) Current resonance C) Series resonance D) Power resonance

**13. In a parallel AC circuit, the total admittance  $Y$  in complex form is written as:** A)  $Y = G + jB$  B)  $Y = R + jX$  C)  $Y = G - R$  D)  $Y = Z + jG$

**14. If a circuit has a Conductance of 0.06 S and Susceptance of 0.08 S, the Admittance is:** A) 0.14 S B) 0.02 S C) 0.1 S D) 0.48 S

**15. The line current in a parallel resonant circuit is:** A) Maximum B) Minimum C) Infinite D) Equal to branch currents

**16. Which method is most convenient for solving parallel AC circuits?** A) Impedance method B) Admittance method C) KVL method D) Loop analysis

**17. For a pure capacitor, the conductance ( $G$ ) is:** A) 1 B)  $\infty$  C) 0 D)  $C$

**18. The dynamic impedance of a parallel tank circuit is given by:** A)  $L/(C \cdot R)$  B)  $C/(L \cdot R)$  C)  $R/(L \cdot C)$  D)  $L \cdot C \cdot R$

**19. Why is a parallel resonant circuit called a "Rejactor Circuit"?** A) It rejects high voltage B) It rejects signals at resonant frequency (high impedance) C) It rejects power D) It rejects DC current

**20. Comparing series and parallel resonance, series resonance produces:** A) Current Magnification B) Voltage Magnification C) Impedance Magnification D) Power Magnification

## B. Short Answer / Viva Questions

**Context:** These questions assess reasoning and the “Analyze” (N) or “Evaluate” (E) levels of Bloom’s Taxonomy mentioned in the syllabus.

- 1. Explain the “Phasor Method” for parallel circuits.**
  - Hint: Describe how currents are split into active ( $I\cos\phi$ ) and reactive ( $I\sin\phi$ ) components and added vectorially because they are not in phase.
- 2. Differentiate between Admittance ( $Y$ ) and Impedance ( $Z$ ).**
  - Hint: Focus on definition ( $Z = V/I$  vs  $Y = I/V$ ), units (Ohm vs Mho), and why  $Y$  is preferred for parallel connections.
- 3. Define Susceptance. How do Inductive and Capacitive Susceptance differ in calculation?**
  - Hint: Susceptance is the imaginary part of admittance. Mention that  $B_L = 1/X_L$  (treated as negative  $j$ ) and  $B_C = 1/X_C$  (treated as positive  $j$ ).
- 4. Why is the “Admittance Method” preferred over the “Impedance Method” for parallel circuits?**
  - Hint: Explain that in parallel, admittances ( $G$  and  $B$ ) can be added arithmetically/algebraically, whereas impedances must be added as reciprocals ( $1/Z_{total} = 1/Z_1 + 1/Z_2$ ), which is mathematically complex.
- 5. Draw and explain the Admittance Triangle.**
  - Hint: The student should sketch a right triangle with Conductance ( $G$ ) on the x-axis, Susceptance ( $B$ ) on the y-axis, and Admittance ( $Y$ ) as the hypotenuse.
- 6. State the condition for Resonance in a parallel R-L-C circuit.**
  - Hint: The condition occurs when the reactive component of the line current is zero, or when Inductive Susceptance equals Capacitive Susceptance ( $B_L = B_C$ ).
- 7. What is “Dynamic Impedance”? Why is it important?**
  - Hint: It is the purely resistive impedance of the parallel circuit at resonance ( $L/CR$ ). It represents the maximum opposition to current flow at the resonant frequency.
- 8. Contrast the Power Factor of a Parallel AC circuit at Resonance versus off-Resonance.**
  - Hint: At resonance, PF is Unity (1). Below or above resonance, the circuit behaves as either inductive (lagging) or capacitive (leading).
- 9. Why is the line current minimum at parallel resonance?**
  - Hint: Since the inductive and capacitive currents cancel each other out (being  $180^\circ$  apart), the source only supplies the small active current required by the resistance.
- 10. Explain the term “Current Magnification” in the context of parallel resonance.**
  - Hint: The circulating current between the inductor and capacitor can be many times larger than the current drawn from the supply. ( $Q$ -factor  $\times$  Source Current).

---

### Answer Key (MCQs)

Q.No	Answer	Q.No	Answer
1	B	11	B
2	C	12	B
3	C	13	A
4	B	14	C
5	C	15	B

Q.No	Answer	Q.No	Answer
6	A	16	B
7	B	17	C
8	C	18	A
9	A	19	B
10	C	20	B

**Note on Q14 Calculation:**  $Y = \sqrt{G^2 + B^2} = \sqrt{0.06^2 + 0.08^2} = \sqrt{0.0036 + 0.0064} = \sqrt{0.01} = 0.1 \text{ S.}$

---

**Next Step for Faculty/Student:** Would you like me to generate a **step-by-step numerical problem** with a solution for the “Admittance Method” to use as a tutorial example?

## Digital Resource Library: Single Phase AC Parallel Circuits

### 1. AI Tools & Digital Learning Tools

These tools are selected to help you visualize complex AC concepts (like phase differences and resonance) and perform the specific experiments mentioned in your syllabus list (Practicals 9, 10, & 11).

Tool Name	Type	Purpose / Use-Case for Unit 3	How it Helps Learning
<b>Virtual Labs</b> (vlab.co.in) [cite: 88]	Virtual Lab / Simulation	<b>Performing Virtual Experiments:</b> specifically for measuring Voltage, Current, Power, and Power Factor in RL, RC, and RLC parallel circuits.	Directly supports the syllabus “List of Laboratory” requirements. Allows you to safely practice circuit connections and take readings before the actual hardware lab.
<b>Falstad Circuit Simulator</b>	Web-based Circuit Visualizer	<b>Visualizing Current Flow &amp; Phasors:</b> Build parallel R-L-C circuits and see the current splitting into branches in real-time.	Helps you “see” why branch currents ( $I_R$ , $I_L$ , $I_C$ ) are different and how they add up vectorially (phasor sum) rather than arithmetically.
<b>WolframAlpha</b>	Computational Engine	<b>Complex Algebra Calculator:</b> Use it to check your “Admittance Method” calculations, specifically converting Impedance ( $Z = R + jX$ ) to Admittance ( $Y = G \pm jB$ ).	Parallel circuit problems involve difficult complex number division ( $1/Z$ ). This tool verifies your math accuracy for homework and tutorial problems.
<b>GeoGebra</b>	Graphing Tool	<b>Dynamic Phasor Diagrams:</b> Plot currents and voltages as vectors to understand “Lagging” vs. “Leading” in parallel branches.	Great for visualizing the <b>Admittance Triangle</b> and seeing how changing frequency affects the vectors during <b>Parallel Resonance</b> .

## 2. Video Learning Repository

This collection features content from reliable educational channels, including NPTEL (as recommended in your syllabus ) and other student-friendly platforms.

Topic Name	Recommended Channel / Source	Search Keywords (Copy & Paste these)
Basics of AC Parallel Circuits	Neso Academy	Neso Academy parallel AC circuit analysis phasor diagram
Admittance, Conductance & Susceptance	Ekeeda or Tikle's Academy	Admittance Conductance Susceptance definition diploma electrical
Solving Parallel Circuits (Admittance Method)	Engineering Funda	Admittance method for solving parallel AC circuits problems
Parallel Resonance & Bandwidth	NPTEL (IIT Kharagpur)	NPTEL Basic Electrical Engineering Parallel Resonance
Comparison: Series vs. Parallel Resonance	Last Moment Tutorials	Difference between series and parallel resonance engineering
Calculations in Parallel R-L-C Circuits	Electrical4U [cite: 86]	Parallel RLC circuit solved problems electrical4u

### Student Tips for Using These Resources:

- **For Revision:** Watch the Neso Academy videos to clear your concepts on how current divides in parallel branches.
- **For Exams:** Use the Comparison video to prepare for the common theory question: "Compare Series and Parallel Resonance".
- **For Practicals:** Use Virtual Labs to simulate the "Parallel Resonance" condition before your final lab exam.

---

**Next Step for Faculty/Student:** Would you like me to generate a "10-Minute Rapid Fire Quiz" based on these video topics to test your retention after watching them?

## External Exposure Module: AC Fundamental

### 1. Beyond the Syllabus – Emerging Technologies

**Objective:** To understand how the basic sine waves and phasors you study today evolve into cutting-edge technology.

#### A. Smart Metering & Advanced Metering Infrastructure (AMI)

- **The Connection:** In **Unit 1**, you learn about RMS values, instantaneous values, and power consumption. A standard energy meter measures this. A Smart Meter takes this further by measuring parameters in real-time and communicating two-way with the utility provider.
- **Why it Matters:** The Indian power sector is aggressively moving towards Smart Grids. Understanding how AC parameters (voltage sags, swells, and power factor) are monitored digitally is a key skill for future jobs in power distribution companies (DISCOMs) like MGCL or UGCL.
- **B. FACTS (Flexible AC Transmission Systems)**
- **The Connection:** In **Unit 2 & 3**, you study Reactive Power, Power Factor, and Impedance. FACTS devices are essentially high-tech versions of the capacitors and inductors you use in labs. They use power electronics to dynamically control the “Impedance” and “Phase Angle” of transmission lines to stabilize voltage.
- **Why it Matters:** As renewable energy (Solar/Wind) grows, grid stability becomes harder to maintain. FACTS technology is the solution. Knowing the basics of “Reactive Power Compensation” (a core outcome of this course ) puts you on the path to understanding these advanced grid stabilizers.

---

### 2. MOOC & Online Course Recommendations

**Objective:** To provide high-quality, self-paced learning resources that reinforce your diploma studies with visualizations and expert explanations.

Course Title / Theme	Platform	How it Complements Your Syllabus
Basic Electrical Circuits	NPTEL / SWAYAM	Recommended in your syllabus. It offers rigorous mathematical derivations for <b>Series and Parallel Resonance</b> , helping you master the complex algebra method mentioned in <b>Unit 3</b> .
Electric Power Systems	Coursera (Audit for Free)	Connects your <b>Unit 4 (Three Phase Systems)</b> to the real world of generation and distribution. It visualizes why we use 3-phase systems instead of single-phase for transmission.

Course Title / Theme	Platform	How it Complements Your Syllabus
Circuit Analysis via Khan Academy	Khan Academy	Also recommended in your syllabus. Excellent for “slow learners” or visual learners. It breaks down <b>Phasor Diagrams</b> and <b>Sinusoidal Functions</b> into very simple, bite-sized video lessons.

### 3. Industrial Exposure / Field Visit Suggestions (Gujarat Focus)

**Objective:** To see the “AC Fundamental” concepts (Star/Delta, Transformers, Generation) in action within the Gujarat industrial ecosystem.

#### A. GETCO Substations (Gujarat Energy Transmission Corporation)

- **Location:** Various locations across Gujarat (e.g., Jambuva, Ranasan).
- **What to Observe:**
  - **3-Phase Systems:** See the actual physical arrangement of Red, Yellow, and Blue (R-Y-B) busbars.
  - **Transformers:** Observe Star-Delta connections in power transformers.
  - **Capacitor Banks:** See large-scale “Parallel Capacitors” used for Power Factor Correction, directly relating to **Unit 3** concepts.

#### B. Transformer Manufacturing Units (e.g., Voltamp, Shilchar - Vadodara)

- **Location:** Vadodara (The hub of electrical engineering in Gujarat).
- **What to Observe:**
  - **Coil Winding:** See how inductance (L) is created physically.
  - **Testing Labs:** Witness “Open Circuit” and “Short Circuit” tests which rely heavily on AC circuit analysis and phasor interpretation.

#### C. Solar Parks (e.g., Charanka Solar Park)

- **Location:** Patan District, Gujarat.
- **What to Observe:**
  - **Inverters:** Since solar panels produce DC, you will see huge Inverters converting DC to AC. This reinforces the “Comparison between AC and DC Systems” from **Unit 1**.
  - **Grid Synchronization:** Learn how the AC frequency generated by the park is matched exactly to the 50Hz grid frequency (Unit 1 concepts).

### 4. Conferences, Seminars & Technical Events

**Objective:** To inspire professional growth and networking.

#### A. ELECRAMA

- **Theme:** The world's largest electrical show, held periodically in Greater Noida (accessible for major trips).
- **Benefit:** You can see the latest AC circuit breakers, smart grids, and testing equipment. It gives you a vision of the scale of the electrical industry beyond the textbook.

#### B. IEEE India Council / Gujarat Section Events

- **Theme:** Technical symposiums often held at major colleges (IIT Gandhinagar, SVNIT, MSU).
- **Benefit:** Attending student-level paper presentations exposes you to how other students are applying **AC principles** to build projects like "Wireless Power Transfer" or "Smart Home Automation."

#### C. Regional "Project Expos" at GTU

- **Theme:** Final year project showcases.
- **Benefit:** Observing final year projects (often involving Induction Motors or Generators ) helps you understand how the **Unit 4** (Three Phase) concepts are used to build working models.

---

**Next Step for Faculty/Student:** Would you like me to draft a "**Field Visit Observation Sheet**" for a visit to a Substation, specifically guiding students on what AC parameters to record (e.g., Line Voltage vs Phase Voltage)?

## Predicted Question Bank: Single Phase AC Parallel Circuits

### 1. Most Repeated / High-Probability Questions

**Context:** These questions are based on the core topics listed in the syllabus (Admittance, Resonance, Vector Methods) and represent the standard theory questions asked in Diploma exams.

#### Short Answer Questions (2-3 Marks)

- 1. Define Admittance, Conductance, and Susceptance.**
  - Reference: Syllabus Topic 3(2) - Terms related to AC parallel circuits.
  - Expected Answer: Define each term (Y, G, B), state their units (Siemens/Mho), and their formulas relative to Impedance (Z), Resistance (R), and Reactance (X).
- 2. State the condition for Parallel Resonance.**
  - Reference: Syllabus Topic 3(5) - Resonance condition.
  - Expected Answer: State that resonance occurs when the reactive component of line current is zero (or Inductive Susceptance  $B_L =$  Capacitive Susceptance  $B_C$ ).
- 3. Draw the Admittance Triangle.**
  - Reference: Syllabus Topic 3(2).
  - Expected Answer: \* Note: A diagram showing Conductance (G) on the horizontal axis, Susceptance (B) on the vertical axis, and Admittance (Y) as the hypotenuse.
- 4. Why is the Admittance method preferred over the Impedance method for parallel circuits?**
  - Reference: Syllabus Topic 3(3) - Admittance method.
  - Expected Answer: Explain that admittances add up arithmetically/algebraically in parallel ( $Y_T = Y_1 + Y_2$ ), whereas impedances add inversely ( $1/Z_T = 1/Z_1 + 1/Z_2$ ), making calculation easier.

#### Descriptive / Long Answer Questions (4-7 Marks)

- 5. Compare Series Resonance and Parallel Resonance.**
  - Reference: Syllabus Topic 3(6).
  - Expected Answer: A comparison table covering:
    - Impedance (Min vs Max)
    - Current (Max vs Min)
    - Power Factor (Unity for both)
    - Magnification (Voltage vs Current)
    - Behavior below resonant frequency (Capacitive vs Inductive).
- 6. Explain the Phasor (Vector) Method for solving a Parallel RC circuit.**
  - Reference: Syllabus Topic 3(1).
  - Expected Answer: Draw the circuit diagram, the phasor diagram showing Voltage as the reference vector, and derive the expression for total current  $I = \sqrt{I_R^2 + I_C^2}$ .
- 7. Derive the expression for Resonant Frequency ( $f_r$ ) in a parallel R-L-C circuit.**
  - Reference: Syllabus Topic 3(5).
  - Expected Answer: Start with the condition  $I_C = I_L \sin(\phi_L)$  or  $B_C = B_L$  and solve for f to get the standard resonant frequency formula.
- 8. Explain the term "Dynamic Impedance" of a parallel circuit and derive its formula.**
  - Reference: Syllabus Topic 3(5).

- Expected Answer: Define it as the impedance at resonance ( $L/CR$ ) and explain why it is purely resistive and maximum in value.
- 

## 2. Application & Logical Thinking Questions

**Context:** These questions test “Concept Application” (A-Level) and “Analysis” (N-Level), distinguishing high-scoring students. They focus on why the circuit behaves a certain way.

5. **“A parallel resonant circuit is often called a Rejector Circuit.” Justify this statement.**
    - Concept Tested: Impedance characteristics at resonance.
    - Reasoning: At resonance, the parallel circuit offers maximum dynamic impedance to the flow of current from the source. Therefore, it “rejects” (allows minimum current to pass) signals at that specific resonant frequency while allowing others to pass.
  6. **In a parallel AC circuit, if the supply frequency is increased, what happens to the Inductive Susceptance ( $B_L$ ) and Capacitive Susceptance ( $B_C$ )?**
    - Concept Tested: Frequency dependence of  $X_L$  and  $X_C$ .
    - Reasoning:  $B_L = 1/(2\pi fL)$  (inversely proportional) and  $B_C = 2\pi fC$  (directly proportional). As frequency increases, inductive susceptance decreases, and capacitive susceptance increases.
  7. **Why does “Current Magnification” occur in parallel resonant circuits?**
    - Concept Tested: Internal energy exchange vs source current.
    - Reasoning: The current circulating between the inductor and capacitor is much larger than the line current drawn from the source. The source only supplies the active losses, while L and C exchange reactive power internally.
  8. **A student calculates the total current in a parallel RL circuit by adding the branch currents arithmetically ( $I = I_R + I_L$ ). Is this correct? Explain why or why not.**
    - Concept Tested: Vector representation of alternating quantity.
    - Reasoning: No. In AC circuits, currents in parallel branches have phase differences (Resistive is in phase, Inductive lags by  $90^\circ$ ). They must be added vectorially (Phasor Sum), not arithmetically.
  9. **If a capacitor is connected in parallel across an inductive coil (R-L series branch), what is the effect on the overall Power Factor of the circuit?**
    - Concept Tested: Admittance and Power Factor correction principles.
    - Reasoning: The capacitor draws a leading current that neutralizes the lagging component of the inductor’s current. This reduces the total reactive current drawn from the supply, thereby improving (increasing) the overall power factor towards unity.
- 

### Note for Exam Preparation (Numericals)

According to the syllabus, there is a specific listing for “**Numerical based on AC parallel circuits and parallel resonance.**” Students must practice problems involving:

- Calculating Y, G, and B given R,  $X_L$ ,  $X_C$ .
- Finding Total Current and Power Factor using the **Admittance Method**.
- Finding Resonant Frequency and Dynamic Impedance given circuit parameters.

**Next Step for Student:** Would you like me to generate a **Sample Numerical Problem** with the step-by-step solution using the “Admittance Method” to practice for the exam.

### Unit 4: Three Phase System and Circuits

- **Total Weightage:** 23%
- **Total Teaching Hours:** 12 Hours
- **Course Outcome (CO4):** Apply principles of three phase system to solve electrical circuits.

#### Strategic Study Plan

This plan is logically sequenced to build your understanding step-by-step: from Generation → Terminology → Connections → Calculations.

Topic Sequence	Syllabus Content	Type	Est. Hours	Learning Goals & Exam Relevance
1. The “Why” & “How”	(1) Comparison between single and three phase systems (2) Principle of generation of three phase alternating voltage	Core Concept	2 Hours	<b>Goal:</b> Understand why we use 3-phase (efficiency, power) and how 3 coils at 120° create it. <b>Exam:</b> High probability of “Compare 1- $\phi$ vs 3- $\phi$ ” theory question.
2. The Language of 3-Phase	(3) Three phase system terminology:- Phase sequence (R-Y-B)- Balanced & Unbalanced supply/load- Importance of these terms	Supporting	1 Hour	<b>Goal:</b> Speak the industry language. Know what happens if phase sequence is reversed (motor direction changes). <b>Viva:</b> Crucial for oral exams.
3. Voltage & Current Definitions	(4) Values of voltage and current in three phase system:- Line Voltage ( $V_L$ ) vs Phase Voltage ( $V_{ph}$ )- Line Current ( $I_L$ ) vs Phase Current ( $I_{ph}$ )	Core Concept	1 Hour	<b>Goal:</b> Distinguish between what you measure between wires (L – L) vs. wire-to-neutral (L – N). <b>Key:</b> $V_L$ is not equal to $V_{ph}$ !
4. Star Connection (Y)	(5) Three phase star connection	Core Application	2 Hours	<b>Goal:</b> Master the Star relationships: $I_L = I_{ph}$ and $V_L = \sqrt{3}V_{ph}$ . <b>Exam:</b>

Topic Sequence	Syllabus Content	Type	Est. Hours	Learning Goals & Exam Relevance
				Derivation of these relations is a standard exam question.
5. Delta Connection ( $\Delta$ )	(6) Three phase delta connection	Core Application	2 Hours	<b>Goal:</b> Master the Delta relationships: $V_L = V_{ph}$ and $I_L = \sqrt{3}I_{ph}$ . <b>Practical:</b> Most industrial motors run in Delta.
6. Solving Circuits (Numericals)	(7) Numerical based on three phase circuits	Application	4 Hours	<b>Goal:</b> Calculate Power ( $P = \sqrt{3}V_L I_L \cos\phi$ ) for both Star and Delta loads. <b>Exam:</b> High weightage. Expect a full numerical problem asking for Line Current, Phase Current, and Total Power.

### Mentor's Insight for Success

- **Focus on the "Magic Number":** The square root of 3 ( $\sqrt{3} = 1.732$ ). It appears everywhere in this unit. If you are calculating 3-phase power or converting Line/Phase values and you don't use  $\sqrt{3}$ , check your work again!
- **Visual Learning:** Don't just memorize formulas. Draw the **Phasor Diagrams** for Star and Delta voltages. Visualizing the  $30^\circ$  angle difference is the difference between passing and scoring an 'A'.
- **Practical Connection:**
  - **Lab 12 & 13:** You will verify these relations physically in the lab. Treat the lab as a practice exam.
  - **Project Idea:** Build a chart showing the difference between Star and Delta connections as part of your suggested project list.

### Next Step

Would you like me to generate a **Comparison Table for Star vs. Delta Connections** that you can print out as a "Cheat Sheet" for revision.

## Unit 4: Three Phase System and Circuits

## Topic 1: Comparison between Single and Three Phase Systems.

---

### Lecture: Single Phase vs. Three Phase Systems – The Power Upgrade

**Topic:** Comparison between Single Phase and Three Phase Systems

**Duration:** 60 Minutes

**Reference:** Unit 4,

Topic 1

---

#### 1. Hook / Introduction (5 Minutes)

**“The Bicycle vs. The Car Engine”** Good morning, future engineers! Imagine you are riding a bicycle with only one pedal. Every time that pedal reaches the top or bottom dead center, your power delivery stops for a split second. You move in “pulses.” Now, imagine a car engine with multiple cylinders firing one after another. The power is smooth, continuous, and strong.

This is exactly the difference between the **Single Phase** supply in your house (the bicycle) and the **Three Phase** supply in industries (the car engine).


Today, we answer the big question: Why does the entire world generate and transmit electricity in Three Phases, not one? It’s not just a random choice—it’s about saving money and increasing efficiency.

---

#### 2. Core Concepts (40 Minutes)
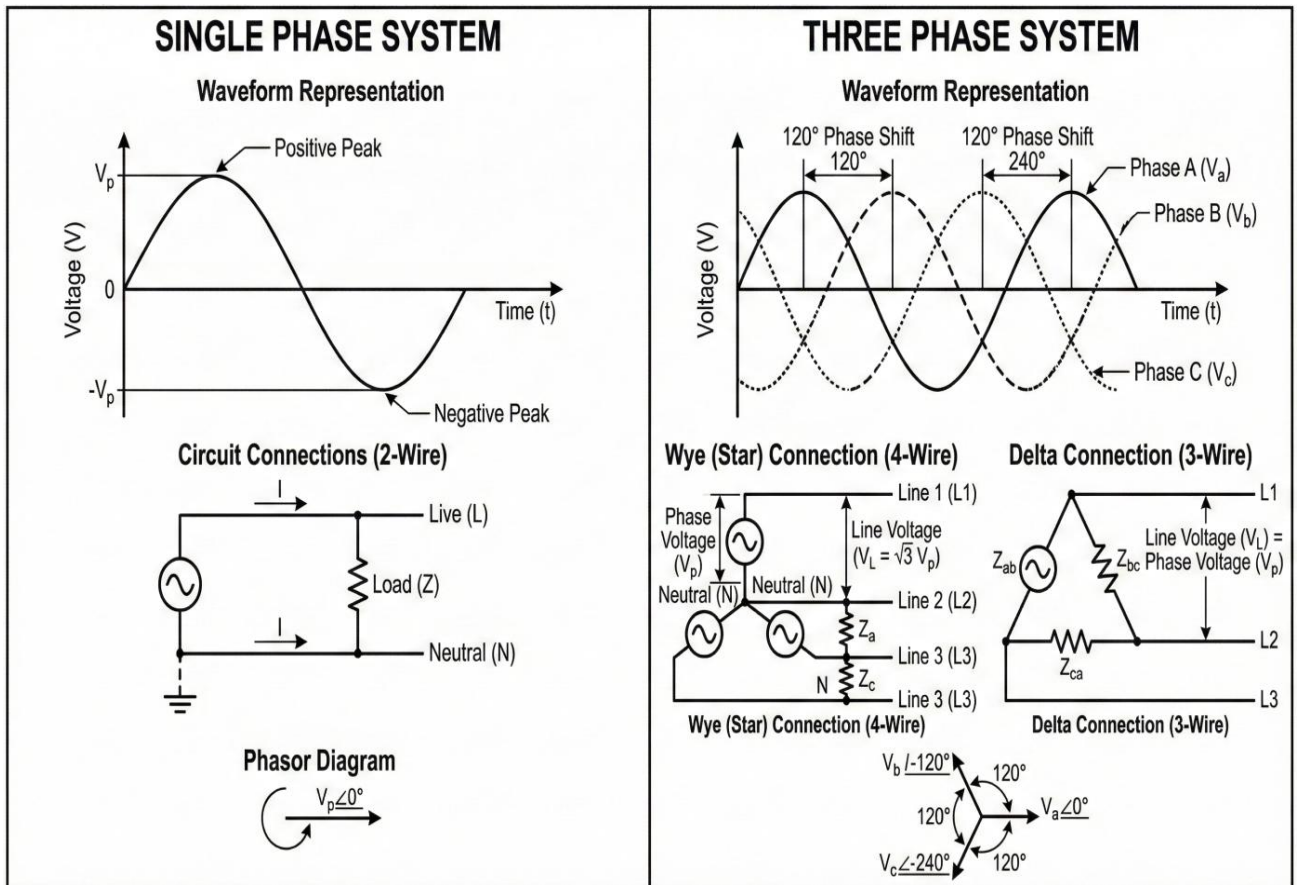
##### A. Understanding the Difference

- **Single Phase (1- $\phi$ ):** Think of it as a single alternating voltage source connected to a load. It requires two wires: one Phase (Live) and one Neutral. The voltage peaks and hits zero 100 times a second (at 50Hz). This means the power delivered is pulsating—it actually touches zero instant by instant! \*
- **Three Phase (3- $\phi$ ):** Here, we have three separate voltages of the same frequency but shifted by  $120^\circ$  in time. It requires 3 or 4 wires (R, Y, B, and Neutral). When Phase R is at zero, Phase Y and B are conducting. The result? A constant, steady flow of power that never drops to zero.



## B. Key Advantages of 3-Phase over 1-Phase (The Exam Favorites)

1. **More Power for the Same Size:** A 3-phase motor produces about 1.5 times the output of a 1-phase motor of the same physical size.
2. **Constant Power Flow:** In 1-phase circuits, instantaneous power pulsates. In balanced 3-phase circuits, the total instantaneous power is constant. This results in **less vibration** in motors.
3. **Self-Starting Motors:**
  - 1-Phase Motor: Like a parked bicycle, it needs a push (capacitor/auxiliary winding) to start because it produces a pulsating magnetic field.
  - 3-Phase Motor: The three time-shifted currents create a **Rotating Magnetic Field (RMF)** naturally. The motor starts running the moment you switch it on.
4. **Copper Economy (The Money Saver):** To transmit the same amount of power over a fixed distance, a 3-phase system requires much less conductor material (copper/aluminum) than a 1-phase system. This saves millions in transmission costs.

### 3. Real-World / Industry Applications (10 Minutes)

- **The Power Grid:** Look at the high-tension towers outside the city. You will always see wires in multiples of three (3, 6, or 12). Generation and Transmission are exclusively 3-phase because it is the most efficient way to move energy.
  - **Industrial Floor:** Walk into any factory in Gujarat—textile, chemical, or auto. The heavy motors driving conveyor belts, pumps, and lathes are all **3-Phase Induction Motors**. Why? They are rugged, cheaper, and don't need complex starting switches like the fans in your house.
  - **Fun Fact:** Did you know that electric trains often use single-phase overhead lines but convert it to 3-phase inside the locomotive to run the traction motors? That's how superior 3-phase torque is!
- 

### 4. Summary & Q&A (5 Minutes)

#### Quick Recap:

- **1-Phase:** Two wires, pulsating power, motors are not self-starting, less efficient. Used for domestic loads (TV, Lights, Fans).
- **3-Phase:** Three/Four wires, constant power, self-starting motors, saves copper. Used for Generation, Transmission, and Heavy Industries.

**Typical Student Doubt:** "Sir, if 3-phase is so good, why don't we use it for our TV and phone chargers?"

- **Answer:** Cost and complexity. You don't need industrial efficiency to charge a phone, and wiring every wall socket with 4 wires would be too expensive and dangerous for a home.
- 

#### Mentor's Career Tip

"Students, mastering 3-Phase systems is your gateway to core electrical jobs. Whether you work for **GETCO** (Transmission) or private giants like **Reliance/Adani** (Generation), the interviewers will ask about 'Star-Delta' connections and 'Phase Sequence.' Treat this unit not just as theory, but as the manual for your future toolkit."

## Topic 2: Principle of Generation of Three Phase Alternating Voltage.

### Lecture: The Symphony of Power – Generating Three Phase Voltage

#### Topic: Principle of Generation of Three Phase Alternating Voltage

Duration: 60 Minutes

Reference: Unit 4, Topic 2

---

#### 1. Hook / Introduction (5 Minutes)

**“The Three-Cylinder Engine”** Welcome back, class! In Unit 1, we learned how a single coil rotating in a magnetic field generates a single sine wave. Imagine that single coil is like a cyclist pedaling with one leg. It works, but it’s jerky.

Now, imagine a powerful car engine. Does it have just one piston? No, it usually has multiple pistons firing in a specific sequence to create smooth, continuous power. Today, we are going to upgrade our “electrical engine.” We aren’t just going to spin one coil; we are going to spin three identical coils simultaneously. This is the birth of the **Three Phase System**—the heartbeat of every major industry in the world.

**Thought Question:** Why do you think the coils must be placed exactly  $120^\circ$  apart? Keep that number in mind— $120^\circ$ . It is the magic number for today!


---

#### 2. Core Concepts (40 Minutes)

**A. The Physical Setup (The Alternator)** To generate three-phase voltage, we use a machine called an **Alternator** (AC Generator). Unlike the single-phase generator you studied earlier, this machine has a specific construction:

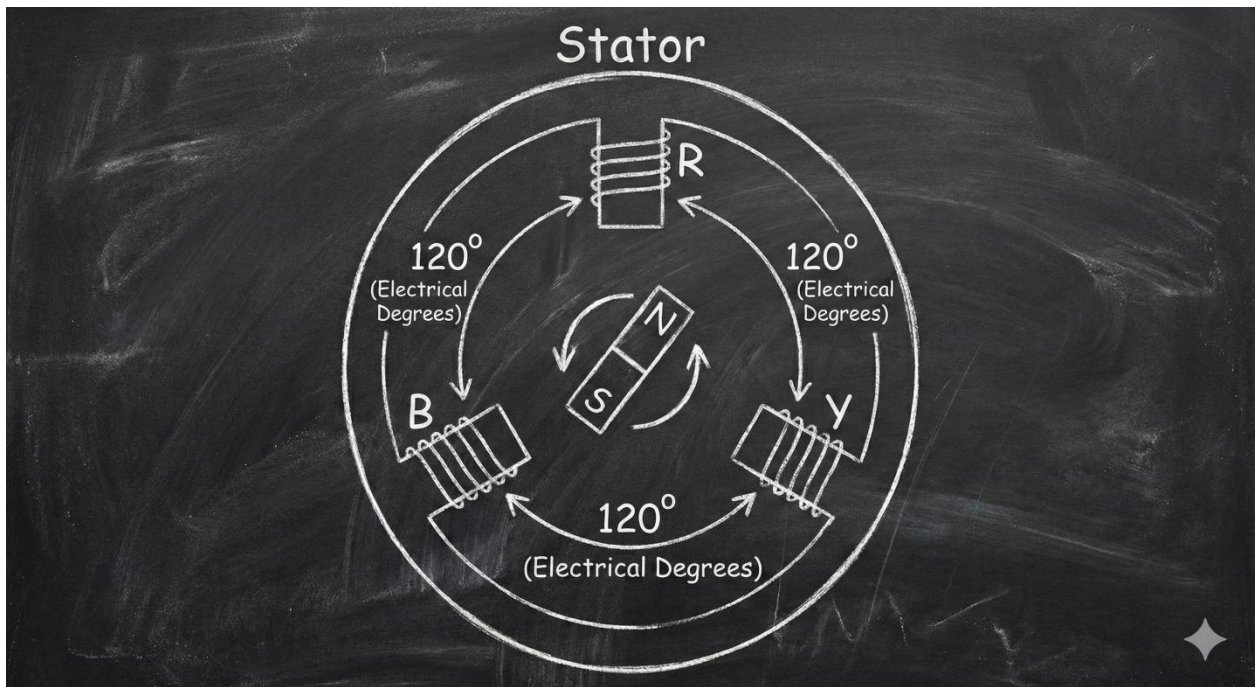1. **Three Coils:** We take three identical coils (let’s call them **R**, **Y**, and **B** for Red, Yellow, Blue). Each coil has the same number of turns.
2.  **$120^\circ$  Displacement:** This is crucial. We place these coils on the stator (the stationary part) physically spaced  $120^\circ$  **apart** from each other in space.
  - Coil R is at  $0^\circ$ .
  - Coil Y is at  $120^\circ$ .
  - Coil B is at  $240^\circ$  (or  $-120^\circ$ ).
3. **The Rotor:** A strong magnet (electromagnet) rotates inside these coils at a constant speed ( $\omega$  rad/sec).

**Visual Description for Board Work:** Draw a circle representing the stator. Place three rectangles representing coils at the 12 o’clock (R), 4 o’clock (Y), and 8 o’clock (B) positions. Draw a North-South magnet in the center. Label the angle between any two coils as  $120^\circ$  (**electrical degrees**). **B. The Generation Process (Faraday’s Law in Action)** As the magnet rotates, it cuts the flux of each coil sequentially.



- **At Instant 1:** The North pole passes Coil R. Maximum EMF is induced in R.
- **Rotation Continues:** The magnet has to rotate  $120^\circ$  to reach Coil Y. This takes a fraction of time.
- **At Instant 2:** Now, maximum EMF is induced in Coil Y. But remember, this happens after Coil R has peaked.
- **At Instant 3:** The magnet rotates another  $120^\circ$  to reach Coil B. Now Coil B peaks.


Because the coils are mechanically displaced by  $120^\circ$ , the voltages generated are **electrically displaced by  $120^\circ$** . They have the same amplitude ( $E_{\max}$ ) and the same frequency ( $f$ ), but they do not start at the same time.

**C. The Equations (The Mathematical Beauty)** If we take the voltage in Coil R as the reference, the equations for the instantaneous voltages are:

4.  $e_R = E_m \sin(\omega t)$
5.  $e_Y = E_m \sin(\omega t - 120^\circ)$  (Lags R by  $120^\circ$ )
6.  $e_B = E_m \sin(\omega t - 240^\circ)$  (Lags Y by another  $120^\circ$ )

**Visual Description for Board Work:** Draw the waveform diagram. \* Start a sine wave (R) from the origin (0). \* Start the second sine wave (Y) from a point on the x-axis marked " $120^\circ$ ". \* Start the third sine wave (B) from a point marked " $240^\circ$ ". \* Show that at any vertical line you draw, the sum of the three voltages is zero ( $e_R + e_Y + e_B = 0$ ).

## THREE-PHASE WAVEFORM DIAGRAM

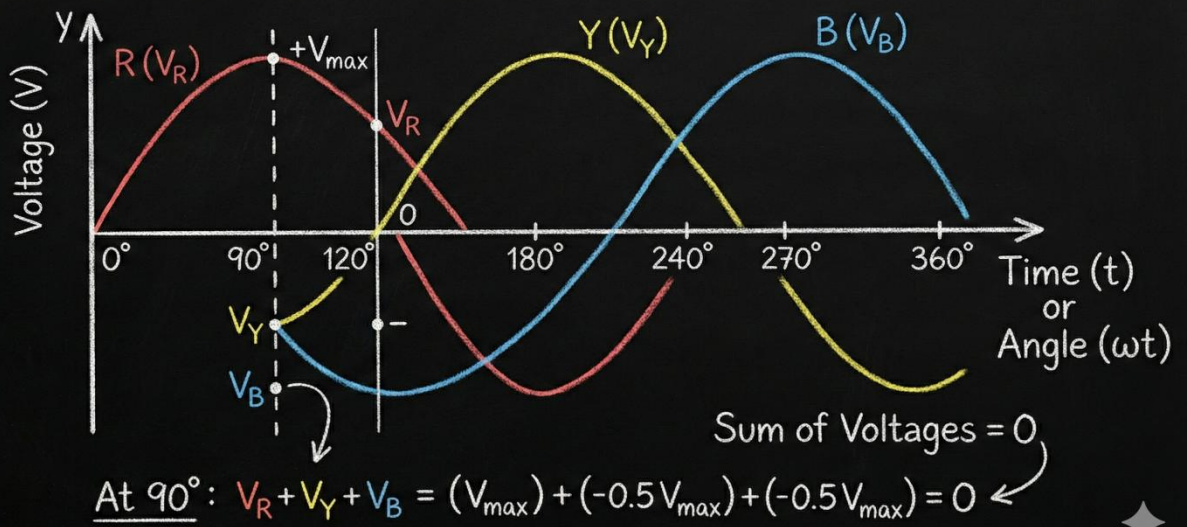

### 3. Real-World / Industry Applications (10 Minutes)

- **Power Plants:** Whether it's the **Ukai Thermal Power Station** or a hydro plant at **Sardar Sarovar**, the generators used are massive 3-Phase Synchronous Generators.

## Topic 3: Three Phase System Terminology.

### Lecture: Speaking the Language of Three Phase – Terminology & Concepts

**Topic:** Three Phase System Terminology (Phase Sequence, Balanced/Unbalanced Supply & Load)

**Duration:** 60 Minutes

**Reference:** Unit 4, Topic 3

#### 1. Hook / Introduction (5 Minutes)

**“The Case of the Backward Motor”** Imagine you are a junior engineer at a factory. Your boss asks you to connect a huge conveyor belt motor. You connect the three wires—Red, Yellow, Blue. You hit the “Start” button, and disaster strikes! Instead of moving the products forward, the conveyor runs backward, dumping everything on the floor.


What went wrong? The motor was fine. The power was fine. The problem was the **Phase Sequence**. You swapped two wires without realizing it.



Today, we will learn the essential vocabulary of the three-phase world. These aren’t just definitions; they are the safety rules that prevent expensive equipment (and your career) from crashing.

#### 2. Core Concepts (40 Minutes)
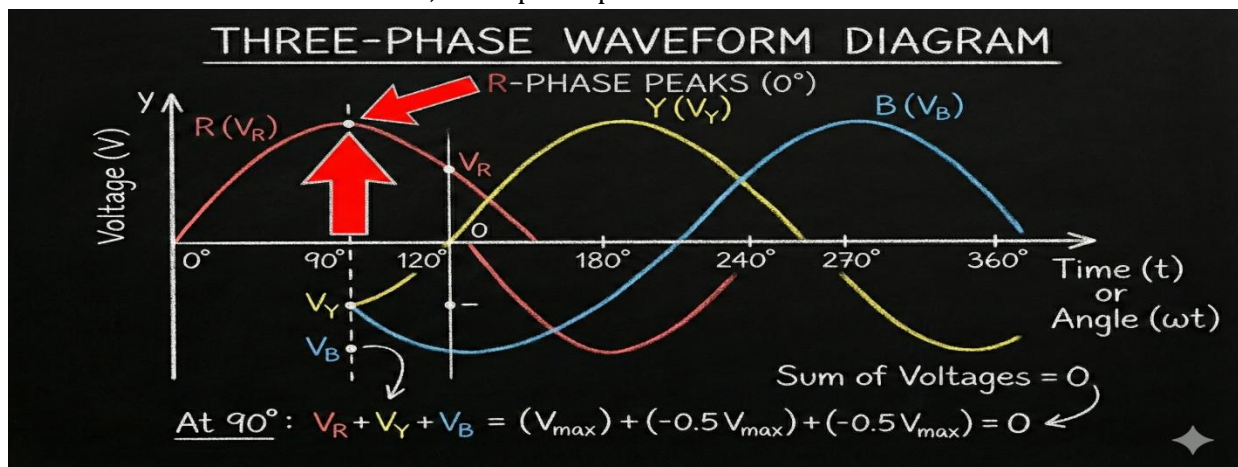
##### A. Phase Sequence (The Order of Arrival)

- **Definition:** Phase sequence is the order in which the voltages of the three phases reach their maximum positive value.
- **Standard Sequence:** The universal standard is **R-Y-B** (Red, Yellow, Blue).
  - First, the R-phase peaks.
  - 120° later, the Y-phase peaks.
  - Another 120° later, the B-phase peaks.



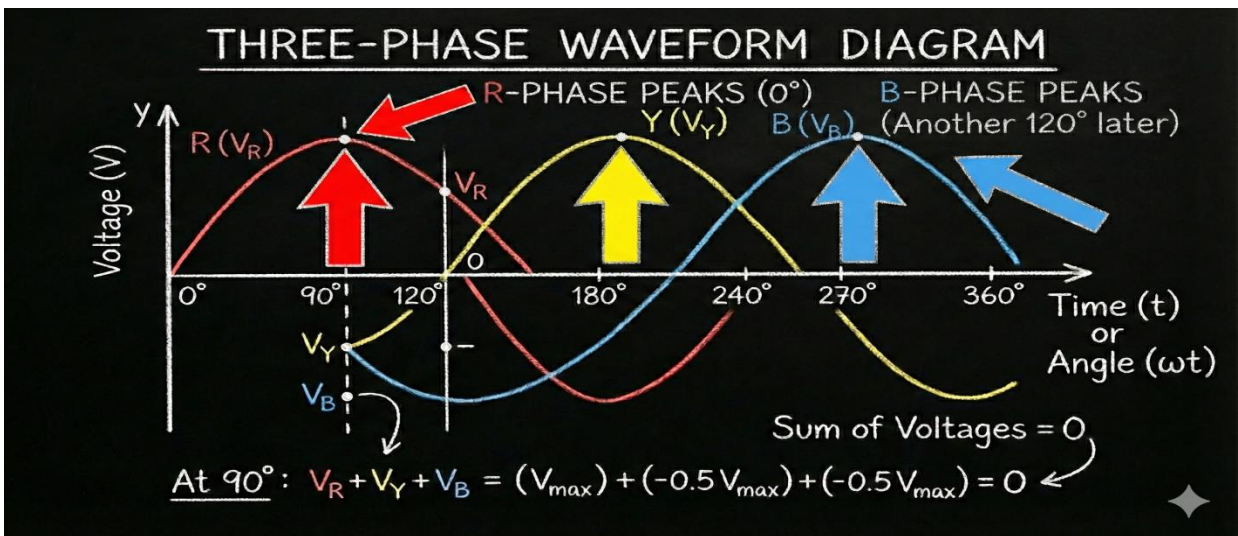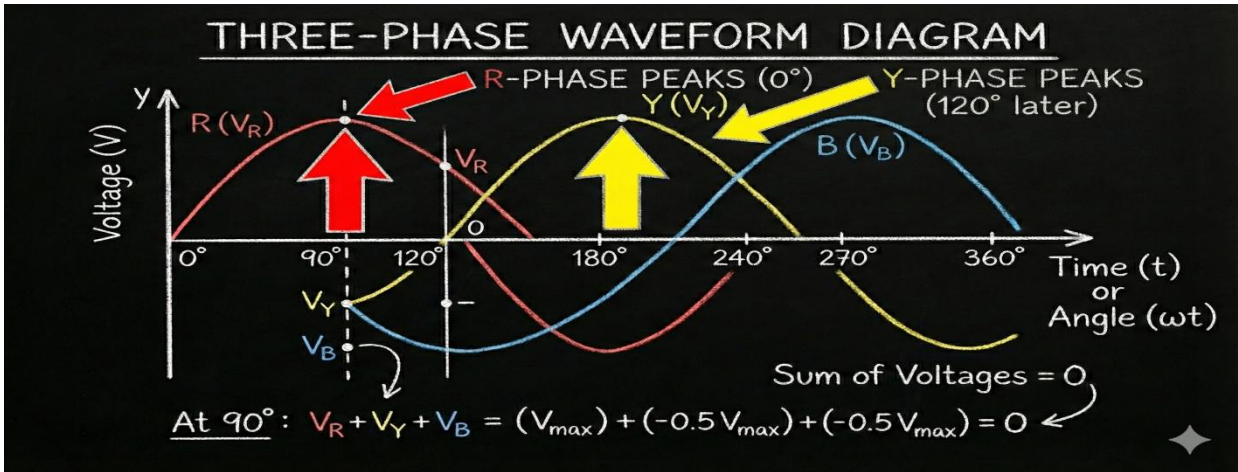


- **Reversing Sequence:** If you swap any two wires (e.g., connect R-B-Y instead of R-Y-B), the rotation of the magnetic field reverses. This is why our “Backward Motor” accident happened!
- **Visual Check:** We use an instrument called a “Phase Sequence Indicator” to check this before connecting motors.


**Visual Description for Board Work:** Draw three sine waves starting at different points.  
 \* Label the first peak “R”. \* Label the second peak “Y” (appearing to the right of R). \* Label the third peak “B”. \* Draw an arrow showing time flowing from Left to Right.
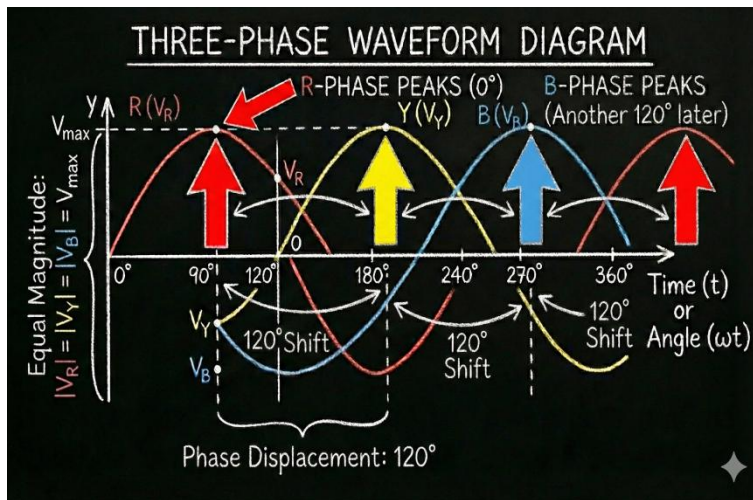
#### B. Balanced vs. Unbalanced Supply

- **Balanced Supply:** A three-phase voltage source is “Balanced” if:
  1. All three voltages are equal in magnitude ( $V_R = V_Y = V_B$ ).



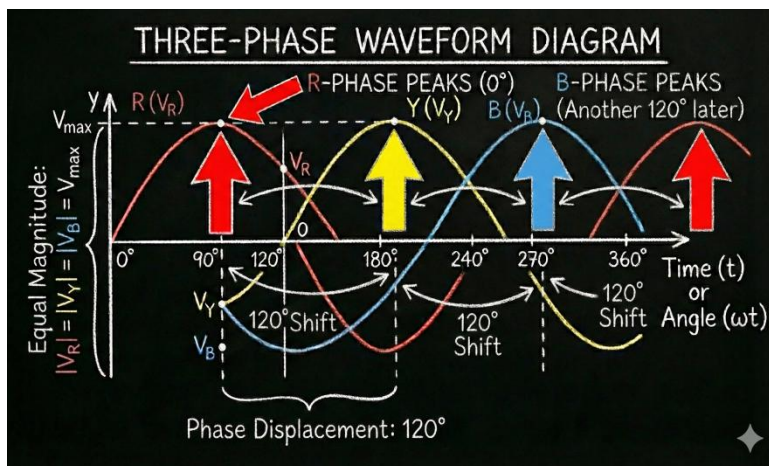
2. They are displaced by exactly  $120^\circ$  from each other.





- **Unbalanced Supply:** If the magnitudes are unequal or the phase angle is not exactly  $120^\circ$ , the supply is unbalanced. This is bad news—it causes heating and vibrations in machines.
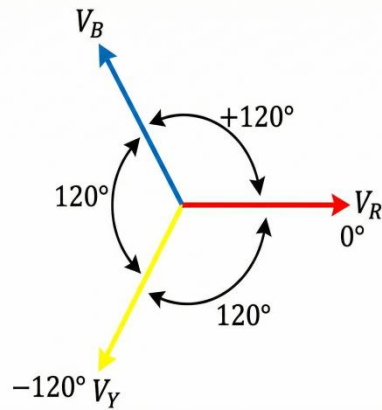
### C. Balanced vs. Unbalanced Load

- **Balanced Load:** A load is balanced if the impedance ( $Z$ ) in all three phases is identical in magnitude and phase angle.
  - Example: A 3-phase induction motor is a balanced load because all three windings are identical.
  - Currents: In a balanced load, the sum of the three currents is always zero ( $I_R + I_Y + I_B = 0$ ). This means current doesn't flow in the neutral wire!



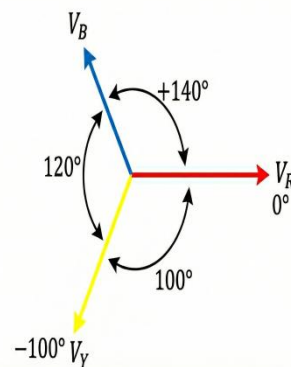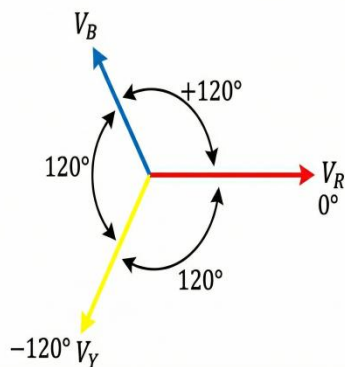- **Unbalanced Load:** If the impedances across the three phases are different.
  - Example: A building where Phase R feeds the ACs, Phase Y feeds the lights, and Phase B feeds the computers. Since these loads are different, the system is unbalanced.
  - Currents: The currents are unequal, and a “resultant current” flows through the neutral wire.



**Visual Description for Board Work:** \* **Diagram 1 (Balanced):** A Star connection where each arm has a resistor of  $10\Omega$ . Label it “Balanced Load.” \* **Diagram 2 (Unbalanced):** A Star connection where Arm R has a 100W bulb, Arm Y has a 1000W heater, and Arm B has a fan. Label it “Unbalanced Load.”

### 3. Real-World / Industry Applications (10 Minutes)

- **The Neutral Wire Problem:** In office buildings (Unbalanced Load), the neutral wire often carries current. If the load is very unbalanced, the neutral wire can overheat and even catch fire. This is why electricians must carefully distribute single-phase loads (Lights, ACs) equally across R, Y, and B phases to keep the system as “Balanced” as possible.
- **Motor Protection Relays:** In modern factories, we use “Phase Failure Relays.” If the supply becomes unbalanced (e.g., one fuse blows), the relay senses the imbalance and trips the motor instantly to prevent it from burning out.

#### 4. Summary & Q&A (5 Minutes)

##### Quick Recap:

- **Phase Sequence:** The order R-Y-B. Swap any two to reverse motor direction.
- **Balanced Load:** Identical Z in all phases. No neutral current ( $I_N = 0$ ).
- **Unbalanced Load:** Different Z. Neutral current exists ( $I_N \neq 0$ ).

##### Typical Student Doubt: “Sir, does a balanced load require a neutral wire?”

- **Answer:** Theoretically, no! Since the neutral current is zero, you can remove the wire. That’s why 3-phase motors (delta connected) have only 3 wires and no neutral.

---

##### Mentor’s Career Tip

“In the industry, ‘Balancing the Load’ is a daily task for maintenance engineers. If you can analyze a distribution panel and suggest how to move loads from Phase R to Phase B to balance the system, you save the company energy and equipment wear. That’s the kind of practical skill that gets you promoted!”

## Topic 4: Values of Voltage and Current in Three Phase System

---

### Lecture: Decoding the Meter – Line vs. Phase Values

**Topic: Values of voltage and current in three phase system: Define terms - line voltage, phase voltage, line current, and phase current.**

**Duration: 60 Minutes**

**Reference: Unit 4, Topic 4**

---

#### 1. Hook / Introduction (5 Minutes)

**“The 440V Mystery”** Good morning, class! Let me start with a question you might have heard outside the classroom. You know that standard household voltage in India is **230V**. But when you walk past a large distribution box or a factory motor, you see a danger sign that says **“440V”** or **“415V”**.

How can the same system have two different voltage ratings? Is it magic? No, it’s geometry.

The difference lies in where you place your multimeter probes. Today, we are going to clear up the biggest source of confusion for electrical students: the difference between **Line Values** and **Phase Values**. If you master this definition today, you will never burn out a motor or a meter in your career.

---

#### 2. Core Concepts (40 Minutes)

**A. The Setup: Wires and Windings** To understand these definitions, visualize a 3-Phase system (like an alternator or a motor) which has three windings (coils) and three outgoing wires (lines) R, Y, and B.

#### B. Defining Voltage Values


##### 1. Phase Voltage ( $V_{ph}$ )

- **Definition:** The potential difference measured across **one single phase winding** or between one Line conductor and the Neutral point.
- **The “Home” Analogy:** This is what you have at home. One wire comes from the pole (Line), and one is Neutral.
- **Standard Value:** In India,  $V_{ph} = 230V$ .
- **How to Measure:** Connect voltmeter between **Line R** and **Neutral**.
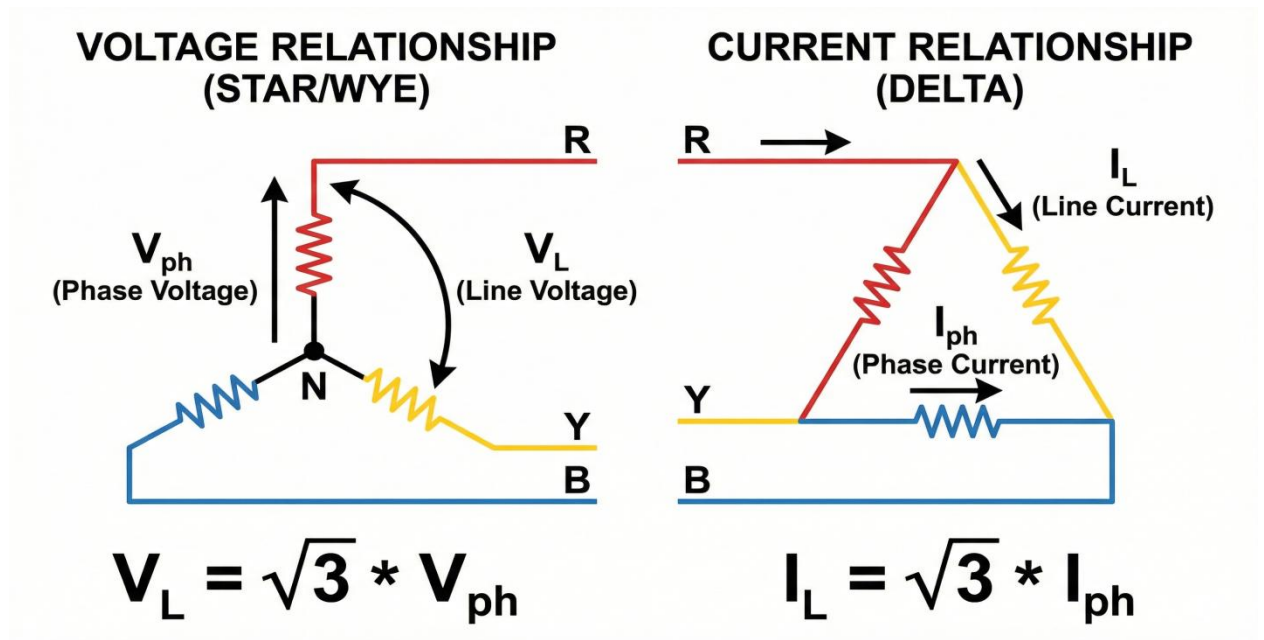
##### 2. Line Voltage ( $V_L$ )

- **Definition:** The potential difference measured between **any two Line conductors**.
- **The “Industry” Analogy:** This is the “heavy duty” voltage used for big motors.
- **Standard Value:** In India,  $V_L = 400V - 415V$ .
- **How to Measure:** Connect voltmeter between **Line R** and **Line Y** (or Y-B, or B-R).
- **Key Relationship:**  $V_L$  is always larger than  $V_{ph}$ . Specifically,  $V_L = \sqrt{3} \times V_{ph}$ . (We will prove this in the next lecture on Star connections).

**Visual Description for Board Work:** Draw a Star-connected system (Y-shape). \* Draw arrows from the center point (Neutral) to the tip of one arm (R). Label this  $V_{ph}$ . \* Draw arrows connecting the tip of arm R to the tip of arm Y. Label this  $V_L$ .



### C. Defining Current Values

#### 1. Line Current ( $I_L$ )

- **Definition:** The current flowing through any **Line conductor** (the wire connecting the supply to the load).
- **Visualization:** Imagine the wire coming out of the generator terminal. The current in that wire is  $I_L$ .

#### 2. Phase Current ( $I_{ph}$ )

- **Definition:** The current flowing through **one single phase winding** or component (impedance).
- **Visualization:** Imagine the current actually passing through the copper coil inside the motor. That is  $I_{ph}$ .

### D. The Twist: Star vs. Delta Behavior

- **In Star Connection:** The wire is directly connected to the winding. So, the current in the line is the current in the winding.
  - **Rule:**  $I_L = I_{ph}$  (Current is same) but  $V_L > V_{ph}$ .
- **In Delta Connection:** The line current splits into two paths at the junction.
  - **Rule:**  $V_L = V_{ph}$  (Voltage is same) but  $I_L > I_{ph}$ .

**Visual Description for Board Work:** \* **Diagram 1 (Star):** Trace a path from the wire into the coil. Show there is no junction. Write " $I_L = I_{ph}$ ". \* **Diagram 2 (Delta):** Trace a path from the wire hitting a corner of the triangle. Show it splits. Write " $I_L = \sqrt{3}I_{ph}$ ".

### 3. Real-World / Industry Applications (10 Minutes)

- **The Multimeter Test:** When you go to an industry, if you check the nameplate of a 3-Phase Induction Motor, you will often see “415V / 50Hz”. This always refers to the **Line Voltage**. Unless specified otherwise, industry ratings are always Line values.
  - **Safety Precaution:** If you mistakenly touch two active wires (Line-to-Line), you get a 415V shock. If you touch one wire and the ground (Line-to-Ground), you get a 230V shock. Both are dangerous, but the 415V shock is far more lethal. This is why 3-phase breakers are much larger and robust than household switches.
- 

### 4. Summary & Q&A (5 Minutes)

#### Quick Recap:

- $V_{ph}$ : Voltage across one coil (or Line-to-Neutral). Standard: 230V.
- $V_L$ : Voltage between two lines. Standard: 415V.
- $I_{ph}$ : Current inside the winding.
- $I_L$ : Current in the supply wire.

**Typical Student Doubt:** “Sir, is Line Voltage just the arithmetic sum of two Phase Voltages (230 + 230 = 460V)?”

- **Answer:** No! Because they are AC phasors with a  $120^\circ$  angle, they add vectorially. The math is  $2 \times 230 \times \cos(30^\circ) = 230 \times \sqrt{3} \approx 400V$ .
- 

#### Mentor’s Career Tip

“When you face a technical interview, the interviewer might simply ask: ‘What is the relation between Line and Phase voltage?’ Don’t just give the formula. Ask them ‘In Star or Delta?’ asking that clarifying question shows you think like an engineer, not just a student who memorized a book.”

## Topic 5: Three Phase Star Connection.

---

### Lecture: The Star Connection – The Heart of Distribution

#### Topic: Three Phase Star Connection (Y)

Duration: 60 Minutes

Reference: Unit 4, Topic 5

---

#### 1. Hook / Introduction (5 Minutes)

**“The Mercedes Logo & Your Home Socket”** Good morning, engineers! Visualize the famous Mercedes-Benz logo—a three-pointed star inside a circle. That shape isn’t just a car symbol; it represents the most common electrical connection in the world: the **Star Connection**.

Think about this: The high-voltage lines running on towers outside are 3-phase (400V+). Yet, the socket you use to charge your phone is single-phase (230V). How do we get a single phase out of a three-phase system? The answer lies in the magic of the **Star Connection** and its secret weapon: the **Neutral Wire**.

Today, we decode the “Star” (Y) configuration. This is the setup that powers everything from the Alternator in a power plant to the distribution box outside your house.

---

#### 2. Core Concepts (40 Minutes)

**A. The Construction (Tying the Knots)** Imagine you have three separate coils (R, Y, B). Each coil has a “Start” end and a “Finish” end.


- To form a Star connection, we take the **three “Finish” ends** (or three “Start” ends) and tie them together at a common junction point.
- This common point is called the **Neutral Point (N)**.
- The remaining three ends are brought out as Line Conductors (R, Y, B).
- This gives us a **3-Phase, 4-Wire System**.

**Visual Description for Board Work:** Draw three coils arranged in a “Y” shape, meeting at the center. Label the center “N”. Label the outer tips R, Y, and B. Draw a wire coming from N (dotted line) and label it “Neutral Wire”.

**B. Current Relationship ( $I_L$  vs  $I_{ph}$ )** Look at your diagram. Trace the path of current coming from the Line wire (R). It enters the coil directly. There is no split, no diversion. The current flowing in the line is the exact same current flowing through the phase winding.

- **Conclusion:** In a Star connection, **Line Current = Phase Current.**
- **Formula:**

$$I_L = I_{ph}$$

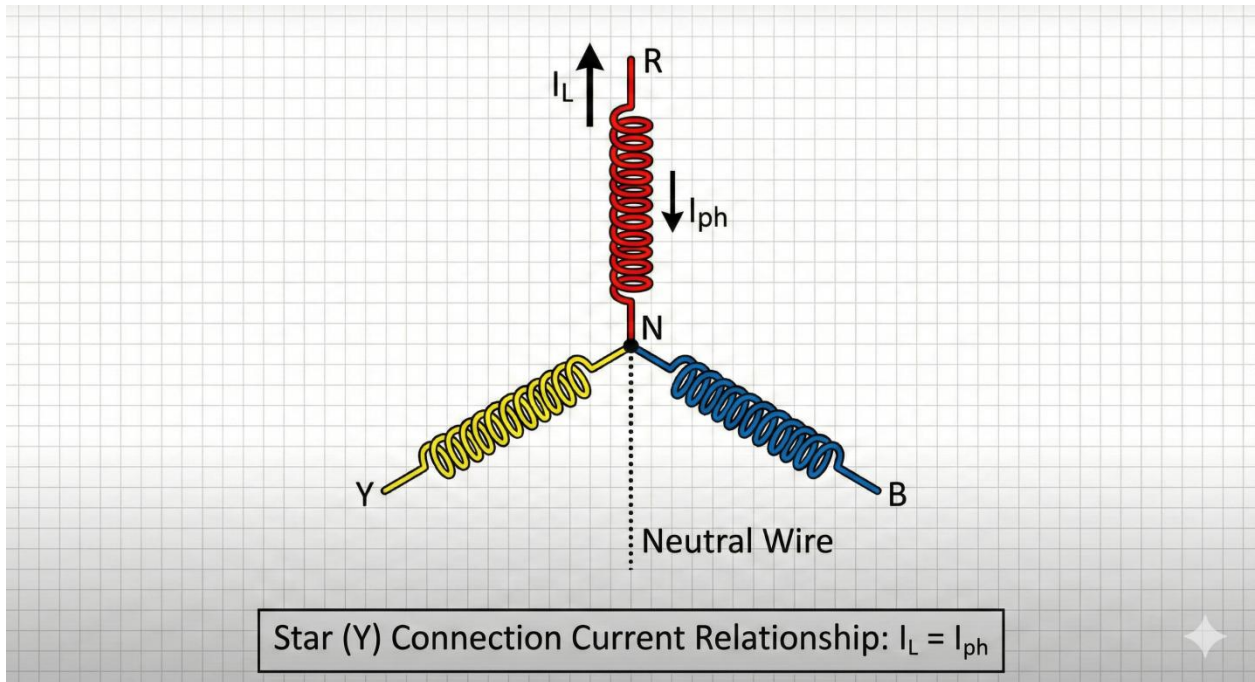

**C. Voltage Relationship ( $V_L$  vs  $V_{ph}$ )** Now, look at the voltage.


- **Phase Voltage ( $V_{ph}$ )** is measured between a Line (R) and the Neutral (N).
- **Line Voltage ( $V_L$ )** is measured between two Lines (R and Y).
- If you look at the phasor diagram, the Line Voltage is actually the **vector difference** of two Phase Voltages (e.g.,  $V_{RY} = V_R - V_Y$ ).
- Because the phases are  $120^\circ$  apart, the geometry (using a  $30^\circ$  bisector) gives us a specific multiplier:  $\sqrt{3}$  or **1.732**.
- **Conclusion:** Line Voltage is  $\sqrt{3}$  times the Phase Voltage.
- **Formula:**

$$V_L = \sqrt{3}V_{ph}$$

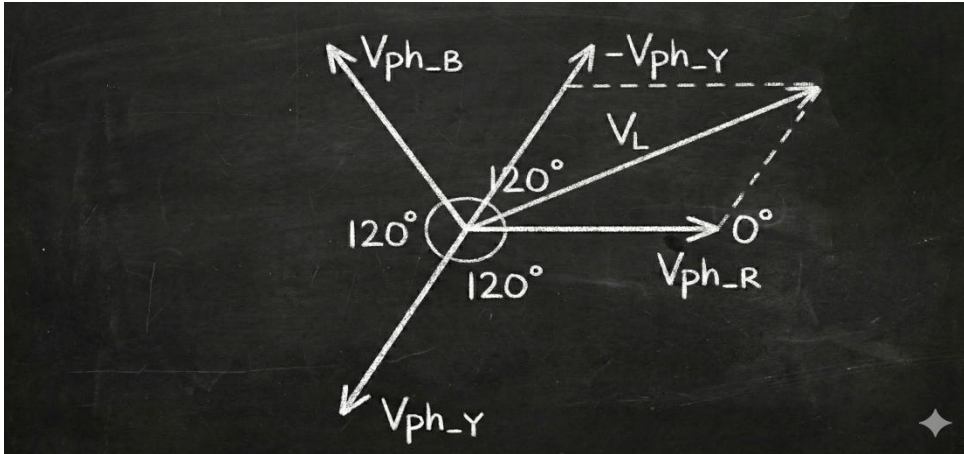**D. Power Calculation** Since total power is the sum of power in three phases ( $3 \times V_{ph} \times I_{ph} \times \cos\phi$ ), if we substitute our Line values into this, we get the universal 3-phase power equation:

$$P = \sqrt{3}V_L I_L \cos\phi$$

**Visual Description for Board Work:** Draw a Phasor diagram. Show  $V_R, V_Y, V_B$  at  $120^\circ$ . Reverse vector  $V_Y$  to get  $-V_Y$ . Add  $V_R$  and  $-V_Y$  using the parallelogram law to show the resultant  $V_L$  is longer than  $V_{ph}$ .



### 3. Real-World / Industry Applications (10 Minutes)

- **Power Distribution:** This is the #1 use case. Your local transformer is “Delta-Star”. The secondary side is Star-connected so that the utility company can give you a Neutral wire. This allows them to send 415V ( $V_L$ ) to a flour mill and 230V ( $V_{ph}$ ) to your house from the **same** transformer.
- **Alternators:** Almost all electricity generators (Alternators) are Star-connected. Why? Because the Neutral point can be grounded (Earthed), which protects the expensive generator from faults and lightning strikes.

### 4. Summary & Q&A (5 Minutes)

#### Quick Recap:

3. **Connection:** End-to-End joined at Neutral.
4. **Current:**  $I_L = I_{ph}$  (Same).
5. **Voltage:**  $V_L = \sqrt{3}V_{ph}$  (Line is higher).
6. **System:** 3-Phase, 4-Wire.

**Typical Student Doubt:** “Sir, if  $I_L = I_{ph}$ , does that mean the Neutral wire carries  $3 \times I_{ph}$ ?”

- **Answer:** No! Remember phasor addition? In a **Balanced Load** (as defined in Topic 3), the three currents cancel each other out, and the current in the Neutral wire is **Zero**. That’s why the neutral wire is often thinner than the line wires!

#### 💡 Mentor’s Career Tip

“In your upcoming Practical 12, you will verify these relations using voltmeters and ammeters. Pay attention there. When you graduate and work in maintenance, knowing that ‘**Star gives me a Neutral**’ is the key to solving half of your wiring problems. If a machine needs 230V control power but you only have a 415V supply, looking for that Star point is your solution!”

## Topic 6: Three Phase Delta Connection.

---

### Lecture: The Delta Connection – The Powerhouse Configuration

#### Topic: Three Phase Delta Connection ( $\Delta$ )

Duration: 60 Minutes

Reference: Unit 4, Topic 6;

---

#### 1. Hook / Introduction (5 Minutes)

**“The Triangle of Torque”** Welcome back, engineers! In our last session, we looked at the “Star” connection, which gave us the useful Neutral wire for our lights and fans. But today, we are going to look at the brute force of the electrical world: the **Delta Connection** (Mesh Connection).

Imagine a group of three people holding hands in a circle. If one person pulls, the force is transferred around the loop. This is the logic of the Delta connection. It forms a closed loop—a triangle ( $\Delta$ ).

**Thought Question:** If I connect three voltage sources in a closed loop, shouldn't it cause a massive short circuit? Spoiler: It doesn't! And understanding why is the key to unlocking the secret of how industrial motors generate massive torque. Let's dive in.

---

#### 2. Core Concepts (40 Minutes)

**A. The Construction (The Ring Road)** Unlike the Star connection where all ends meet at a central neutral point, the Delta connection is a series loop.

1. **Connection Logic:** We connect the **Finish** end of the first coil to the **Start** end of the second coil.
2. **The Loop:** Finish of 2 → Start of 3. Finish of 3 → Start of 1.
3. **Terminals:** The three junction points where the coils meet are tapped out as the Line conductors (R, Y, B).
4. **No Neutral:** Notice something missing? There is no center point. Therefore, a **Delta system is a 3-Phase, 3-Wire system.**

**Visual Description for Board Work:** Draw three coils arranged in a triangle ( $\Delta$ ). Label the corners R, Y, and B. Show that the wire R is connected directly to the junction of Coil 1 and Coil 3.

**B. Voltage Relationship ( $V_L$  vs  $V_{ph}$ )** Look closely at your diagram.

- Place your voltmeter probes across **Line R** and **Line Y**.
- Now look at the coil connected between these two points. It is the **Phase winding** itself!
- Therefore, the voltage across the line wires is exactly the same as the voltage across the coil.
- **Rule:** In Delta, **Line Voltage = Phase Voltage.**
- **Formula:**

$$V_L = V_{ph}$$


### C. Current Relationship ( $I_L$ vs $I_{ph}$ )

Now, let's look at the current.

- Current comes in from Line R. When it hits the corner of the triangle, it splits into two paths (some goes to Phase 1, some to Phase 3).
- According to Kirchhoff's Current Law (KCL), the Line Current is the **vector difference** of the two Phase Currents ( $I_R = I_{RY} - I_{BR}$ ).
- Using phasor algebra (just like we did for voltage in Star), the  $120^\circ$  displacement results in a factor of  $\sqrt{3}$ .
- **Rule:** Line Current is  $\sqrt{3}$  times the Phase Current.
- **Formula:**

$$I_L = \sqrt{3} \times I_{ph}$$

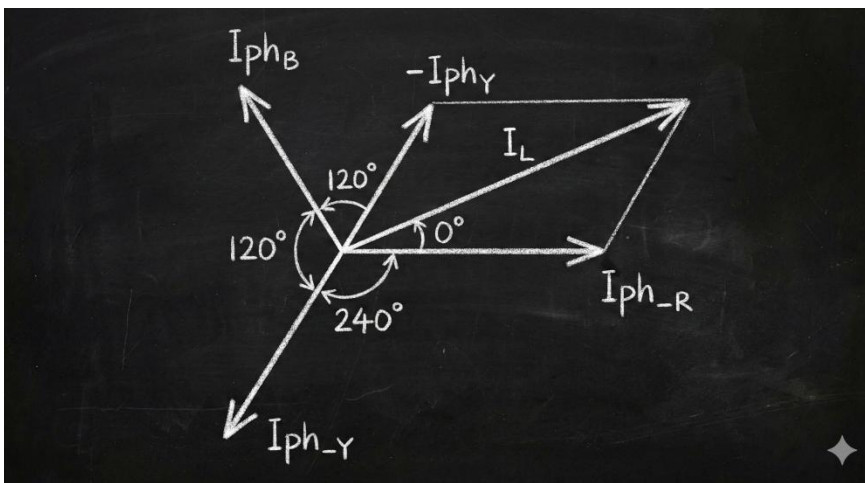**Visual Description for Board Work:** Draw a Phasor diagram. Show three phase currents  $I_{RY}$ ,  $I_{YB}$ ,  $I_{BR}$ . Perform vector subtraction to show the resultant Line Current ( $I_L$ ) is larger than the individual Phase Currents.



### D. Power Calculation

The power formula remains consistent for any 3-phase system:

- **Total Power (P)** =  $\sqrt{3} \times V_L \times I_L \times \cos\phi$
- Note: Even though the internal voltage/current relations are different from Star, the final power calculation using Line values is identical.

---

### 3. Real-World / Industry Applications (10 Minutes)

- **Induction Motors:** This is the most common application. 90% of industrial motors run in Delta configuration. Why? Because  $V_{ph} = V_L$ . If you have a 415V supply, the full 415V is applied across the motor coils, producing maximum torque.
  - **Distribution Transformers:** The primary windings of distribution transformers are usually Delta-connected. This allows the transformer to block "Third Harmonic" currents from reaching the transmission lines, keeping the grid clean.
  - **Rotary Converters:** Used in heavy industries where high current output is needed (since  $I_L$  is magnified by  $\sqrt{3}$ ).
-

#### 4. Summary & Q&A (5 Minutes)

##### Quick Recap:

- **Connection:** End-to-Start Loop.
- **Wires:** 3-Phase, 3-Wire (No Neutral).
- **Voltage:**  $V_L = V_{ph}$  (Same).
- **Current:**  $I_L = \sqrt{3}I_{ph}$  (Line current is higher).

**Typical Student Doubt:** “Sir, you said the voltages sum to zero in the loop. But what if one coil is wrongly connected?”

- **Answer:** Excellent question! If you reverse one coil in the Delta loop, the voltages will not sum to zero. A huge circulating current will flow inside the closed triangle, even with no load attached, and the coils will burn out in seconds. This is why polarity testing is critical!

---

---

##### Mentor’s Career Tip

“Students, you will often hear the term **‘Star-Delta Starter’** in interviews. This is a clever method where a motor starts in ‘Star’ (to reduce the starting current) and then switches to ‘Delta’ (to run at full power). If you can draw the control circuit for a Star-Delta starter during an interview, you are almost guaranteed a job in industrial automation!”

## Topic 7: Numerical based on three phase circuits.

This lecture synthesizes the theory from Star/Delta connections into practical problem-solving, directly addressing **Course Outcome 4 (CO4)** and preparing students for the **Numerical Problem Solving** activity suggested in the syllabus.

---

### Lecture: The Calculator as a Tool – Mastering 3-Phase Numericals

**Topic:** Numerical based on three phase circuits **Duration:** 60 Minutes **Reference:** Unit 4, Topic 7; Suggested Practical List 14 & 15.

---

#### 1. Hook / Introduction (5 Minutes)

**“The Million-Rupee Calculation”** Good morning, engineers! We have spent the last few lectures learning the theory of **Star (Y)** and **Delta (Δ)**. Today, we stop talking and start calculating.

Imagine you are a site engineer. A client asks, “I have a 10kW motor. What size cable do I need?” If you guess, the cable might burn (fire hazard) or be too thick (wasting money). You need an exact number.

Many students fear “Numericals” because they hate math. But in engineering, math is just a tool, like a screwdriver. Today, I will teach you the **“3-Step Protocol”** to solve any three-phase problem without confusion. Get your calculators out—let’s become engineers!

---

#### 2. Core Concepts (40 Minutes)

**A. The “Cheat Sheet” (5 Minutes)** Before we solve, we must have our weapons ready. Let’s write the Golden Rules on the board. (Students, write this at the top of your page!).

Connection	Voltage Relation	Current Relation	Power Formula
<b>Star (Y)</b>	$V_L = \sqrt{3}V_{ph}$	$I_L = I_{ph}$	$P = \sqrt{3}V_L I_L \cos\phi$
<b>Delta (Δ)</b>	$V_L = V_{ph}$	$I_L = \sqrt{3}I_{ph}$	$P = \sqrt{3}V_L I_L \cos\phi$

Note:  $V_L$  is Line Voltage (400V-415V),  $V_{ph}$  is Phase Voltage (230V).

**B. The 3-Step Protocol (Methodology)** Every problem in your exam can be solved using this sequence:

5. **Identify:** Is it Star or Delta? (This changes everything!)
6. **Convert:** Find the **Phase Values** ( $V_{ph}$ ,  $I_{ph}$ ) first. Never calculate using Line values directly inside the load impedance.
7. **Scale Up:** Convert back to **Line Values** ( $I_L$ ) and calculate Total Power.

#### C. Solved Problem 1: The Star Load (15 Minutes)

- **Problem:** A balanced 3-phase Star-connected load has an impedance of  $10\Omega$  per phase. It is connected to a 400V, 50Hz supply. Calculate: (a) Phase Voltage, (b) Phase Current, (c) Line Current, (d) Total Power (assuming UPF).

- **Solution:**

1. **Identify:** Connection = **Star**. Supply = **Line Voltage ( $V_L$ ) = 400V**.

2. **Step 1 (Find  $V_{ph}$ ):** In Star,  $V_L = \sqrt{3}V_{ph}$ .

$$V_{ph} = 400/1.732 = 230.9V$$

3. **Step 2 (Find  $I_{ph}$ ):** Ohm's Law applies to the phase.

$$I_{ph} = V_{ph}/Z = 230.9/10 = 23.09A$$

4. **Step 3 (Find  $I_L$ ):** In Star, Current is same.

$$I_L = I_{ph} = 23.09A$$

5. **Step 4 (Total Power):**

$$P = \sqrt{3} \times V_L \times I_L \times \cos\phi$$

$$P = 1.732 \times 400 \times 23.09 \times 1 = 16,000W \text{ or } 16kW$$

**Visual Description:** Draw a Star circuit. Label  $V_L$  between two outer wires (400V) and  $V_{ph}$  across one coil (231V). Show the calculation flow clearly on the board.

#### D. Solved Problem 2: The Delta Load (15 Minutes)

- **Problem:** The same three coils ( $10\Omega$  each) are re-connected in Delta across the same 400V supply. Calculate Line Current and Power.

- **Solution:**

6. **Identify:** Connection = **Delta**.

7. **Step 1 (Find  $V_{ph}$ ):** In Delta, Voltage is same.

$$V_{ph} = V_L = 400V$$

(Notice the difference! The coil gets full 400V now).

8. **Step 2 (Find  $I_{ph}$ ):**

$$I_{ph} = V_{ph}/Z = 400/10 = 40A$$

9. **Step 3 (Find  $I_L$ ):** In Delta, Line current splits.

$$I_L = \sqrt{3} \times I_{ph} = 1.732 \times 40 = 69.28A$$

10. **Step 4 (Total Power):**

$$P = 1.732 \times 400 \times 69.28 \times 1 = 48,000W \text{ or } 48kW$$

#### E. The "Aha!" Moment Compare the power: **Star (16kW)** vs **Delta (48kW)**.

- $16 \times 3 = 48$ .
- **Concept:** A Delta connection draws **3 times more power** than a Star connection for the same load. This validates the practical syllabus outcome of "Testing relation between power consumption in star and delta".

---

### 3. Real-World / Industry Applications (10 Minutes)

- **The Star-Delta Starter:**
    - Why do we use those big grey boxes to start motors? Look at our math.
    - In **Star**, the motor draws only **23A**. In **Delta**, it draws **69A**.
    - If we switch on a big motor directly in Delta, the huge current (69A+) acts like a hammer blow to the grid. So, we start it in **Star** (soft start) and after a few seconds, switch to **Delta** (full power).
  - **Cable Sizing:**
    - As an engineer, you size cables based on **Line Current ( $I_L$ )**. If you miscalculate Delta current as Star current, your wire will be too thin and will melt.
- 

### 4. Summary & Q&A (5 Minutes)

#### Quick Recap:

8. **Star:** High Voltage on Line, Low Voltage on Phase. ( $I_L = I_{ph}$ ).
9. **Delta:** High Voltage on Phase. ( $I_L > I_{ph}$ ).
10. **Power:**  $\sqrt{3}V_L I_L \cos\phi$ .

**Typical Student Doubt:** “Sir, why do we use  $\sqrt{3}$  in the power formula for both Star and Delta?”

**Answer:** Because the power formula uses **Line Values**. The factor of  $\sqrt{3}$  compensates for the internal differences (Voltage split in Star, Current split in Delta) automatically. It’s the universal formula!

---

#### Mentor’s Career Tip

“In your next job interview, they won’t ask you to derive a theorem. They will ask: ‘I have a 10HP motor. What is the full load current?’ If you can pull out your phone calculator, apply  $P = \sqrt{3}VI\cos\phi$ , and give an answer within 30 seconds, you are hired. Practice these numericals—they are the language of your profession.”

## Student AI Toolkit: Three Phase System and Circuits

### A. Low-Level Prompts (10 Prompts)

**Goal:** Master the basics, definitions, and theory questions. Use these to build your foundation.

1. "Explain the difference between a single-phase and a three-phase system in simple language suitable for a diploma engineering student. Use a real-life analogy."
  2. "What are the main advantages of using a three-phase system over a single-phase system for power transmission?"
  3. "Define the terms 'Phase Sequence', 'Balanced Load', and 'Unbalanced Load' in the context of electrical circuits. Give one simple example for each."
  4. "What is the principle of generating three-phase alternating voltage? Explain how the coils are arranged and how the voltage is induced."
  5. "Create a simple glossary of key terms for Three Phase Circuits including: Line Voltage, Phase Voltage, Line Current, and Phase Current."
  6. "State the mathematical relationship between Line Voltage and Phase Voltage for a Star connection. Just provide the formula and a brief sentence explaining it."
  7. "State the mathematical relationship between Line Current and Phase Current for a Delta connection. Just provide the formula and a brief sentence explaining it."
  8. "Why is the phase angle difference between the three phases exactly 120 degrees? Explain in 2-3 sentences."
  9. "What is the formula for calculating total power in a three-phase circuit? Explain what each symbol (P, V, I, cos phi) stands for."
  10. "Summarize the key differences between Star and Delta connections in a table format, comparing voltage, current, and number of wires."
- 

### B. Moderate-Level Prompts (10 Prompts)

**Goal:** Apply your knowledge to solve problems, analyze circuits, and understand "why" things work.

1. "I am confused about why Line Voltage is root 3 times Phase Voltage in a Star connection. Can you explain the phasor addition logic behind this derivation simply?"
2. "A 3-phase motor is connected in Delta. If the supply voltage is 415V, what is the voltage across each winding? Explain your reasoning."
3. "Compare a 'Balanced Supply' with an 'Unbalanced Supply'. What are the negative effects of an unbalanced supply on an electrical machine?"
4. "Generate a step-by-step guide to solving a numerical problem where I need to find the total power of a Star-connected load given the resistance per phase and line voltage."
5. "Why is a Neutral wire necessary in a Star-connected system with an unbalanced load, but optional for a balanced load? Explain with a practical example like a building's wiring."
6. "What happens to the direction of a 3-phase motor if I swap the Red (R) and Yellow (Y) phase wires? Explain the concept of Phase Sequence reversing."
7. "Draft a short explanation suitable for a viva exam on why industrial motors are preferred to be 3-phase rather than single-phase."

8. "Test me: Ask me 5 multiple-choice questions about Star vs Delta voltage and current relations. Don't show the answers immediately; let me guess first."
  9. "Explain the relationship between power consumption in a Star-connected load versus a Delta-connected load if the same resistors are used. Which one consumes more power and by how much?"
  10. "Visualize the waveform of a 3-phase system. Describe how the three sine waves overlap and identify the points where they cross the zero line."
- 

### C. High-Level Prompts (5 Prompts)

**Goal:** Design, create, and think like an engineer. Use these for projects and distinction-level prep.

1. "Design a simple troubleshooting flowchart for a factory electrician to check if a 3-phase motor is receiving a balanced supply. Include steps for measuring Line and Phase voltages."
2. "I need to build a physical model to demonstrate 'Generation of Alternating EMF' for my college project. Suggest a list of low-cost materials and a basic assembly plan."
3. "Create a 'Cheat Sheet' for 3-Phase Circuits that I can use for quick revision before the exam. Include all relevant formulas, circuit diagrams (described in text), and key theory points."
4. "Analyze the safety risks of a broken neutral wire in a 3-phase 4-wire distribution system supplying a residential building. What happens to the voltage across the appliances?"
5. "Imagine you are explaining the concept of 'Power Factor' in 3-phase circuits to a non-technical person. Write a script using an analogy like beer or a horse pulling a cart."

### Mastery Check: Three Phase System and Circuits

#### 1. Key Definitions / Glossary

**Objective:** Master the technical vocabulary required for Unit 4 exams, vivas, and practical sessions (Expt 12-15).

1. **Three Phase System:** A system of AC supply consisting of three voltages of the same magnitude and frequency but displaced from one another by 120 electrical degrees.
2. **Phase Sequence:** The specific order in which the voltages of the three phases (R, Y, B) reach their maximum positive value.
3. **Balanced Supply:** A three-phase supply where all three phase voltages are equal in magnitude and displaced by exactly 120°.
4. **Balanced Load:** A load where the impedance in all three phases is identical in magnitude and phase angle.
5. **Unbalanced Load:** A load condition where the impedances in the three phases are not identical, causing unequal currents to flow.
6. **Star Connection (Y):** A connection method where similar ends (Start or Finish) of the three coils are joined to form a common neutral point.
7. **Delta Connection ( $\Delta$ ):** A connection method where the starting end of one coil is connected to the finishing end of the next, forming a closed loop.

8. **Line Voltage ( $V_L$ ):** The potential difference measured between any two line conductors (e.g., between R and Y).
9. **Phase Voltage ( $V_{ph}$ ):** The potential difference measured across a single phase winding or between one line and the neutral point.
10. **Line Current ( $I_L$ ):** The current flowing through any one of the supply line conductors.
11. **Phase Current ( $I_{ph}$ ):** The current flowing through an individual phase winding or load component.
12. **Neutral Point:** The common junction point in a Star connection where the three phases meet, often connected to the ground.
13. **Phase Difference:** The angular displacement between the waveforms of the three phases, which is  $120^\circ$  or  $2\pi/3$  radians.
14. **Active Power ( $P$ ):** The total real power consumed by the three-phase circuit, calculated as  $P = \sqrt{3}V_L I_L \cos\phi$  for balanced loads.
15. **Rotating Magnetic Field (RMF):** The magnetic field produced by a three-phase system that rotates in space, essential for self-starting motors.

## 2. FAQ & Assessment Section

### A. Multiple Choice Questions (MCQs)

**Context:** These questions test the syllabus topics: Generation, Terminology, Star/Delta Connections, and Power Calculations.

1. **In a balanced three-phase voltage system, the phase difference between any two phases is:** A)  $90^\circ$  B)  $120^\circ$  C)  $180^\circ$  D)  $360^\circ$
2. **Which of the following is NOT a standard color code for a three-phase system?** A) Red (R) B) Yellow (Y) C) Blue (B) D) Green (G)
3. **In a Star connection, the relationship between Line Voltage ( $V_L$ ) and Phase Voltage ( $V_{ph}$ ) is:** A)  $V_L = V_{ph}$  B)  $V_L = \sqrt{3}V_{ph}$  C)  $V_L = V_{ph}/\sqrt{3}$  D)  $V_L = 3V_{ph}$
4. **In a Delta connection, the relationship between Line Current ( $I_L$ ) and Phase Current ( $I_{ph}$ ) is:** A)  $I_L = I_{ph}$  B)  $I_L = I_{ph}/\sqrt{3}$  C)  $I_L = \sqrt{3}I_{ph}$  D)  $I_L = 3I_{ph}$
5. **The standard phase sequence generally followed is:** A) R-B-Y B) R-Y-B C) Y-R-B D) B-R-Y
6. **In a balanced Star-connected system, the current flowing in the neutral wire is:** A) Maximum B) Equal to Line Current C) Zero D) Infinite
7. **Which connection system provides a Neutral point?** A) Delta Connection B) Star Connection C) Mesh Connection D) Series Connection
8. **For the same line voltage and current, the power in a 3-phase circuit is given by:** A)  $3V_L I_L \cos\phi$  B)  $\sqrt{3}V_L I_L \cos\phi$  C)  $V_L I_L \cos\phi$  D)  $3V_{ph} I_{ph} \cos\phi$
9. **In a Delta connection, the Line Voltage ( $V_L$ ) is equal to:** A) Phase Voltage ( $V_{ph}$ ) B)  $\sqrt{3} \times$  Phase Voltage C) Phase Voltage /  $\sqrt{3}$  D)  $3 \times$  Phase Voltage
10. **If the phase sequence of the supply to a 3-phase motor is reversed, the motor will:** A) Burn out B) Run at higher speed C) Run in the reverse direction D) Stop immediately

11. A 3-phase system is preferred over a 1-phase system because: A) It requires more copper B) It produces constant power and torque C) It is less efficient D) It is more complex
12. In a Star connection, the Line Current ( $I_L$ ) is: A) Equal to Phase Current ( $I_{ph}$ ) B)  $\sqrt{3}$  times Phase Current C) Less than Phase Current D) Zero
13. A “Balanced Load” implies that: A) Only resistance is equal in all phases B) Current is zero in all phases C) Impedance ( $Z$ ) is same in magnitude and angle in all phases D) Voltage is different in all phases
14. Which system requires only 3 wires for transmission? A) Star with Neutral B) Delta Connection C) Single Phase D) 2-Phase 3-Wire
15. If a 3-phase load consumes  $P$  watts in Star connection, how much power will it consume if reconnected in Delta across the same supply voltage? A)  $P$  (Same) B)  $3P$  C)  $P/3$  D)  $\sqrt{3}P$
16. The value of  $\sqrt{3}$  used in 3-phase calculations is approximately: A) 1.414 B) 1.732 C) 3.142 D) 0.707
17. Line voltage is measured between: A) One Phase and Ground B) One Phase and Neutral C) Any two Phase wires D) Neutral and Ground
18. In a 3-phase, 4-wire system, the fourth wire is used for: A) Protection B) Neutral return path C) Extra phase D) Communication
19. Identify the relation for Total Power ( $P$ ) using Phase values: A)  $P = \sqrt{3}V_{ph}I_{ph}\cos\phi$  B)  $P = 3V_{ph}I_{ph}\cos\phi$  C)  $P = V_{ph}I_{ph}\cos\phi$  D)  $P = 3V_L I_L \cos\phi$
20. The angle between the voltage vectors of R-phase and B-phase in a standard sequence is: A)  $120^\circ$  B)  $240^\circ$  C)  $90^\circ$  D)  $180^\circ$

## B. Short Answer / Viva Questions

**Context:** These questions emphasize reasoning and are suitable for the viva exams linked to experiments 12-15.

- Why are three-phase systems preferred over single-phase systems for power transmission?**
  - Reasoning: 3-phase systems are more efficient, use less conductor material (copper) for the same power transmitted, and provide constant (non-pulsating) power transfer.
- Explain the meaning of “Phase Sequence”. Why is it important in industry?**
  - Reasoning: It is the order (R-Y-B) in which voltages peak. It is crucial because reversing the sequence (e.g., to R-B-Y) reverses the direction of rotation of 3-phase induction motors.
- Differentiate between “Line Voltage” and “Phase Voltage”.**
  - Concept: Line voltage is measured between two live conductors ( $V_{RY}$ ), while Phase voltage is measured between one live conductor and the neutral point ( $V_{RN}$ ).
- Why is the Neutral wire needed in a Star-connected system?**
  - Justification: It provides a return path for the current in case of an **Unbalanced Load**. In a perfectly balanced load, the neutral current is zero, and the wire is theoretically optional.
- State the relationship between Line and Phase quantities in a Delta connection.**

- Concept:  $V_L = V_{ph}$  (Voltage is same across line and winding) and  $I_L = \sqrt{3}I_{ph}$  (Line current splits into phases).
6. **Justify why a Delta-connected load consumes 3 times more power than a Star-connected load for the same supply voltage.**
    - Reasoning: In Delta, the full Line Voltage is applied to the impedance ( $V_{ph} = V_L$ ), whereas in Star, only  $V_L/\sqrt{3}$  is applied. Since  $P = V^2/R$ , the factor of  $(\sqrt{3})^2$  results in 3 times the power.
  7. **Draw the vector diagram for a Balanced Star Connection.**
    - Task: (Student should draw three voltage vectors  $120^\circ$  apart and show Line voltage as the vector difference).
  8. **What is the condition for a “Balanced Load”?**
    - Definition: The impedance in each of the three phases must be identical in both magnitude (Resistance/Reactance) and phase angle.
  9. **Write the formula for 3-Phase Power using (a) Line values and (b) Phase values.**
    - Formula: (a)  $P = \sqrt{3}V_L I_L \cos\phi$  and (b)  $P = 3V_{ph} I_{ph} \cos\phi$ .
  10. **In which connection is Line Current equal to Phase Current?**
    - Concept: In the **Star Connection**, because the line conductor is connected directly in series with the phase winding.

#### Answer Key (MCQs)

Q.No	Answer	Q.No	Answer
1	B	11	B
2	D	12	A
3	B	13	C
4	C	14	B
5	B	15	B
6	C	16	B
7	B	17	C
8	B	18	B
9	A	19	B
10	C	20	B

### Digital Resource Library: Three Phase System and Circuits

#### 1. AI Tools & Digital Learning Tools

These tools are selected to help you visualize invisible concepts like “Phase Shift” and “Rotating Magnetic Fields,” and to safely simulate high-voltage 3-phase connections before entering the lab.

Tool Name	Type	Purpose / Use-Case for Unit 4	How it Helps Learning
<b>Virtual Labs</b> (vlab.co.in)	Virtual Simulation	<b>Virtual Experiments:</b> Specifically for verifying Line & Phase relations in Star/Delta connections (Expt 12 & 13) and measuring 3-phase power.	This government-backed tool allows you to connect meters and loads virtually. It is perfect for “pre-lab” practice to ensure you don’t make connection errors in the real hardware lab.
<b>Falstad Circuit Simulator</b>	Web-based Simulator	<b>Visualizing Current Flow:</b> Build a simple 3-phase source and load. Watch how current flows in the Neutral wire for balanced vs. unbalanced loads.	It animates the flow of electrons. You can clearly see why current returns through the neutral wire in unbalanced loads but cancels out to zero in balanced loads.
<b>GeoGebra</b>	Graphing Tool	<b>Phasor &amp; Waveform Plotting:</b> Plot three sine waves shifted by $120^\circ$ ( $0, 2\pi/3, 4\pi/3$ ) to see how they interact.	Helps you understand the “Generation of 3-Phase Voltage” by visually proving that the sum of three balanced voltages at any instant is zero.
<b>WolframAlpha</b>	Computational Engine	<b>Complex Algebra Solver:</b> Use it to solve “Star-Delta” conversion numericals and power calculations involving $\sqrt{3}$ .	3-Phase numericals often involve complex angles (e.g., $415\angle 30^\circ$ ). This tool validates your manual calculations instantly.

## 2. Video Learning Repository

This collection aligns with the syllabus references and focuses on Diploma-level clarity.

Topic Name	Recommended Channel / Source	Search Keywords (Copy & Paste these)
<b>Generation of 3-Phase Voltage</b>	<b>NPTEL (IIT Kharagpur)</b>	NPTEL Basic Electrical Technology Generation of Three Phase Voltage
<b>Star Connection (Line vs Phase)</b>	<b>Neso Academy</b>	Three Phase Circuits Star Connection Relation between Line and Phase Voltages
<b>Delta Connection (Line vs Phase)</b>	<b>Ekeeda / TicTechnical</b>	Delta Connection Line and Phase Current Relation

Topic Name	Recommended Channel / Source	Search Keywords (Copy & Paste these)
		derivation diploma
Balanced vs Unbalanced Load	Electrical4U / Last Moment Tutorials	Difference between balanced and unbalanced three phase load explained
Solving 3-Phase Numericals	Engineering Funda	Three phase circuit numericals star delta connection problems
Comparison: Single Phase vs 3-Phase	Learning Engineering	Advantage of 3 phase system over 1 phase system animation

 **Student Tips for Using These Resources:**

- **For Visualization:** Use Falstad to see the “phase shift” animation—it makes the concept of  $120^\circ$  displacement much clearer than a static textbook diagram.
- **For Exams:** The Neso Academy videos on Star/Delta derivations are excellent for preparing the 4-7 mark descriptive questions typically asked in GTU exams.
- **For Practicals:** Visit vlab.co.in before your actual lab session for “Expt 12 & 13” to practice the circuit connections safely.

Based on the syllabus for **AC Fundamentals (Subject Code: DI02000171)**, here is a designed **External Exposure Module**. This content bridges the gap between your classroom theory of sine waves and phasors and the dynamic world of modern electrical engineering.

---

 **External Exposure Module: AC Fundamentals**

**1. Beyond the Syllabus – Emerging Technologies**

**Objective:** To understand how the basic sine waves, impedance, and power factor concepts you study today evolve into cutting-edge technology.

**A. Smart Grids & Advanced Metering Infrastructure (AMI)**

- **The Connection:** In **Unit 1**, you learn about RMS values, instantaneous values, and power measurement. A standard energy meter measures this simply. A Smart Meter takes this further by measuring parameters (voltage sags, swells, and harmonics) in real-time and communicating two-way with the utility provider.
- **Why it Matters:** The power sector is aggressively moving towards Smart Grids. Understanding how AC parameters are monitored digitally is a key skill for future jobs in power distribution companies (DISCOMs).
- **B. Flexible AC Transmission Systems (FACTS)**
- **The Connection:** In **Unit 2 & 3**, you study Reactive Power, Power Factor, and Impedance. FACTS devices are essentially high-tech, automated versions of the capacitors and inductors you use in labs. They use power electronics to dynamically control the “Impedance” and “Phase Angle” of transmission lines to stabilize voltage.

- **Why it Matters:** As renewable energy grows, grid stability becomes harder to maintain. Knowing the basics of “Reactive Power Compensation” (a core outcome of this course ) puts you on the path to understanding these advanced grid stabilizers.

## 2. MOOC & Online Course Recommendations

**Objective:** To provide high-quality, self-paced learning resources that reinforce your diploma studies with visualizations and expert explanations.

Course Title / Theme	Platform	How it Complements Your Syllabus
Basic Electrical Circuits	NPTEL / SWAYAM	Recommended in your syllabus. It offers rigorous mathematical derivations for <b>Series and Parallel Resonance</b> , helping you master the complex algebra method mentioned in <b>Unit 3</b> .
Electric Power Systems	Coursera (Audit option)	Connects your <b>Unit 4 (Three Phase Systems)</b> to the real world of generation and distribution. It visualizes why we use 3-phase systems instead of single-phase for transmission.
Circuit Analysis	Khan Academy	Explicitly listed in your syllabus resources. Excellent for visual learners. It breaks down <b>Phasor Diagrams</b> and <b>Sinusoidal Functions</b> into very simple, bite-sized video lessons.

## 3. Industrial Exposure / Field Visit Suggestions (Regional Focus)

**Objective:** To observe “AC Fundamentals” (Star/Delta, Transformers, Generation) in action within the industrial ecosystem.

### A. 66kV/132kV Substations (e.g., GETCO - Gujarat Energy Transmission Corp.)

- **Type of Industry:** Power Transmission & Distribution.
- **What to Observe:**
  - **3-Phase Busbars:** See the actual physical arrangement of Red, Yellow, and Blue (R-Y-B) lines.
  - **Capacitor Banks:** Huge banks of capacitors used for **Power Factor Correction**, directly relating to concepts in **Unit 3**.
  - **B. Transformer Manufacturing Units (e.g., Voltamp, Shilchar)**
- **Type of Industry:** Electrical Equipment Manufacturing.

- **What to Observe:**
  - **Star & Delta Connections:** Witness the internal wiring of transformers to see how **Star (Y)** and **Delta ( $\Delta$ )** connections are physically made using copper windings.
  - **Inductive Loads:** See how pure inductance is created (choke coils/windings), reinforcing **Unit 2** concepts.

### C. Solar Parks or Rooftop Solar Installations

- **Type of Industry:** Renewable Energy Generation.
- **What to Observe:**
  - **Inverters:** Since solar panels produce DC, you will see huge Inverters converting DC to AC. This reinforces the “Comparison between AC and DC Systems” from **Unit 1**.
  - **Grid Synchronization:** Learn how the AC frequency generated is matched exactly to the 50Hz grid frequency.

## 4. Conferences, Seminars & Technical Events

**Objective:** To inspire professional growth and networking.

### A. ELECRAMA

- **Theme:** The world’s largest electrical show, often held in India (e.g., Greater Noida).
- **Why Benefit:** It showcases the entire electrical ecosystem from “Source to Socket.” You can see the latest AC circuit breakers, smart grids, and testing equipment. It gives you a vision of the scale of the electrical industry beyond the textbook.

### B. IEEE India Council / Gujarat Section Events

- **Theme:** Technical symposiums often held at major engineering colleges.
- **Why Benefit:** Attending student-level paper presentations exposes you to how other students are applying **AC principles** to build projects like “Wireless Power Transfer” or “Smart Home Automation.”

### C. Regional “Project Expos” (GTU TechFest)

- **Theme:** Final year project showcases.
- **Why Benefit:** Observing final year projects (often involving Induction Motors or Generators) helps you understand how the **Unit 4** (Three Phase) concepts are used to build working models.

Based on the syllabus for **AC Fundamental (Subject Code: DI02000171)**, specifically **Unit 4: Three Phase System and Circuits** which carries the highest weightage of **23%** (approx. 16-18 marks), here is the Predicted Question Bank.

This unit focuses on **Course Outcome 4 (CO4):** Apply principles of three phase system to solve electrical circuits. The questions are categorized by difficulty and type.

## Predicted Question Bank: Three Phase System and Circuits

### 1. Most Repeated / High-Probability Questions

**Context:** These questions cover the core content listed in the syllabus (Topics 1-6) and appear frequently in standard Diploma examinations.

### Short Answer Questions (2 - 3 Marks)

1. **Define the following terms:**
  - (a) Phase Sequence
  - (b) Balanced LoadReference: Syllabus Topic 4(3).
2. **State the relationship between Line Voltage & Phase Voltage and Line Current & Phase Current for:**
  - (a) Star Connection
  - (b) Delta ConnectionReference: Syllabus Topic 4(5) & 4(6).
3. **List three advantages of a Three Phase System over a Single Phase System.**
  - Reference: Syllabus Topic 4(1).
4. **Define Line Voltage and Phase Voltage.**
  - Reference: Syllabus Topic 4(4).
5. **Why is the phase difference between voltages in a 3-phase system exactly 120°?**
  - Reference: Syllabus Topic 4(2).
  -

### Descriptive / Derivation Questions (4 - 7 Marks)

6. **Explain the principle of generation of three-phase alternating voltage with a neat waveform diagram.**
  - Requirement: Draw the three sine waves displaced by 120° and the arrangement of coils.
  - Reference: Syllabus Topic 4(2).
7. **Derive the relationship between Line Voltage and Phase Voltage for a Star Connected system. Draw the necessary circuit and phasor diagrams.**
  - Key Focus: Prove  $V_L = \sqrt{3}V_{ph}$ .
  - Reference: Syllabus Topic 4(5).
8. **Derive the relationship between Line Current and Phase Current for a Delta Connected system. Draw the necessary circuit and phasor diagrams.**
  - Key Focus: Prove  $I_L = \sqrt{3}I_{ph}$ .
  - Reference: Syllabus Topic 4(6).
9. **Compare Star Connection and Delta Connection.**
  - Requirement: Comparison points should include: Connection diagram, Voltage relation, Current relation, Number of wires (3 vs 4), and application (Distribution vs Transmission/Motors).
  - Reference: Syllabus Topic 4(5) & 4(6).
10. **Draw a connection diagram of a 3-phase Star connection supplying a balanced load. Show Line Voltages ( $V_{RY}, V_{YB}, V_{BR}$ ), Phase Voltages ( $V_{RN}, V_{YN}, V_{BN}$ ), and currents.**
  - Reference: Syllabus Topic 4(5).

## 2. Application & Logical Thinking Questions

**Context:** These questions address the “Application (A)” and “Analyze (N)” levels of Bloom’s Taxonomy as specified in the Specification Table. They test if you can use the theory in practical scenarios.

1. **Problem Interpretation:**

- **Question:** A student connects three identical 100W bulbs in a **Star** configuration and then reconnects the same three bulbs in a **Delta** configuration across the same 3-phase supply. In which case will the total brightness (power consumption) be higher and by how much?
  - **Expected Logic:** Power in Delta is 3 times the Power in Star ( $P_{\Delta} = 3P_Y$ ). Therefore, the Delta connection is much brighter. This relates to Syllabus Topic 4(7) and Suggested Practical 15.
2. **System Understanding (Neutral Wire):**
- **Question:** In a 3-phase, 4-wire system powering a residential building, what happens to the potential of the neutral point if the **Neutral wire breaks**?
  - **Expected Logic:** If the load is Unbalanced (which is typical for buildings), a broken neutral causes “Floating Neutral.” Voltage across lightly loaded phases will rise dangerously (causing equipment damage), while voltage across heavily loaded phases will drop. This tests understanding of “Unbalanced Load”.
3. **Logical Reasoning (Phase Sequence):**
- **Question:** You are commissioning a 3-phase induction motor, but it is rotating in the reverse direction. Using your knowledge of “Phase Sequence,” what is the simplest way to fix this without changing the internal motor wiring?
  - **Expected Logic:** Swap any two of the three supply lines (e.g., swap R and Y). This reverses the phase sequence and thus the direction of the rotating magnetic field. Relates to Topic 4(3).
4. **Real-Life Application (Safety):**
- **Question:** Why is a 415V shock (Line-to-Line) considered more dangerous than a 230V shock (Line-to-Neutral), even though they come from the same supply panel?
  - **Expected Logic:** Application of the relation  $V_L = \sqrt{3}V_{ph}$ . The potential difference between two phases is significantly higher (1.732 times) than the phase voltage used for domestic appliances. Relates to Topic 4(4).
5. **Circuit Analysis (Numerical Setup):**
- **Question:** A motor nameplate reads “415V, Delta Connected”. If you accidentally connect it in Star Configuration to the 415V supply, will the motor produce its rated torque? Justify using voltage relationships.
  - **Expected Logic:** No. In Star, the voltage across each winding would be reduced to  $V_L/\sqrt{3}$  (approx 240V) instead of the designed 415V. The motor will run with significantly reduced torque (Torque  $\propto V^2$ ). Relates to Topic 4(5) & 4(6).

---

**Next Step for Student:** Would you like a **sample numerical problem** (Topic 4.7) involving calculation of Line Current and Total Power for a given Star/Delta load, complete with the step-by-step solution?